

Linear Circuits



Nathan V. Parrish

PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering



An introduction to linear electric circuit elements and a study of circuits containing such devices.

School of Electrical and Computer Engineering



Nathan V. Parrish

PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

Kirchhoff's Laws

- *Introduce Kirchhoff's Voltage Law (KVL) and apply to parallel circuits*
- *Introduce Kirchhoff's Current Law (KCL) and apply to series circuits*
- *Use Kirchhoff's Laws to solve a simple circuit*

Previous Class

- ⦿ Introduced Ohm's Law
 - ⦿ Introduced Resistance
 - ⦿ Calculated Resistance
 - ⦿ Equations for behavior *within* a device
- 


Module 2: Resistive Circuits

- ◎ Resistance and Ohm's Law
- ◎ Kirchhoff's Laws
- ◎ Resistors
- ◎ Superposition
- ◎ Obtaining Circuit Equations
- ◎ Maximum Power Transfer
- ◎ Wye-Delta and Wheatstone Bridge

Lesson Objectives

- ◎ Describe KVL and KCL
- ◎ Describe the voltage relationship of parallel elements
- ◎ Describe the current relationship of series elements
- ◎ Use Kirchhoff's Laws to find unknown values in a simple circuit


Kirchhoff's Voltage Law (KVL)

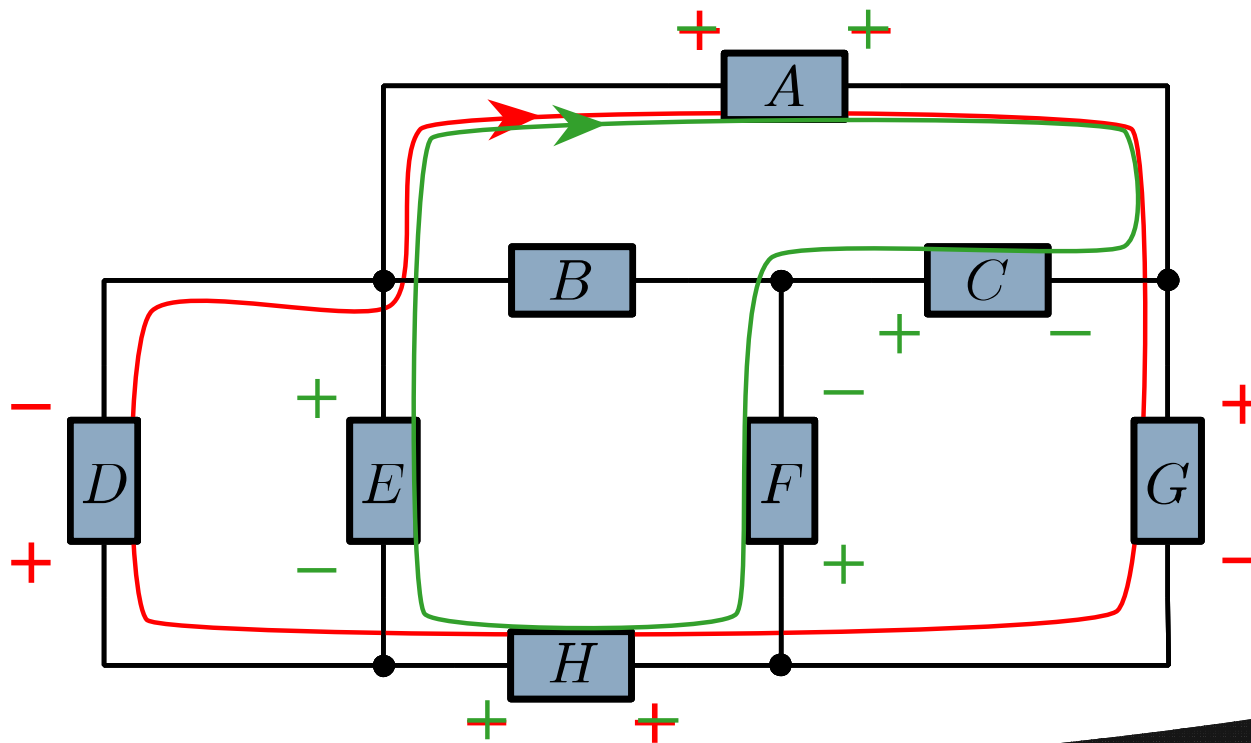

$$v_A + v_G + v_H + v_D = 0$$


$$0 = v_A + v_C + v_F + v_H + v_E$$

KVL and Parallel Circuits

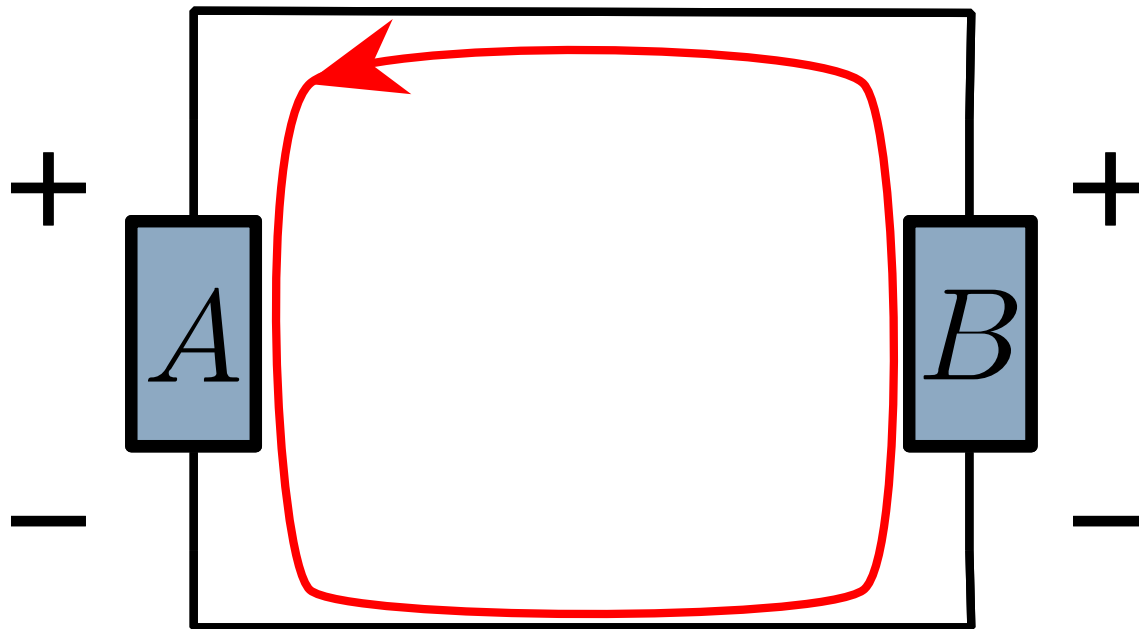


$$v_A - v_B = 0$$
$$v_A = v_B$$

Kirchhoff's Current Law (KCL)

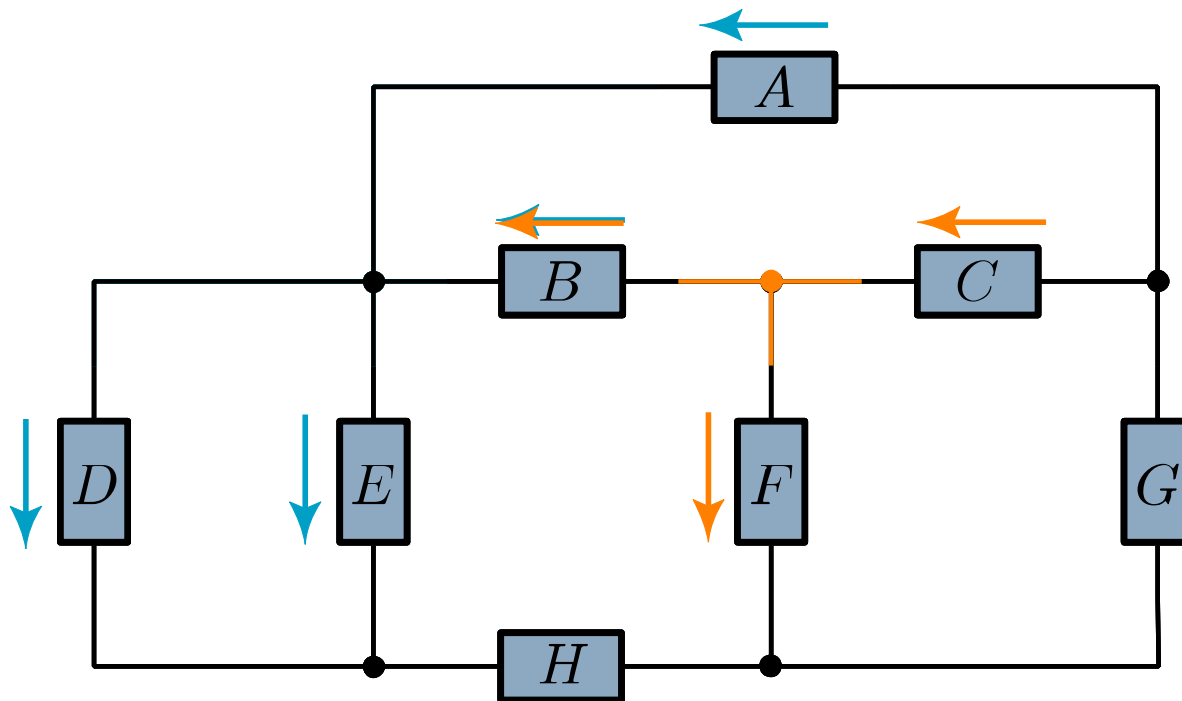


What if?

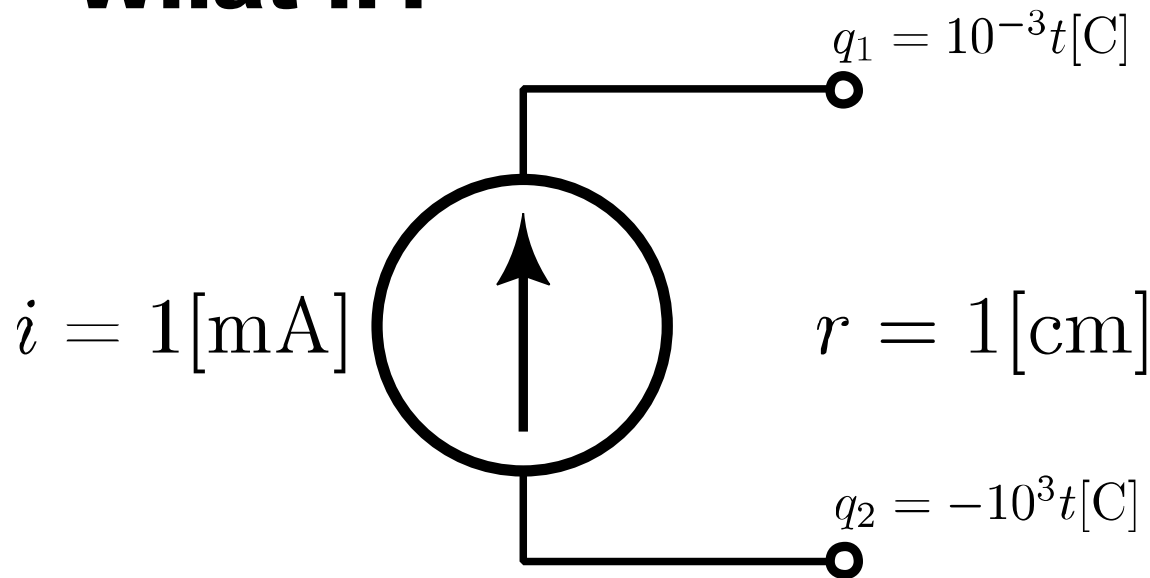

Time	$ F [\text{lbs}]$	$ F [\text{kg}]$
1ms	20.2	9.16
1s	20.2 M	9.16 M
2s	80.8 M	36.6 M


$$|F| = \frac{1}{4\pi\epsilon_0} \frac{|q_1 q_2|}{r^2} = \frac{1}{4\pi\epsilon_0} \frac{(10^{-3}t)(10^3t)}{(0.01)^2} = \frac{1}{4\pi\epsilon_0} \frac{10^{-6}t^2}{10^{-4}} = \frac{1}{4\pi\epsilon_0} 10^{-2}t^2$$

KCL and Series Circuits

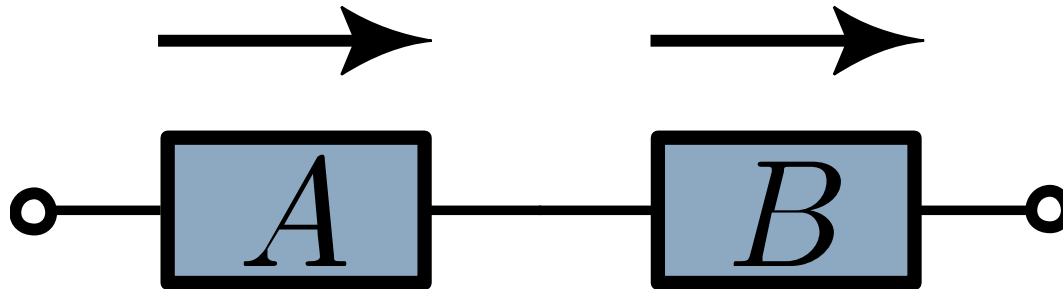

$$i_A = i_B$$

Solving Values in Circuits

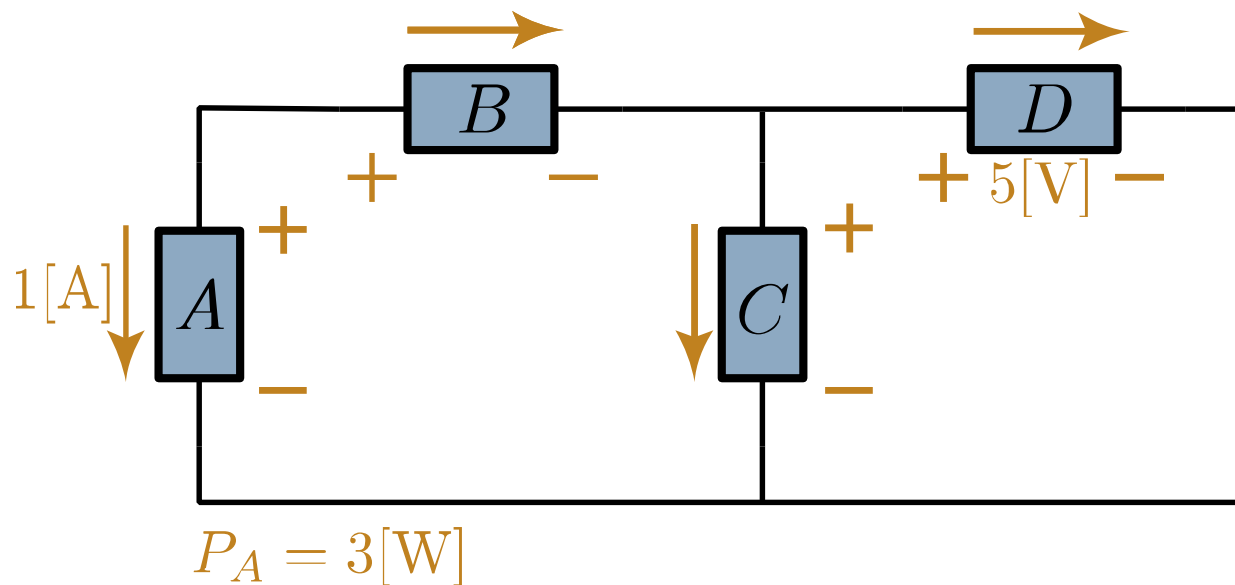

Summary

- ⦿ Introduced KVL and KCL
- ⦿ Applied KVL to parallel elements
- ⦿ Applied KCL to series elements
- ⦿ Gave a justification for KCL
- ⦿ Solved a simple circuit using Kirchhoff's Laws

Next Class

- ◎ Introduce resistors – devices specifically designed to inhibit current flow
- ◎ Apply Ohm's Law and Kirchhoff's Law to resistor circuits