

# Linear Circuits



**Nathan V. Parrish**  
PhD Candidate & Graduate  
Research Assistant  
School of Electrical and  
Computer Engineering



*An introduction to linear electric circuit elements and a study of circuits containing such devices.*

School of Electrical and Computer Engineering



**Nathan V. Parrish**

PhD Candidate & Graduate  
Research Assistant  
School of Electrical and  
Computer Engineering

# Resistors

- 
- *Introduce resistors as a circuit element*
  - *Consider resistors in series and parallel*
  - *Calculate equivalent resistance by combining parallel/series resistors*

## Previous Class

- ◎ Ohm's Law – current/voltage relationship within an element
  - ◎ Kirchhoff's Laws – relationships between elements in a circuit
- 


## **Module 2: Resistive Circuits**

- ◎ Resistance
- ◎ Kirchhoff's Laws
- ◎ Resistors
- ◎ Superposition
- ◎ Obtaining Circuit Equations
- ◎ Maximum Power Transfer
- ◎ Wheatstone Bridge

## Learning Objectives

- ◎ Apply Ohm's Law and Kirchhoff's Laws to simple resistive circuits
- ◎ Calculate an equivalent resistance of resistors in parallel/series
- ◎ Find equivalent resistance through successive application of combining parallel and series resistors


# Resistors

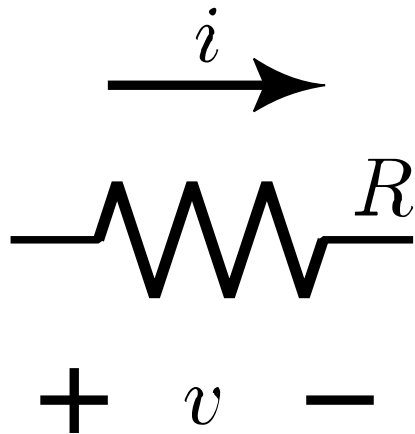

$$v = iR$$


# Review

Ohm's Law

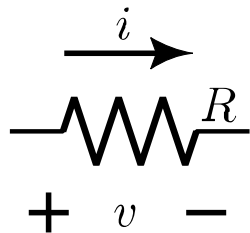


$$v = iR$$

Kirchhoff's Current Law

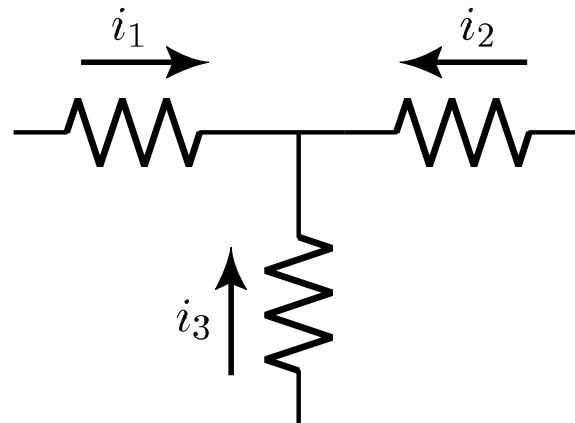


$$i_1 + i_2 + i_3 = 0$$

Kirchhoff's Voltage Law

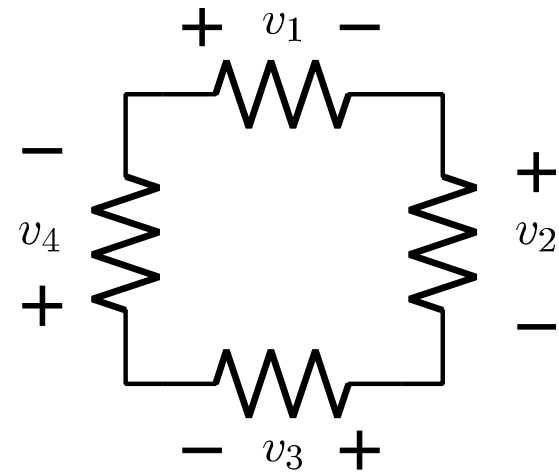

$$v_1 + v_2 + v_3 + v_4 = 0$$

## Resistors in Series

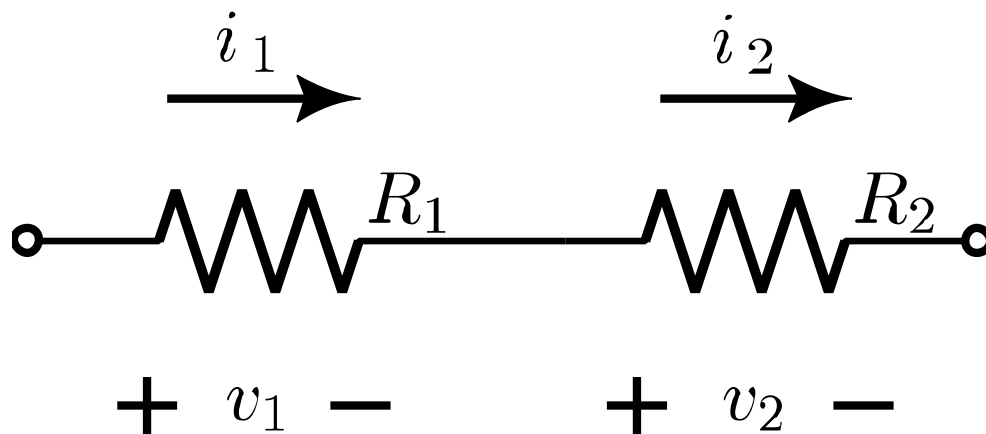

$$i_1 = i_2 = i$$


$$v_1 = iR_1 \quad v_2 = iR_2$$

$$v = v_1 + v_2 = i(R_1 + R_2)$$

$$R = \frac{v}{i} = R_1 + R_2$$


Pause

# Voltage Divider

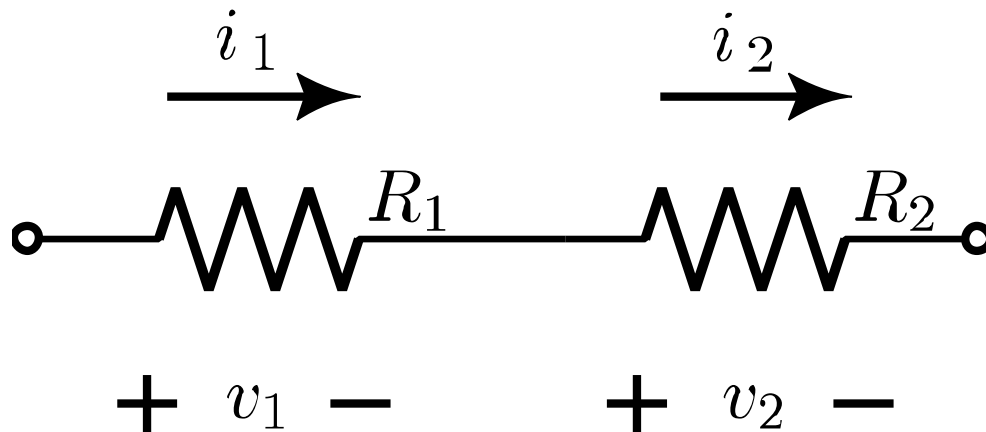

$$i = \frac{v}{R} = \frac{v}{R_1 + R_2}$$
$$v_1 = iR_1 = \frac{v}{R_1 + R_2} R_1 = \frac{R_1}{R_1 + R_2} v$$

## Resistors in Parallel

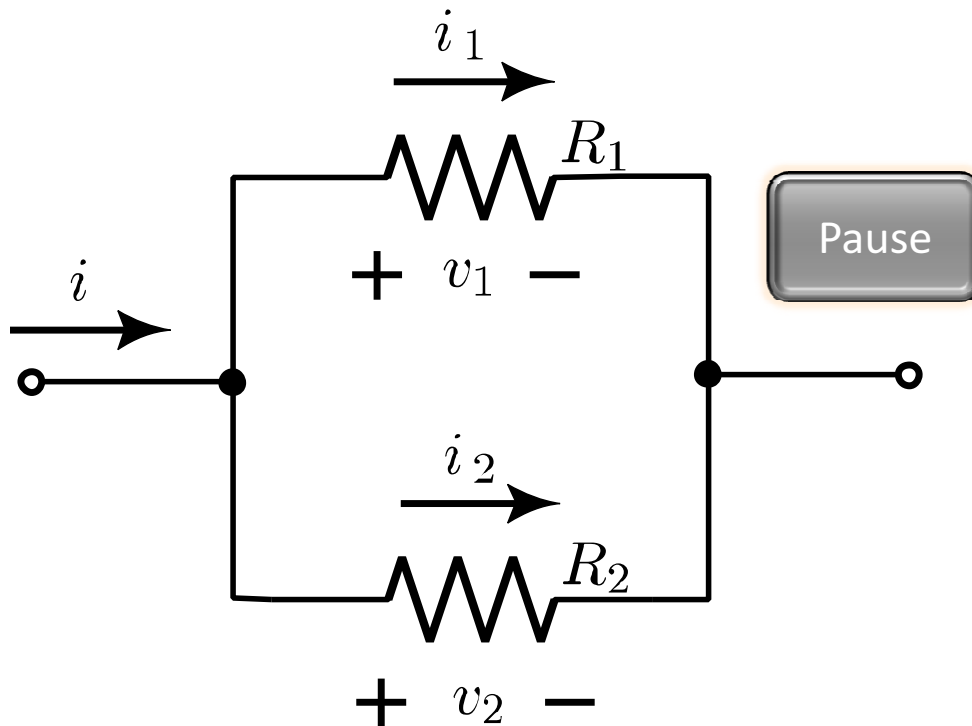

$$v_1 = v_2$$


$$i_1 = \frac{v}{R_1} = vG_1 \quad i_2 = \frac{v_2}{R_2} = vG_2$$

$$i = i_1 + i_2 = vG_1 + vG_2$$

$$G = \frac{i}{v} = G_1 + G_2$$

$$R = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

# Current Divider

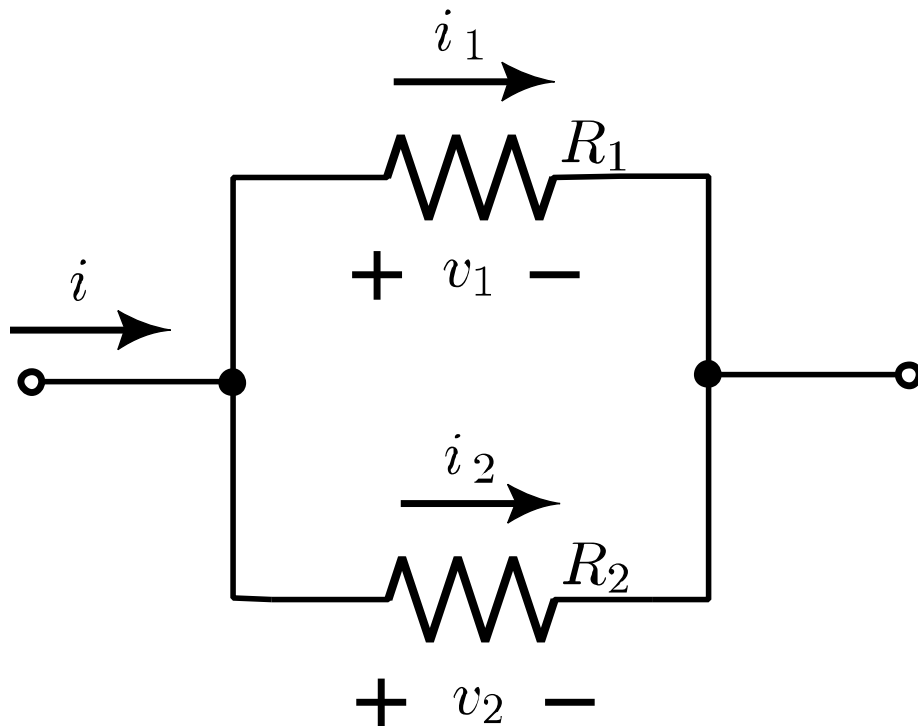


$$v = iR = \frac{i}{G_1 + G_2}$$

$$i_1 = \frac{v}{R_1} = vG_1 = \frac{G_1}{G_1 + G_2}i$$

$$\frac{G_1}{G_1 + G_2} = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{1}{1 + \frac{R_1}{R_2}} = \frac{R_2}{R_2 + R_1}$$

# Example

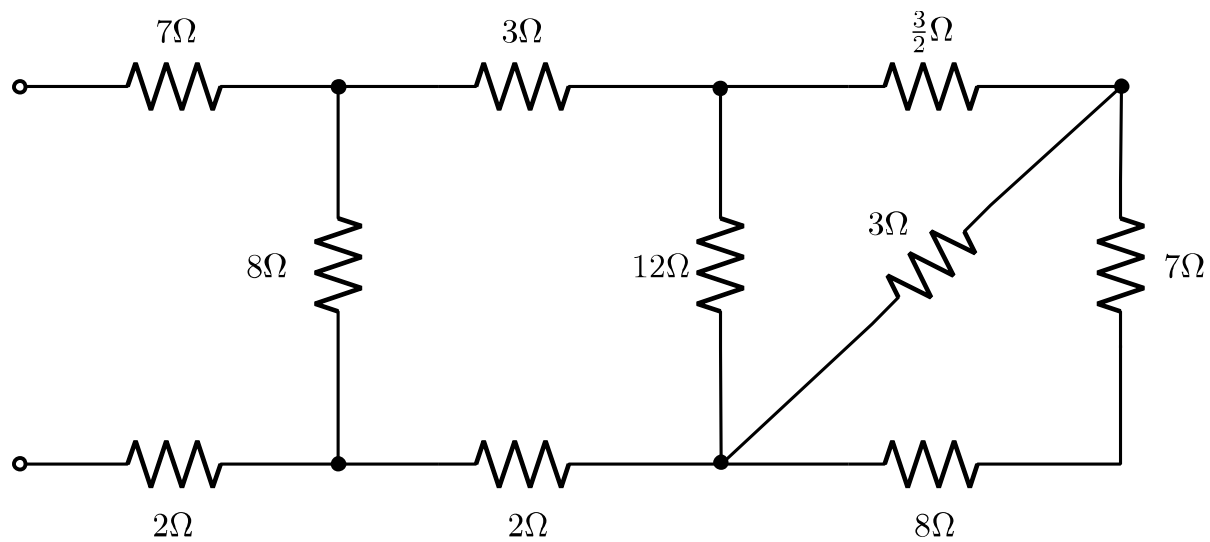

## Summary

- ⦿ Introduced to resistors as a circuit element
- ⦿ Combine series/parallel resistors
- ⦿ Found an equivalent resistance using successive application of series/parallel resistance

## Next Class

- ◎ Virtual lab: behavior of real resistors
- ◎ Superposition