

Linear Circuits



Dr. Bonnie Ferri
Professor and Associate Chair
School of Electrical and
Computer Engineering

An introduction to linear electric circuit elements and a study of circuits containing such devices.

School of Electrical and Computer Engineering



Dr. Bonnie Ferri
Professor and Associate Chair
School of Electrical and
Computer Engineering

Lab Demo: Resistors and Connections



Resistors in series and parallel, measuring voltage and current in circuits.

Module 2: Resistive Circuits


- ⦿ Resistance
- ⦿ Kirchhoff's Laws
- ⦿ Resistors
- ⦿ Superposition
- ⦿ Systematic Solution Methods
- ⦿ Maximum Power Transfer
- ⦿ Application: Sensors

Lesson Objectives

Demonstrate


- ◎ Series and parallel resistance
- ◎ Measure voltage and current using the voltage divider law and Ohm's Law

Review

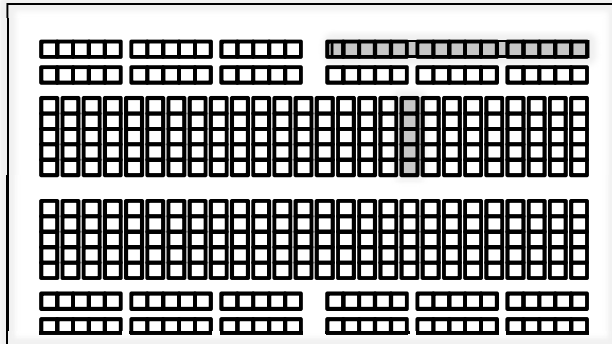


Protoboard

$$R = R_1 + R_2$$

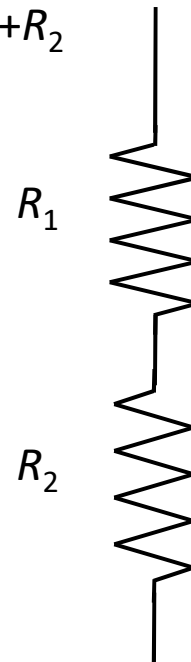

Resistors in Series

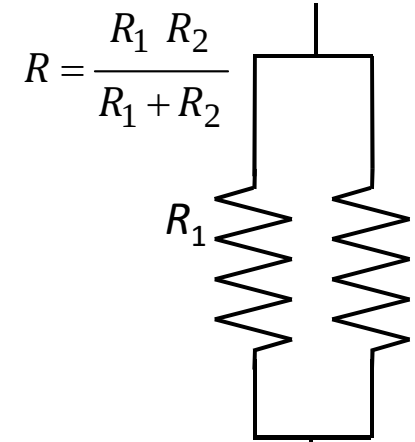

Resistors in Parallel

Lab Demo: Resistors and Connections

Summary

- ◎ Connect physical resistors in parallel and in series
- ◎ Measure voltages and currents in a circuit, applying the voltage divider law and Ohm's Law

Next Lesson

- ◎ Superposition to handle multiple sources

Credits

Thanks to Marion Crowder (School of Electrical and Computer Engineering at Georgia Tech) for video-taping the experiment

DMM used in experiment is manufactured by Fluke Corporation