

# Linear Circuits



**Nathan V. Parrish**

PhD Candidate & Graduate  
Research Assistant  
School of Electrical and  
Computer Engineering

*An introduction to linear electric circuit elements and a study of  
circuits containing such devices.*

School of Electrical and Computer Engineering



**Nathan V. Parrish**

PhD Candidate & Graduate  
Research Assistant  
School of Electrical and  
Computer Engineering

# Superposition



- *Use linearity (particularly superposition) to solve circuits*
- *Identify superposition as an important part of many analysis techniques*

## Previous Lesson

- ◎ Linear operators
  - Superposition
  - Homogeneity
- ◎ Combined linear operators to give new linear operators


## Module 2: Resistive Circuits

- ◎ Resistance and Ohm's Law
- ◎ Kirchhoff's Laws
- ◎ Resistors
- ◎ Superposition
- ◎ Obtaining Circuit Equations
- ◎ Maximum Power Transfer
- ◎ Wye-Delta and Wheatstone Bridge

## Lesson Objectives

- ◎ Given a complex system, generate a set of simple systems, each with a single independent source
- ◎ Using solution of simple systems, find the complete behavior of the system


# Isolating Independent Sources

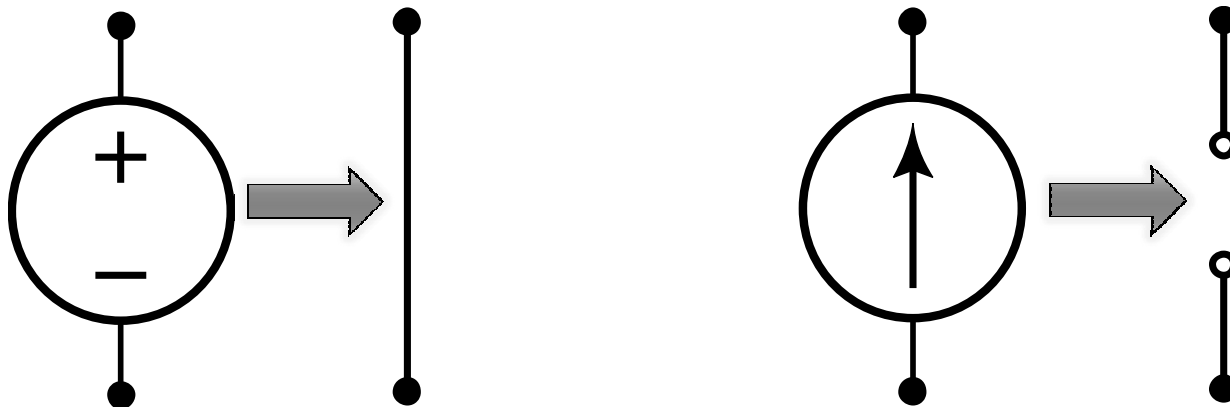

## Steps For Superposition


- ⦿ Zero-out all independent sources
- ⦿ Return sources one at a time and solve for value of interest in simplified system
- ⦿ Take the arithmetic sum of these values to find the final quantity

## Example 1

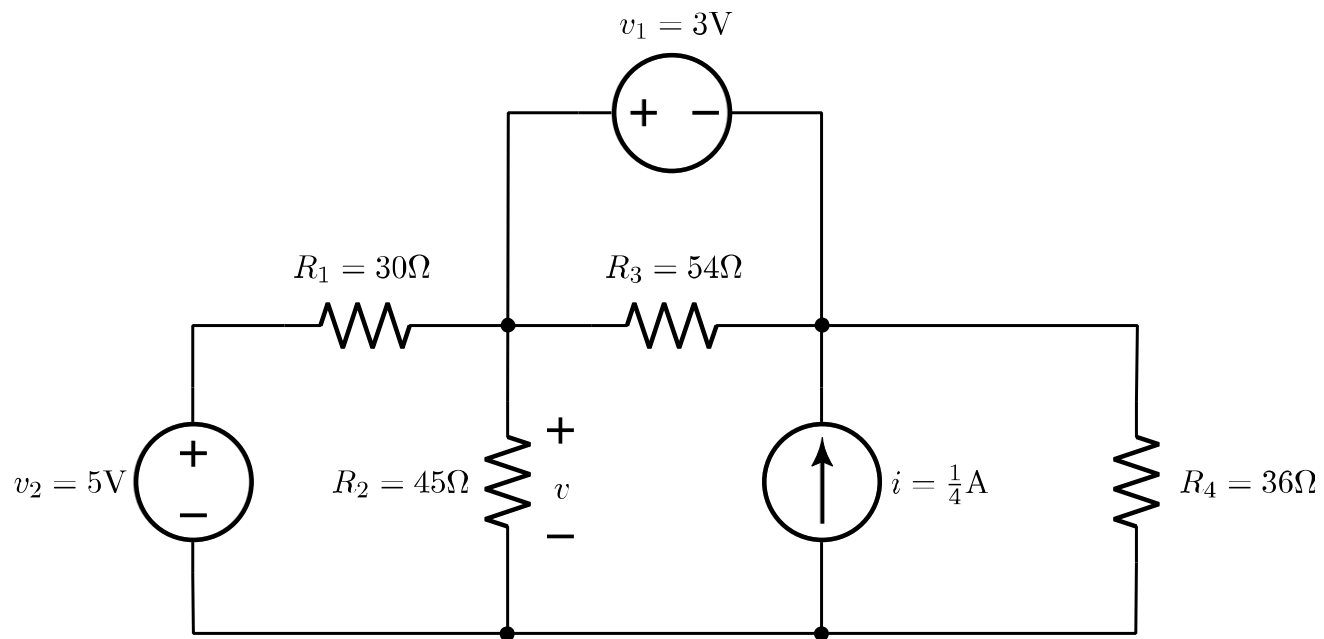




## Example 1 (a)

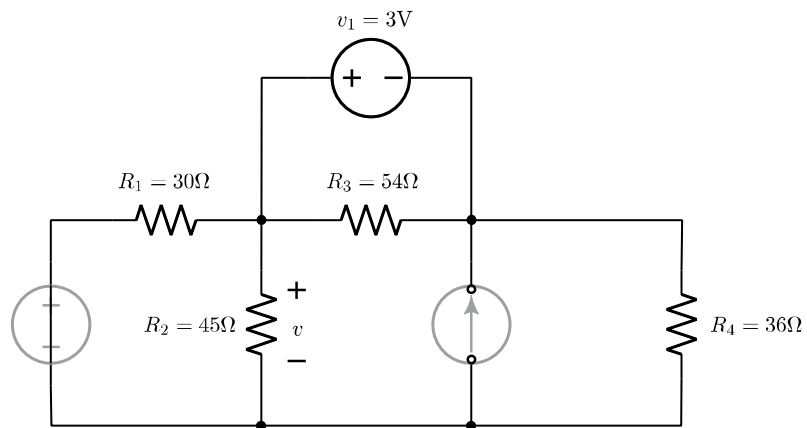

## Example 1 (b)


$$V_{(a)} = 1V$$

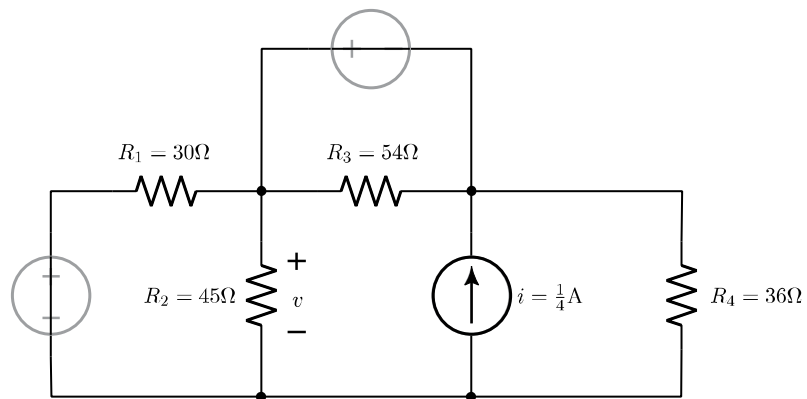

## Example 1 (c)



$$V(a) = 1V$$

$$V(b) = 3V$$

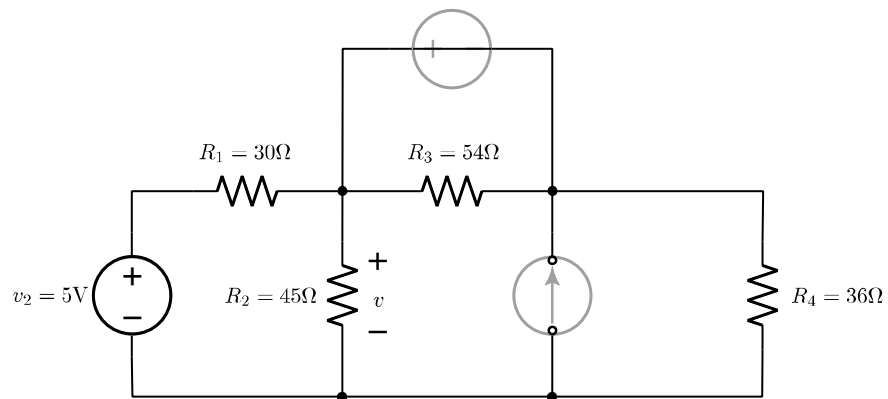

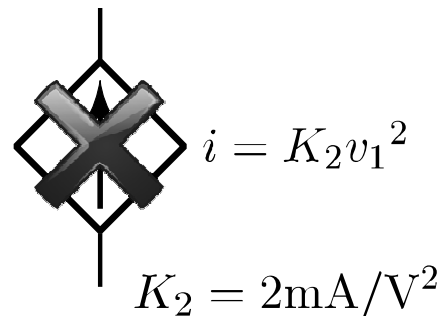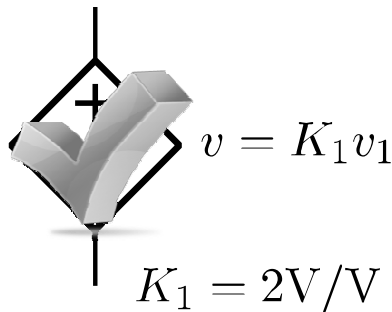
## Working with Dependent Sources


- Dependent sources must be analyzed in each solution
- Must be a linear operator




## Example 2

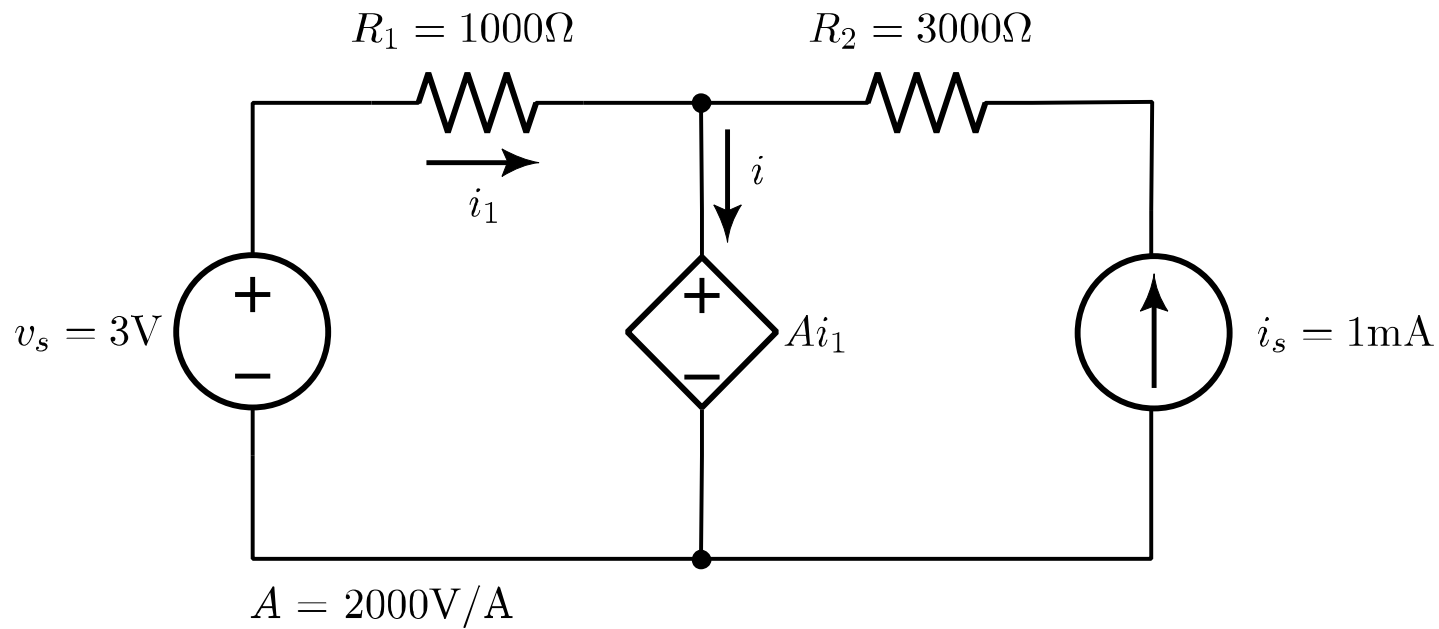

## Example 2 (a)

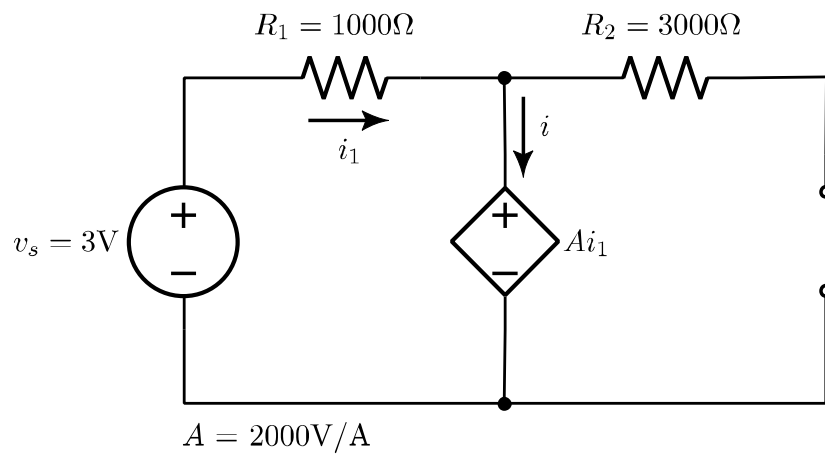

## Example 2 (b)

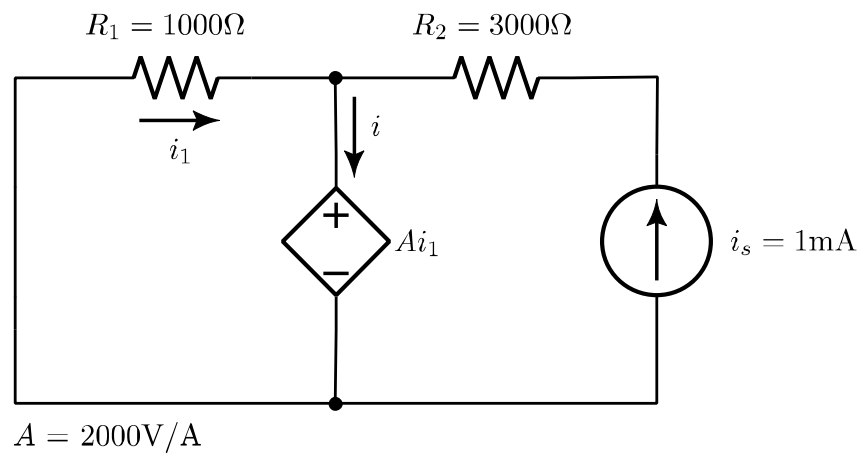

# Summary

- ◎ Used superposition to solve circuits
  - Independent sources only
  - With dependent sources



## Next Lesson

- ◎ Systematic application of Ohm's Law, KCL, and KVL to generate a system of equations
- ◎ Thévenin and Norton equivalent circuits