

# Linear Circuits



**Dr. Bonnie Ferri**  
Professor and Associate Chair  
School of Electrical and  
Computer Engineering



*An introduction to linear electric circuit elements and a study of circuits containing such devices.*

School of Electrical and Computer Engineering



**Dr. Bonnie Ferri**  
Professor and Associate Chair  
School of Electrical and  
Computer Engineering

# Systematic Solution Methods: Part 2



*Introduce several ways of obtaining circuit equations.*

## Module 2: Resistive Circuits

- ⦿ Resistance
- ⦿ Kirchhoff's Laws
- ⦿ Resistors
- ⦿ Superposition
- ⦿ Systematic Solution Methods
- ⦿ Maximum Power Transfer
- ⦿ Application: Sensors



# Lesson Objective

- ◎ Demonstrate
  - Thévenin equivalent and Norton equivalent circuits
  - Source transformations

# Systematic solution Methods

Method	Summary	When to Apply
Mesh Analysis	KVL to obtain simultaneous equations for currents	<ul style="list-style-type: none"><li>• Multiple currents are needed</li><li>• Current sources are present</li></ul>
Node Analysis	KCL to obtain simultaneous equations for voltages	<ul style="list-style-type: none"><li>• Multiple voltages are needed</li><li>• Voltage sources are present</li></ul>
Thévenin and Norton Equivalent Circuits	Simple equivalent circuits, source transformations	<ul style="list-style-type: none"><li>• Intermediate values not important; only output voltage or current</li></ul>

# Thévenin Equivalent

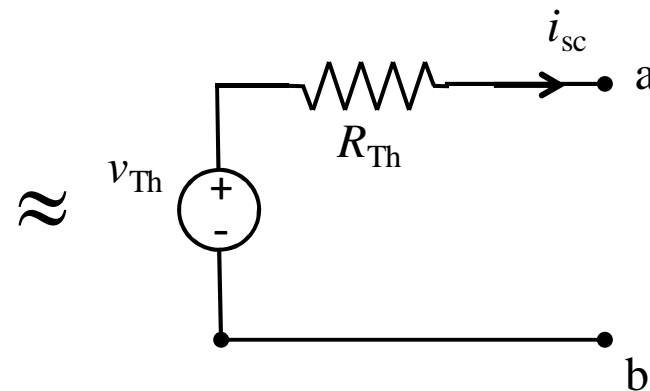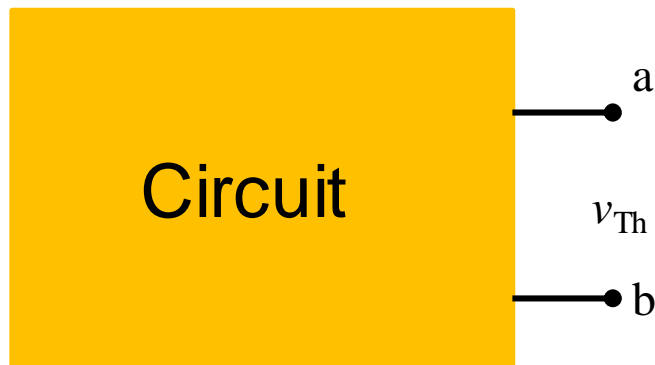


Replace circuit with equivalent  
resistance and voltage source

# Thévenin Equivalent Circuit


- ⊙  $V_{Th}$ : open circuit across a-b and find  $v_{ab} = V_{Th}$
- ⊙  $i_{sc}$ : short circuit across a-b and find  $i_{sc}$

$$V_{Th} = R_{Th} i_{sc}$$

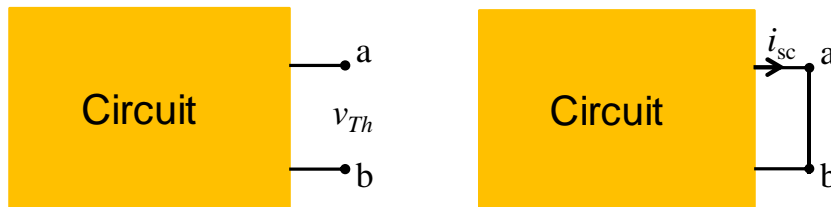


- ⊙  $R_{Th}$ : circuit resistance with voltage sources shorted and current sources open circuited (when no dependent sources are present)

# Thévenin Equivalent Example

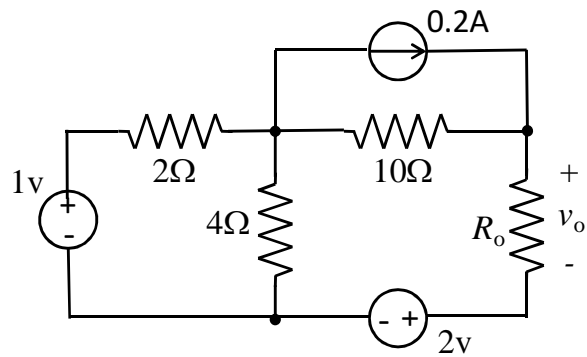




# Norton Equivalent Circuit

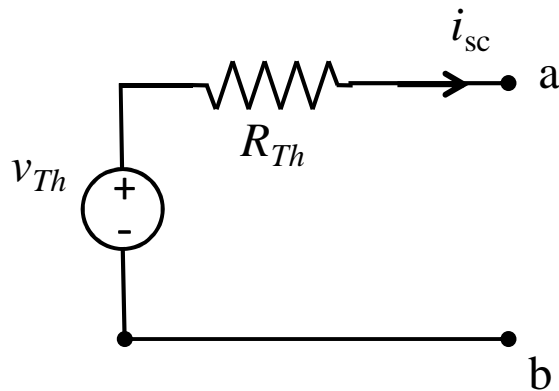

Thévenin equivalent circuit


$\approx$

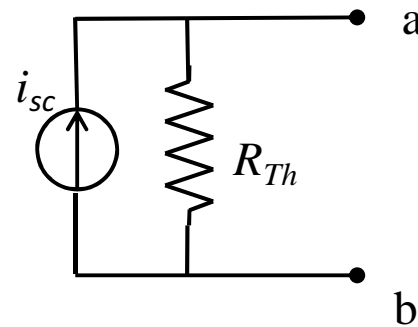

Norton equivalent circuit

**Source Transformation:** these configurations are interchangeable in a circuit

# Source Transformation Example

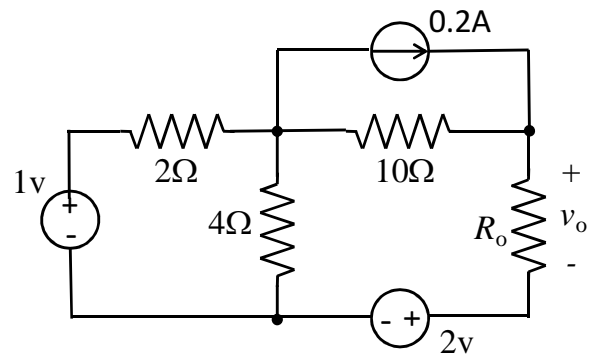

# Summary

- ◎ Mesh and node analysis
  - Systematic ways to find independent simultaneous equations
- ◎ Thévenin and Norton methods
  - Replace most of the circuit with a simple equivalent circuit
  - Source transformations
- ◎ Extra worked problems are given on these methods

## Next Lesson

- ◎ Maximum Power Transfer
  - Uses Thévenin equivalent circuit to find the load to maximize power delivered