

Linear Circuits



Nathan V. Parrish

PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

*An introduction to linear electric circuit elements and a study of
circuits containing such devices.*

School of Electrical and Computer Engineering



Nathan V. Parrish
PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

Maximum Power Transfer

An introduction to linear electric circuit elements and a study of circuits containing such devices.

School of Electrical and Computer Engineering

Previous Lesson

- ◎ Obtaining Circuit Equations
 - Node-voltage
 - Mesh-current
 - Thévenin equivalent
 - Norton equivalent


Module 2: Resistive Circuits

- ⦿ Resistance
- ⦿ Kirchhoff's Laws
- ⦿ Resistors
- ⦿ Superposition
- ⦿ Systematic Solution Methods
- ⦿ Maximum Power Transfer
- ⦿ Wye-Delta and Wheatstone Bridge
- ⦿ Application: Sensors


Lesson Objectives

- ◎ Find the load resistance that gives maximum power transfer to the load
- ◎ Calculate this power consumed by the load resistor giving maximum power transfer

Two-Terminal Linear Circuits

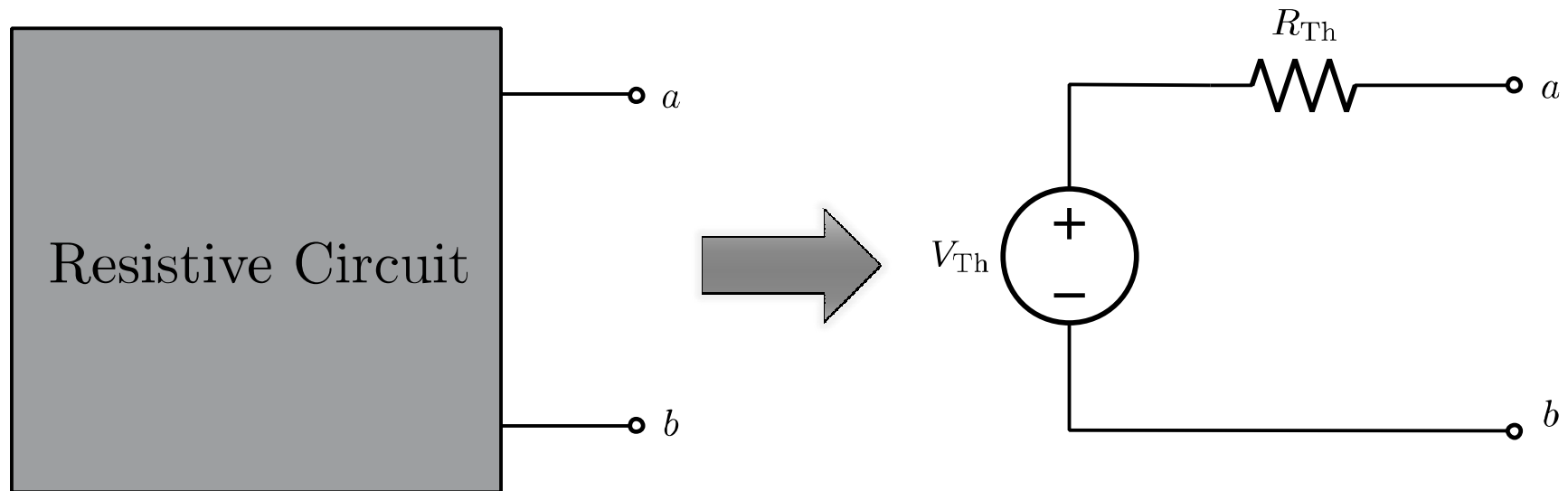

Power Equations for Resistors

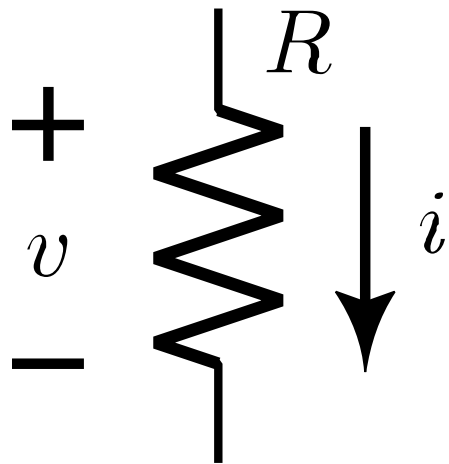


$$p = iv$$


$$v = iR$$

$$p = i^2 R = \frac{v^2}{R}$$

Load Resistance

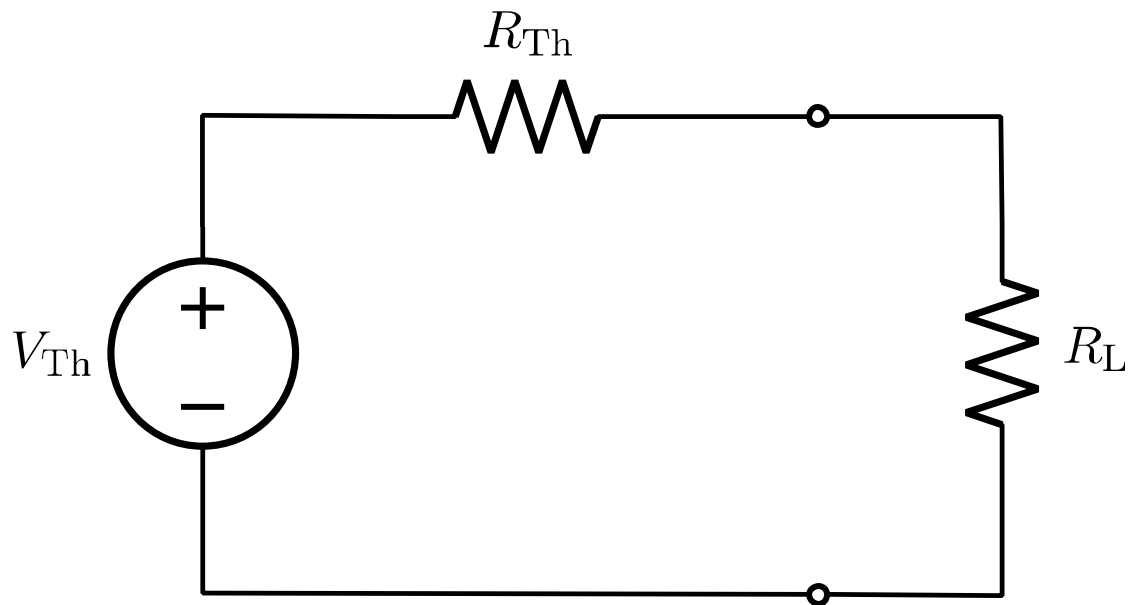

Maximum Power Transfer

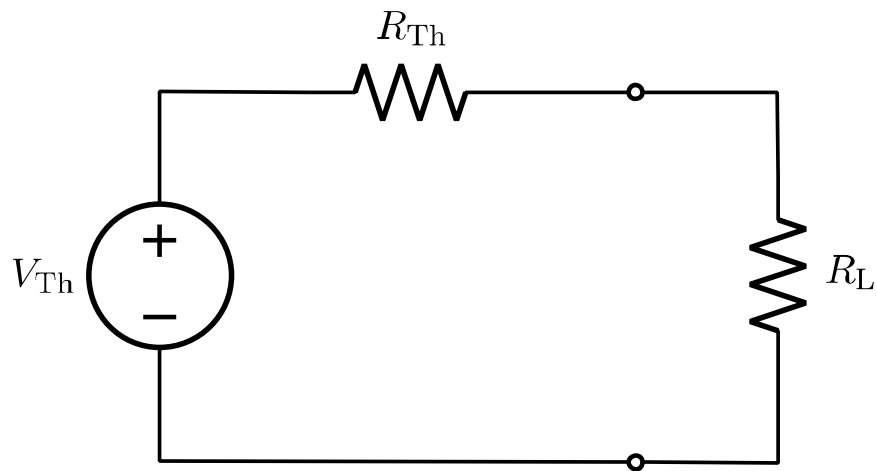

$$p = i^2 R$$

$$p = \frac{V_{Th}^2}{(R_{Th} + R_L)^2} R_L$$

$$p = \frac{V_{Th}^2}{4R_{Th}} \text{ for } R_L = R_{Th}$$

Summary

- ⦿ Specified power equations for resistors
- ⦿ Matched load resistance to system resistance for maximum power transfer
- ⦿ Specified equation for maximum power transfer

Next Lesson

- ◎ Wye-Delta Transformations
- ◎ Wheatstone Bridge