

# Linear Circuits



**Nathan V. Parrish**

PhD Candidate & Graduate  
Research Assistant  
School of Electrical and  
Computer Engineering

*An introduction to linear electric circuit elements and a study of  
circuits containing such devices.*

**School of Electrical and Computer Engineering**



**Nathan V. Parrish**  
PhD Candidate & Graduate  
Research Assistant  
School of Electrical and  
Computer Engineering

# Wye-Delta Transforms and the Wheatstone Bridge

- *Transform resistors from a wye configuration to a delta configuration and vice-versa*
- *How to use a wheatstone bridge to measure a resistance*



## Previous Lesson

- ◎ Obtaining Circuit Equations
- ◎ Maximum Power Transfer


## Module 2: Resistive Circuits

- ⦿ Resistance
- ⦿ Kirchhoff's Laws
- ⦿ Resistors
- ⦿ Superposition
- ⦿ Systematic Solution Methods
- ⦿ Maximum Power Transfer
- ⦿ Wye-Delta and Wheatstone Bridge
- ⦿ Application: Sensors

# Learning Objectives

- ◎ Transform resistor circuits between wye and delta configurations
- ◎ Specify a test resistor which balances a Wheatstone bridge
- ◎ Identify whether the resistor under test in a Wheatstone bridge is below or above the target resistance

# Wye-Delta Transformation

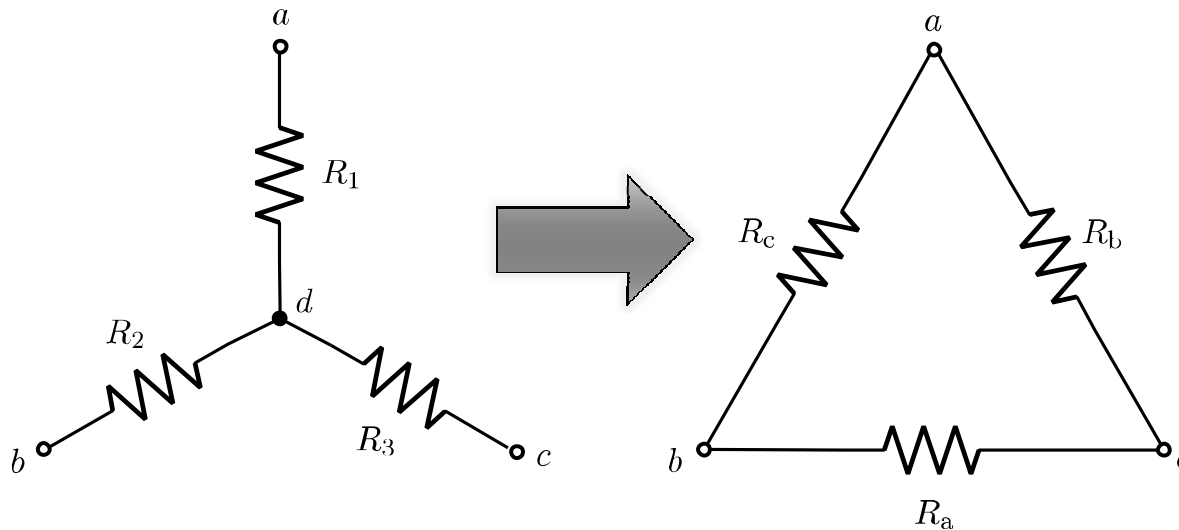


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

# Summary

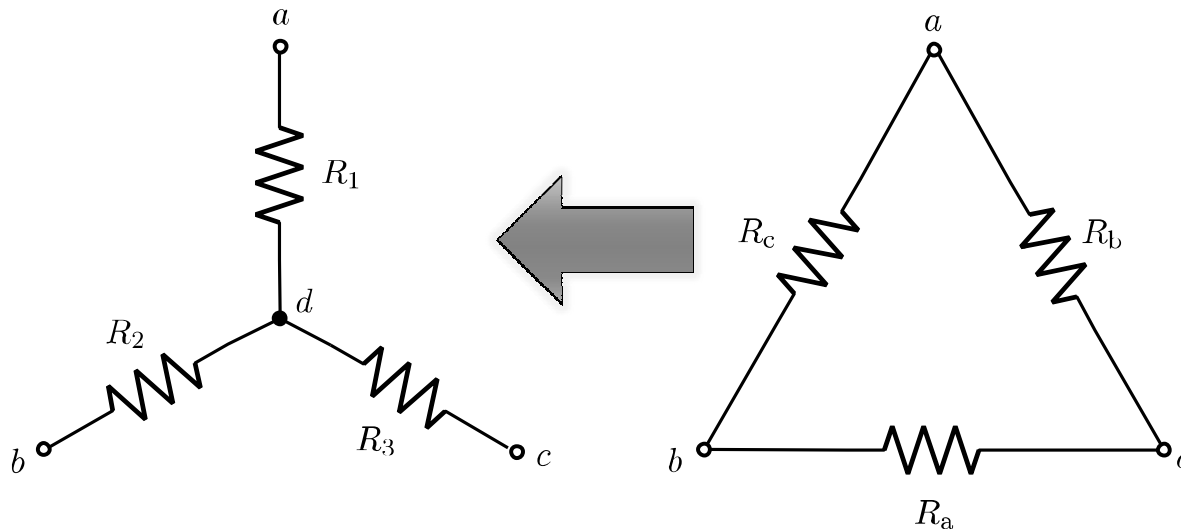


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$


$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

# Example

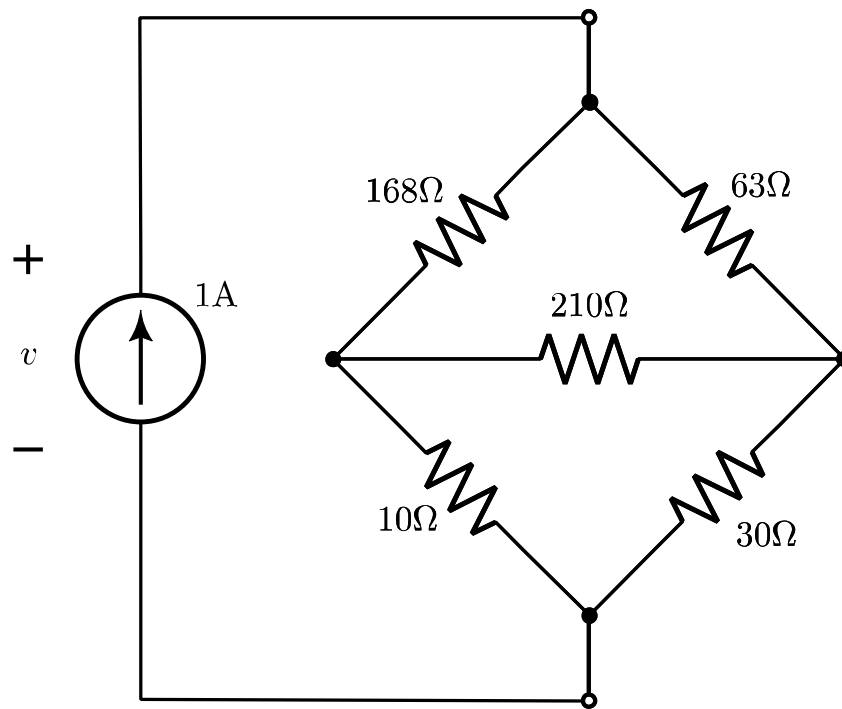



# Wheatstone Bridge

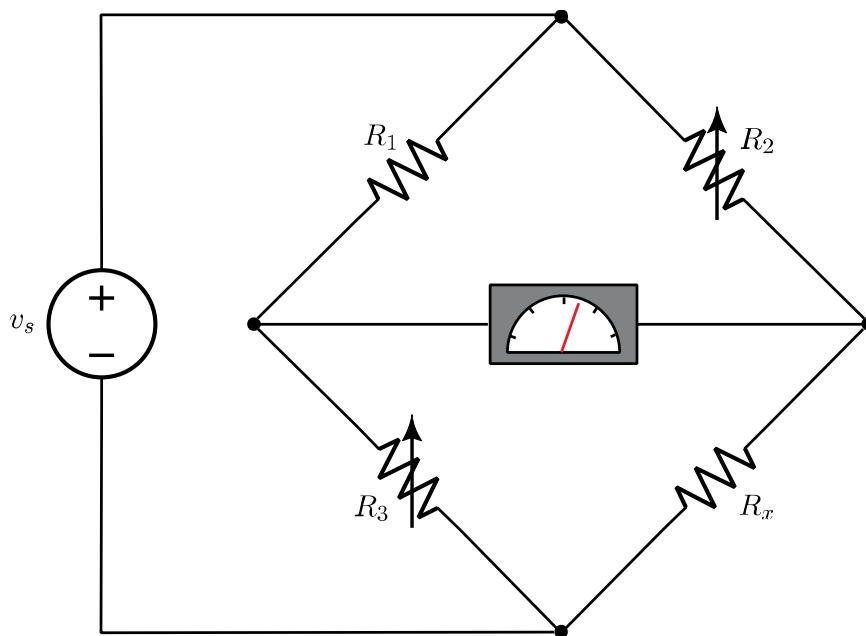

$$\frac{R_1}{R_2} = \frac{R_3}{R_x}$$

## Summary

- ⦿ Used Y- $\Delta$  transform to simplify circuits
- ⦿ Balanced a Wheatstone bridge
- ⦿ Identified whether the resistor under test was above or below balanced resistance based on current across the bridge

## Next Lesson

- ◎ Applications of resistors in sensors
- ◎ Experiment using Wheatstone bridge