

# Linear Circuits



**Dr. Bonnie Ferri**  
Professor and Associate Chair  
School of Electrical and  
Computer Engineering

*An introduction to linear electric circuit elements and a study of circuits containing such devices.*

School of Electrical and Computer Engineering



**Dr. Bonnie Ferri**  
Professor and Associate Chair  
School of Electrical and  
Computer Engineering

# Application: Wheatstone Bridge


*An Wheatstone Bridge used in a sensor.*



## Module 2: Resistive Circuits

- ⦿ Resistance
- ⦿ Kirchhoff's Laws
- ⦿ Resistors
- ⦿ Superposition
- ⦿ Systematic Solution Methods
- ⦿ Maximum Power Transfer
- ⦿ Applications: Sensors

# Wheatstone Bridge

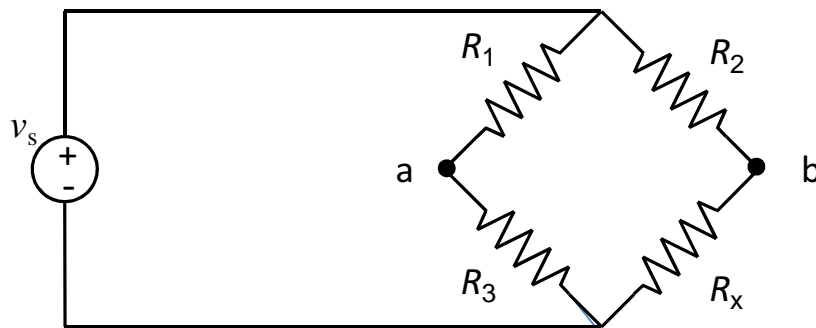

Balance  $R_2$  and  $R_3$  so  $v_a = v_b$  and apply the voltage divider law

$$\frac{R_3}{R_1 + R_3} v_s = \frac{R_x}{R_2 + R_x} v_s$$

Cancel the  $v_s$ . Similarly

$$\frac{R_1}{R_1 + R_3} = \frac{R_2}{R_2 + R_x}$$

Divide both sides of these last equations to get

$$\frac{R_3}{R_1} = \frac{R_x}{R_2}$$

Measure  $v_a - v_b$

# Lab Demo: Wheatstone Bridge

# Summary

- ⦿ Wheatstone bridge is used to detect small changes in resistance
- ⦿ Four strain gauges in a Wheatstone configuration removes thermal effect

# Credits

Thanks to Sterling Skinner for building the flexible beam experimental platform and Dr. Aldo Ferri for expertise on that system (both of the George W. Woodruff School of Mechanical Engineering at Georgia Tech).

Thanks to Marion Crowder (School of Electrical and Computer Engineering at Georgia Tech) for video-taping the experiment

DMM used in experiment is manufactured by Fluke Corporation