



**Nathan V. Parrish**  
PhD Candidate & Graduate  
Research Assistant  
School of Electrical and  
Computer Engineering

# Circuits & Electronics

*An introduction to electric circuit elements and electronic devices, and a study of circuits containing such devices. Both analog and digital systems are considered.*

# RC Circuits



**Nathan V. Parrish**  
PhD Candidate & Graduate  
Research Assistant  
School of Electrical and  
Computer Engineering

- *Generate a differential equation that describes the behavior of a circuit with resistors and capacitors*
- *Solve the differential equation for step inputs (or switching constant inputs)*
- *Graph the behavior*

## Previous Lesson

- ◎ Solving some simple first-order differential equations


## Module 3: Reactive Circuits

- ⊙ Capacitors
- ⊙ Inductors
- ⊙ First-order differential equations
- ⊙ RC Circuits
- ⊙ RL Circuits
- ⊙ Second-order differential equations
- ⊙ RLC Circuits


## Lesson Objectives

- ◎ Generate a differential equation from a circuit
- ◎ Identify initial and final conditions
- ◎ Solve the differential equation
- ◎ Graph the result


# Behavior of RC circuits

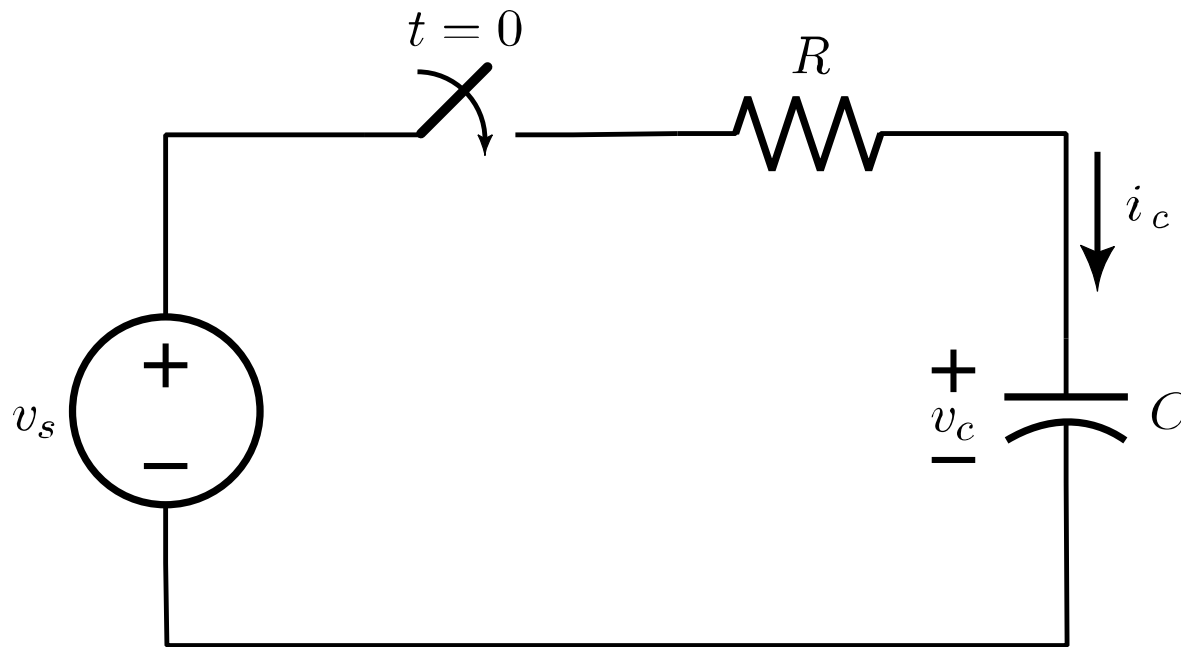
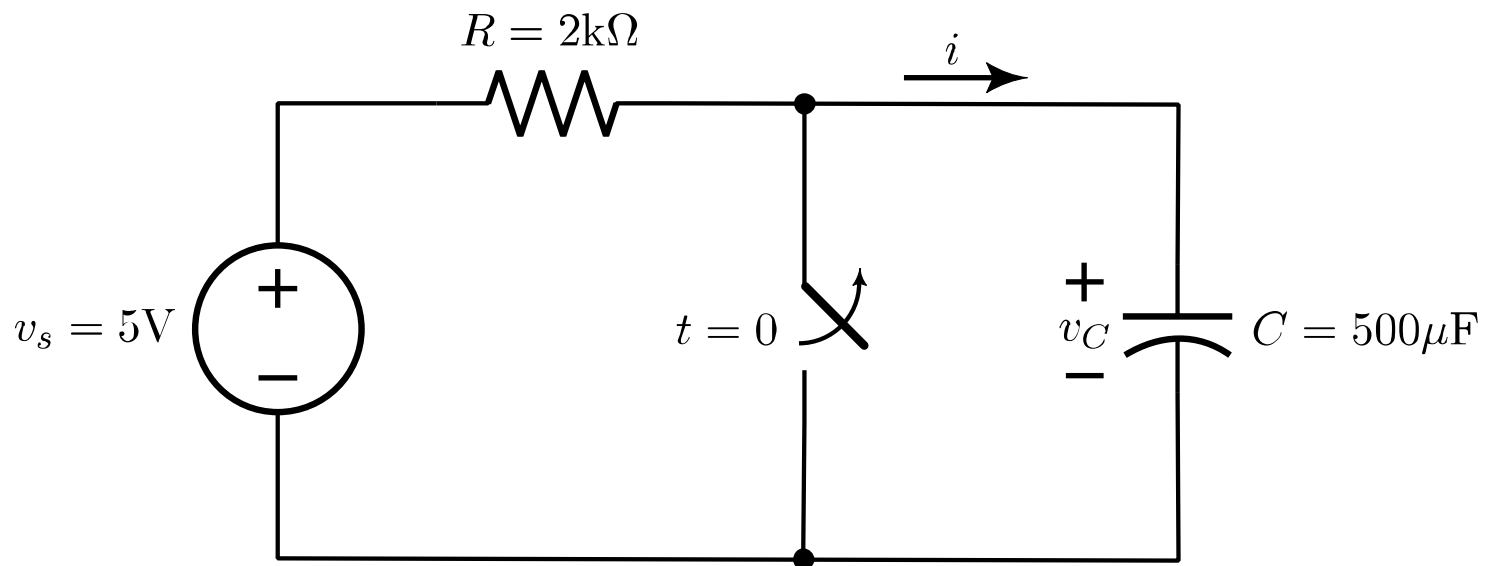
## Example 1: Initial and Final Conditions



## Example 1: Differential Equation

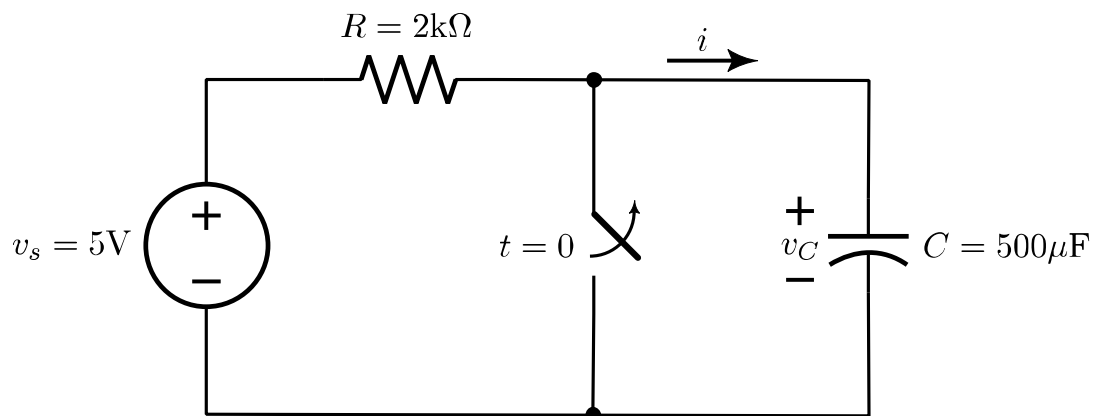

$$\frac{dy}{dt} + ay = K \quad y(0)$$


---


$$y(t) = \frac{K}{a}(1 - e^{-at}) + y(0)e^{-at}, \quad t \geq 0$$

$$v_C = v_s \left[ 1 - e^{-\frac{t}{\tau}} \right]$$

$$i = C \frac{dv_C}{dt} \quad i = \frac{v_s - v_C}{R}$$


$$\frac{v_s - v_C}{R} = C \frac{dv_C}{dt}$$

$$\frac{dv_C}{dt} + \frac{1}{RC} v_C = \frac{v_s}{RC}$$


$$\text{Let } \tau = RC$$




## Example 1: Graph

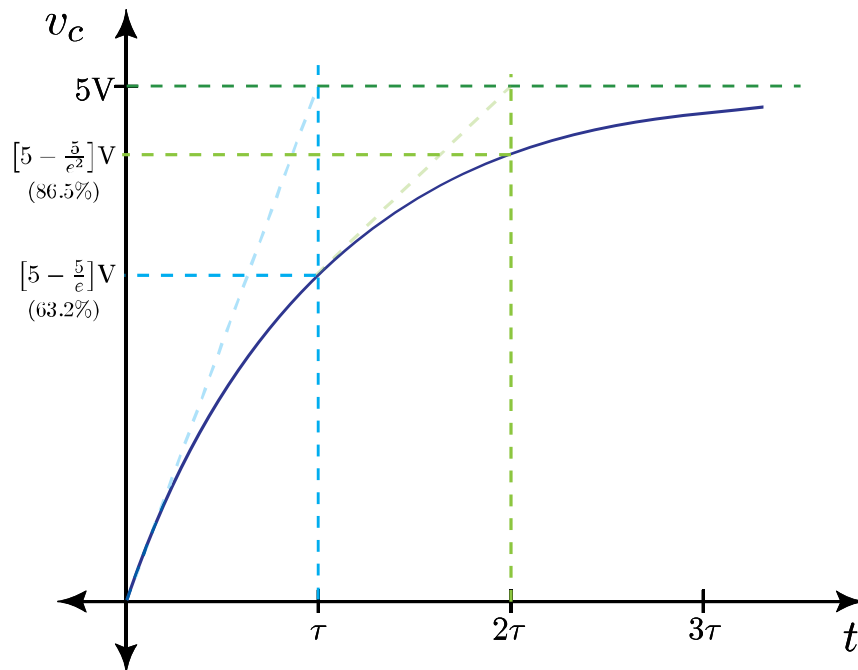

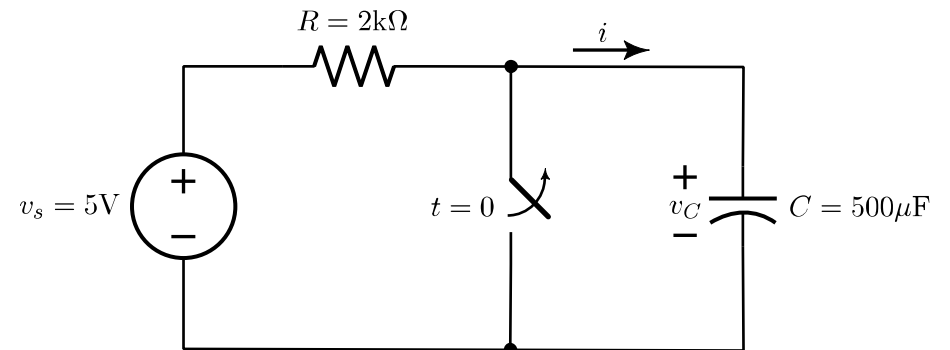
$$v_C = v_s \left[ 1 - e^{-\frac{t}{\tau}} \right]$$


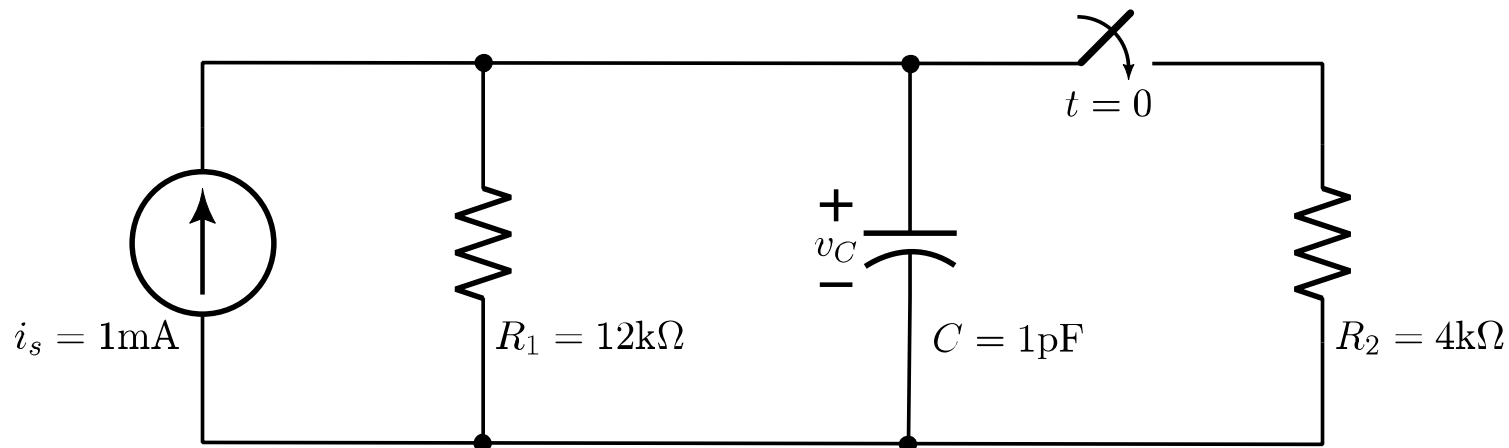
## Example 2: Initial and Final Conditions



## Example 2: Differential Equation

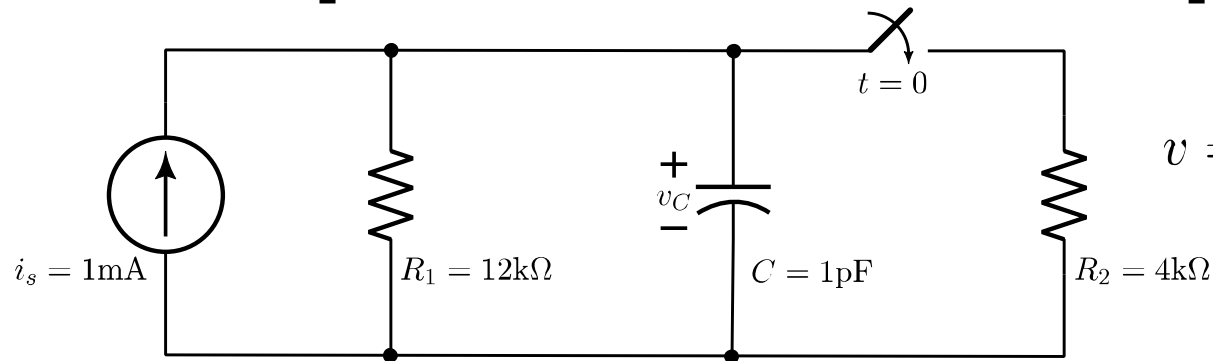

$$v = i_s R_{\text{eq}} (1 + e^{\frac{-t}{\tau}}) + i_s R_1 e^{\frac{-t}{\tau}}$$

$$i_s = i_{R_1} + i_C + i_{R_2}$$

$$i_C = C \frac{dv}{dt}$$

$$i_{R_1} = \frac{v}{R_1}$$

$$i_{R_2} = \frac{v}{R_2}$$


$$i_s = \left( \frac{1}{R_1} + \frac{1}{R_2} \right) v + C \frac{dv}{dt}$$

$$\text{Let } R_{\text{eq}} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$


$$\frac{i_s}{C} = \frac{dv}{dt} + \frac{1}{R_{\text{eq}} C} v$$

$$\text{Let } \tau = R_{\text{eq}} C$$

## Example 2: Graph

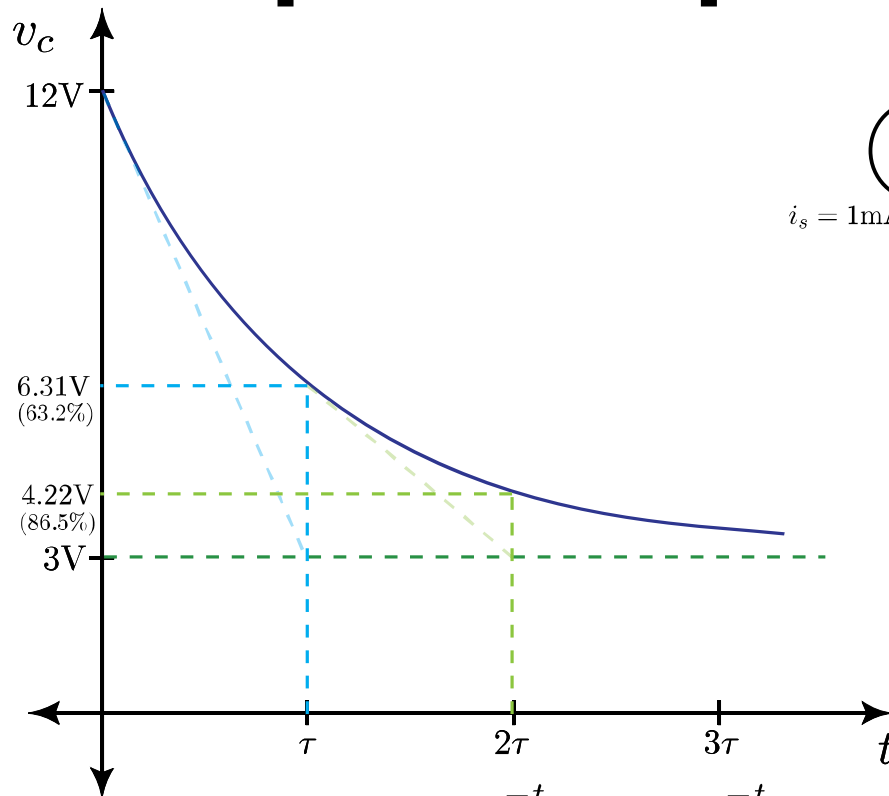
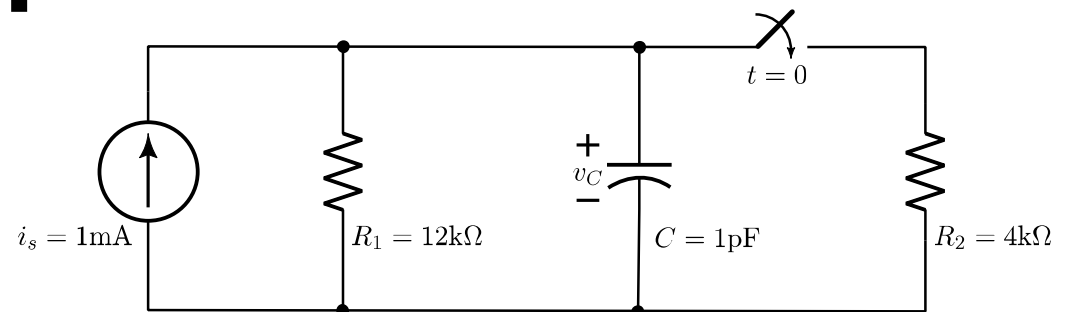
$$v = 3\left(1 + e^{\frac{-t}{\tau}}\right) + 12e^{\frac{-t}{\tau}}$$



## Summary

- ◎ Got some intuition about how RC circuits behave
- ◎ Identified initial and final conditions
- ◎ Found differential equations for the circuit and solved them
- ◎ Graphed the results

## Next Lesson

- ◎ Differential equations applied to systems with resistors and inductors