

# Linear Circuits



**Nathan V. Parrish**  
PhD Candidate & Graduate  
Research Assistant  
School of Electrical and  
Computer Engineering

*An introduction to linear electric circuit elements and a study of circuits containing such devices.*





**Nathan V. Parrish**  
PhD Candidate & Graduate  
Research Assistant  
School of Electrical and  
Computer Engineering

# RLC Circuits Part 1

- *Use differential equations to show the behavior of an RLC circuit as the system changes.*



## Previous Lesson

- © Learned about solving second-order differential equations


## Module 3: Reactive Circuits

- ⊙ Capacitors
- ⊙ Inductors
- ⊙ First-order differential equations
- ⊙ RC Circuits
- ⊙ RL Circuits
- ⊙ Second-order differential equations
- ⊙ RLC Circuits


## Lesson Objectives

- ◎ Generate a second-order differential equation from a RLC circuit
- ◎ Identify initial and final conditions
- ◎ Solve the differential equation
- ◎ Recognize if a system is underdamped/overdamped
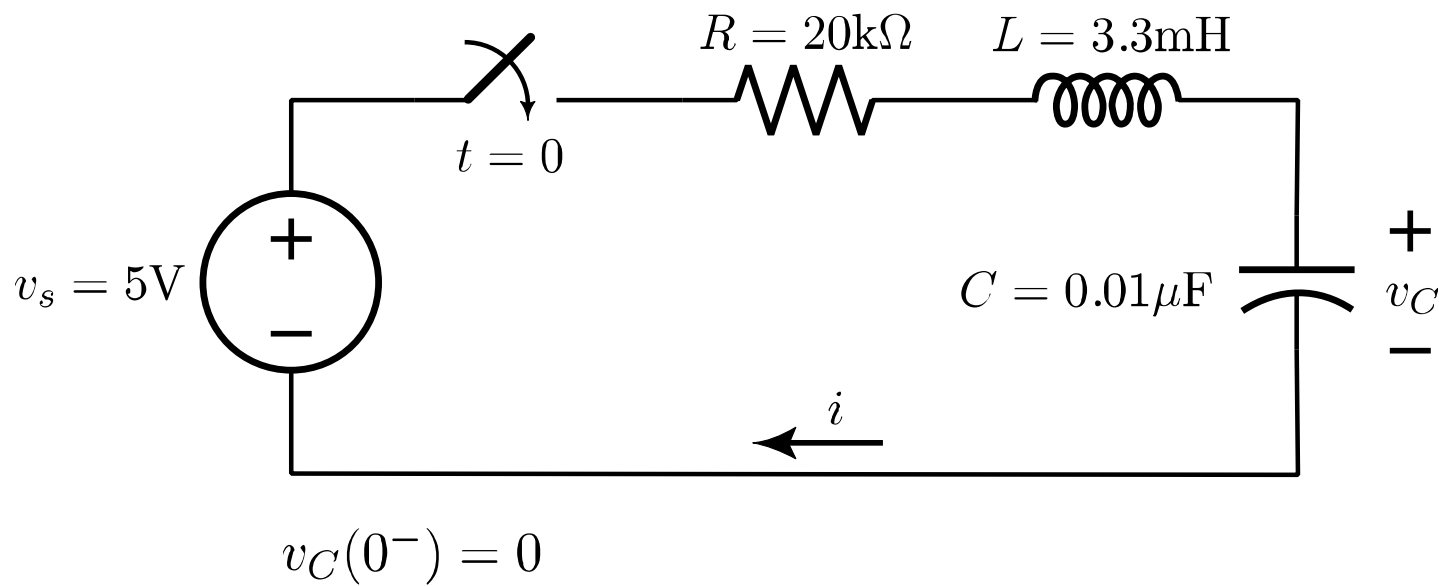
## Example 1: Initial and Final Conditions



## Example 1: Differential Equation

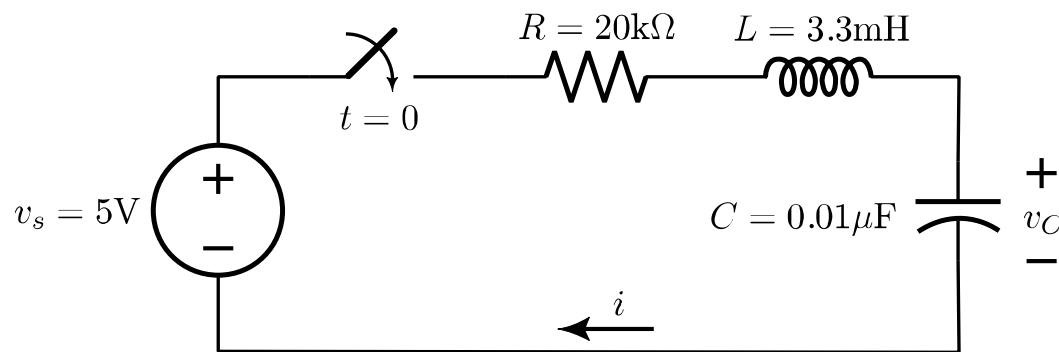

$$LC \frac{d^2 v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C = v_s$$

$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = \frac{v_s}{LC}$$

$$\frac{d^2 y}{dt^2} + a_1 \frac{dy}{dt} + a_2 y = K$$

$$v_s = v_R + v_L + v_C$$

$$v_R = iR \quad v_L = L \frac{di}{dt} \quad i = C \frac{dv_C}{dt}$$

## Example 1: Transient

$$\frac{d^2 v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c = \frac{v_s}{LC}$$

$$\frac{d^2 v_c}{dt^2} + 6.06e6 \frac{dv_c}{dt} + 30.3e9 v_c = 151.5e9$$

Characteristic Equation:

$$s^2 + 6.06e6 s + 30.3e9 = 0$$

Roots:       $-5.00e3$        $-6.06e6$

$$v_{c,t} = K_1 e^{-5.00e3 t} + K_2 e^{-6.06e6 t}$$




## Example 1: Steady State

$$\frac{d^2 v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c = \frac{v_s}{LC}$$

$$v_c \rightarrow \frac{K}{a_2} = LC \frac{v_s}{LC} = v_s$$


$$v_{c,s} = 5$$

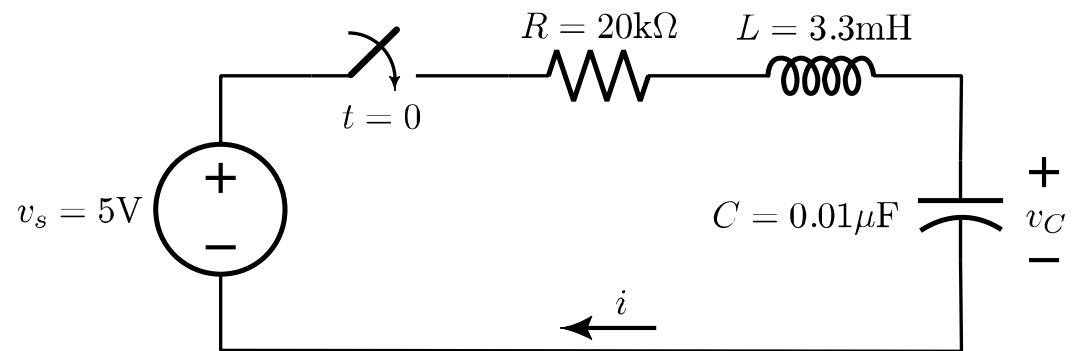
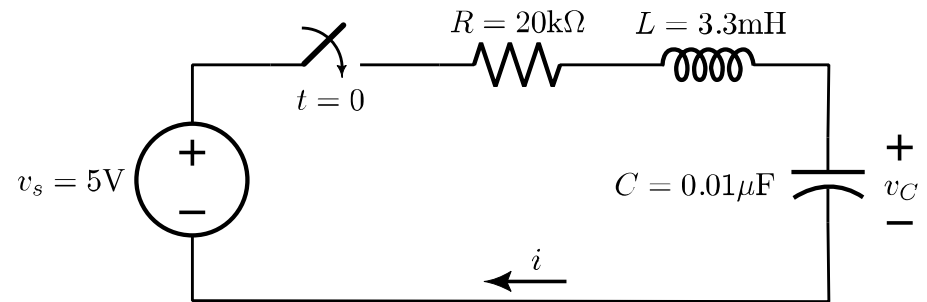
## Example 1: Solving for Constants

$$v_C = v_{C,t} + v_{C,s}$$



$$v_C = K_1 e^{-5.00e3t} + K_2 e^{-6.06e6t} + 5$$



$v_C(0^-) = v_C(0) = 0$	$i(0^-) = i(0) = 0$
$K_1 + K_2 + 5 = 0$	$i = C \frac{dv_C}{dt}$
	$-50e(-6)K_1 - 60.6e(-3)K_2 = 0$

$$K_1 = -5.00413 \quad K_2 = 0.00413$$

## Example 1: Final Solution

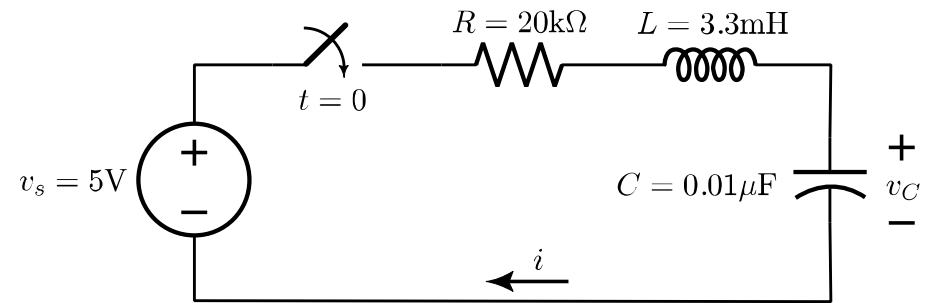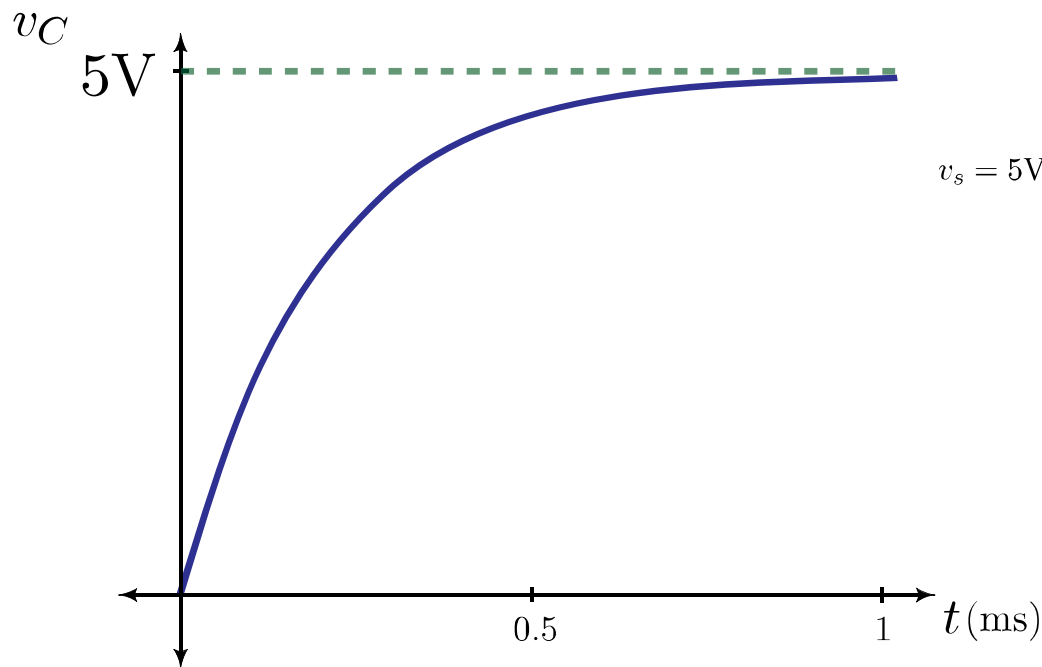

$$v_C = -5.00413e^{-5.00e3t} + 0.00413e^{-6.06e6t} + 5$$

# Summary

- ⦿ Looked at an overdamped case
- ⦿ Identified initial and final conditions
- ⦿ Found and solved representative differential equation
- ⦿ Plotted the results

## Next Lesson

- ◎ Consider an underdamped example