

Linear Circuits



Nathan V. Parrish

PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering



An introduction to linear electric circuit elements and a study of circuits containing such devices.

School of Electrical and Computer Engineering



Nathan V. Parrish
PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

Impedance



Identify impedances – a mathematical tool to analyze reactive circuits with sinusoidal inputs.

Previous Lesson

© Sinusoids and phasors


Module 4: Frequency Analysis

- ⦿ Sinusoids and phasors
 - ⦿ Impedance
 - ⦿ Circuit analysis in AC
 - ⦿ Transfer functions
 - ⦿ Frequency response
 - ⦿ High/low-pass filters
 - ⦿ Bandpass/notch filters
- 

Lesson Objectives

- ◎ Be able to describe impedance
- ◎ Calculate impedances of resistors, capacitors, and inductors
- ◎ Identify the relationship between voltage and current based on and impedance value

Definition of Impedance

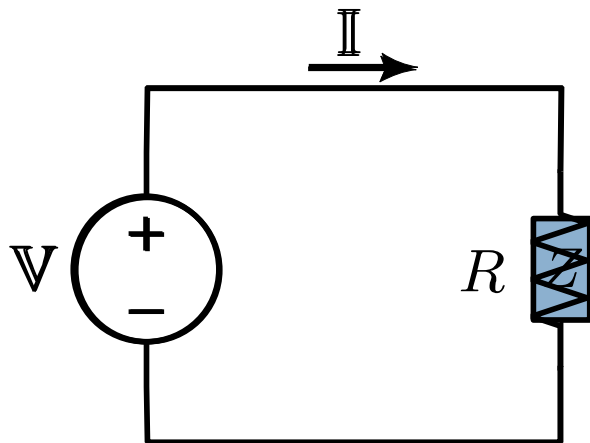


$$V = IZ$$

$$Z_R = R$$

$$v(t) = V_m \cos(\omega t + \theta) \Leftrightarrow V_m \angle \theta$$

$$i(t) = \frac{V_m}{R} \cos(\omega t + \theta) \Leftrightarrow \frac{V_m}{R} \angle \theta$$

Impedance of an Inductor

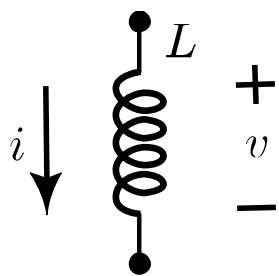

$$v_L = L \frac{di_L}{dt}$$

$$\mathbb{V} = \mathbb{I}Z$$

$$i = I_m \cos(\omega t + \theta) \Leftrightarrow \mathbb{I} = I_m \angle \theta$$


$$v = LI_m\omega \cos\left(\omega t + \theta + \frac{\pi}{2}\right) \Leftrightarrow \mathbb{V} = LI_m\omega \angle \theta + \frac{\pi}{2}$$

$$Z = \frac{\mathbb{V}}{\mathbb{I}} = \frac{LI_m\omega \angle \theta + \frac{\pi}{2}}{I_m \angle \theta} = L\omega \angle \frac{\pi}{2} = j\omega L$$


$$Z_L = j\omega L$$

- Inductor impedance purely imaginary
- Scales based on frequency
- Positive imaginary, so current **lags** voltage

Impedances

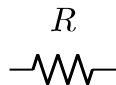

$$Z_R = R$$

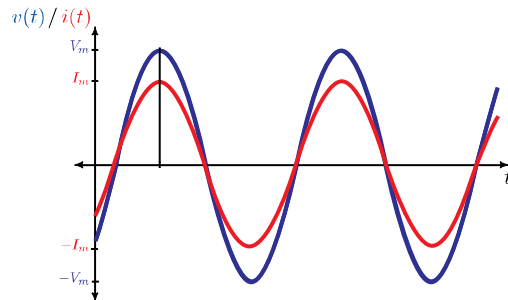


In-phase

Frequency invariant




$$Z_C = \frac{1}{j\omega C}$$

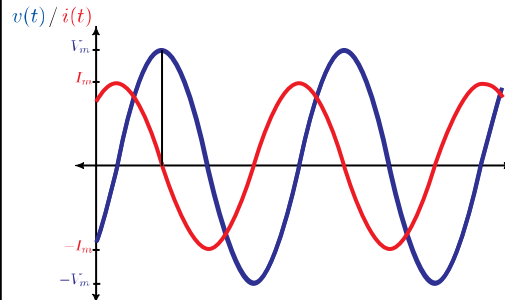


Current leads voltage

Voltage attenuates for high frequency

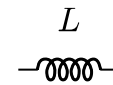

$$Z_L = j\omega L$$

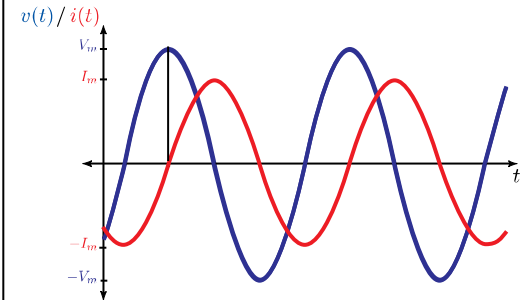

Current lags voltage

Current attenuates for high frequency

Summary

- ◎ Defined impedance and calculated impedance of linear devices
- ◎ Described the relationship between the current and the voltage given impedance

Next Lesson

- ◎ Using impedances, apply analysis techniques to AC systems