

# Linear Circuits



**Nathan V. Parrish**

PhD Candidate & Graduate  
Research Assistant  
School of Electrical and  
Computer Engineering



*An introduction to linear electric circuit elements and a study of circuits containing such devices.*

School of Electrical and Computer Engineering

# AC Circuit Analysis



**Nathan V. Parrish**  
PhD Candidate & Graduate  
Research Assistant  
School of Electrical and  
Computer Engineering



*Identify how past techniques apply to impedances in AC circuit analysis.*

## Previous Lesson

- ◎ Impedance and its relationship to phasors
- ◎ Impedance in reactive circuits changes with frequency


## Module 4: Frequency Analysis

- ⦿ Sinusoids and phasors
- ⦿ Impedance
- ⦿ Analysis of sinusoidal systems
- ⦿ Transfer functions
- ⦿ Frequency response
- ⦿ Low-pass and high-pass filters
- ⦿ Bandpass and notch filters

# Lesson Objectives


- ⦿ Apply techniques from DC analysis to sinusoidal systems
- ⦿ Find equivalent impedances for devices in series/parallel
- ⦿ Use superposition for analysis: particularly for systems with multiple frequencies
- ⦿ Be able to analyze a system using these techniques

# Impedance is Linear

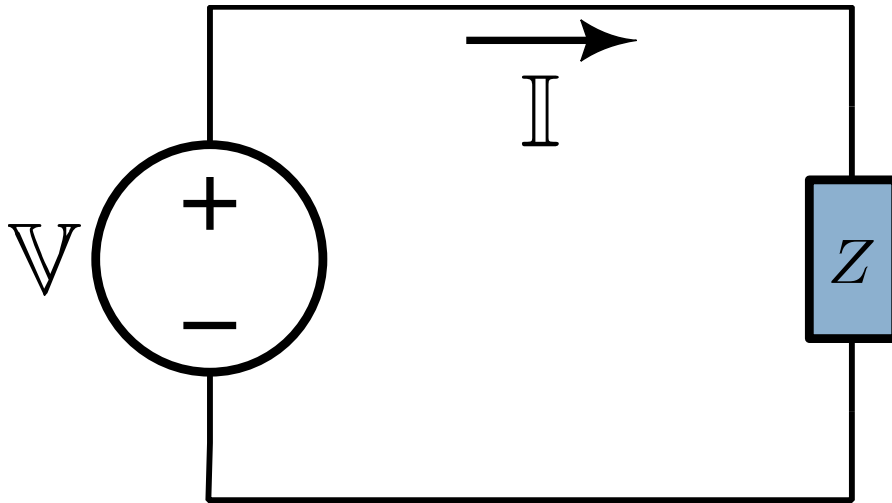


$$V = IZ \sim V = IR$$

# Impedances in Series

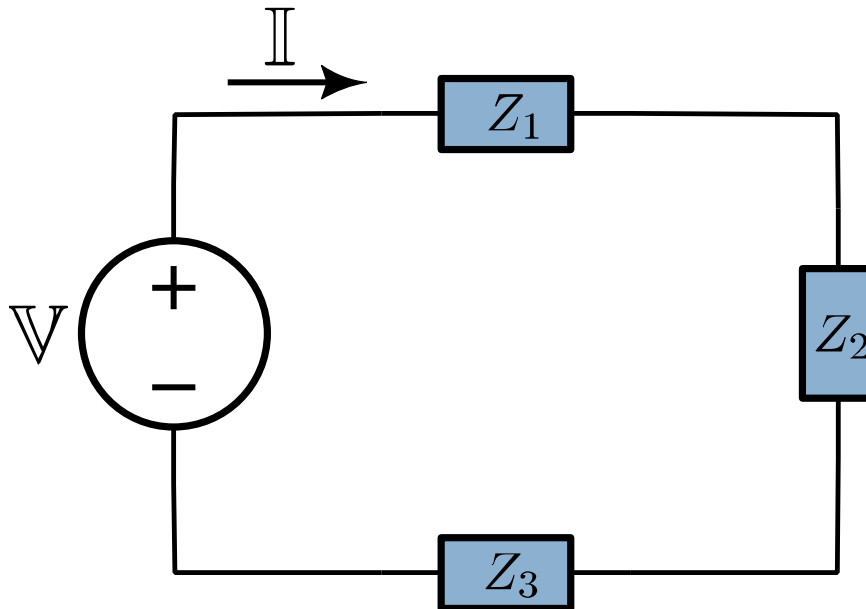

$$Z_{\text{eq}} = \sum_i Z_i$$


# Impedances in Parallel

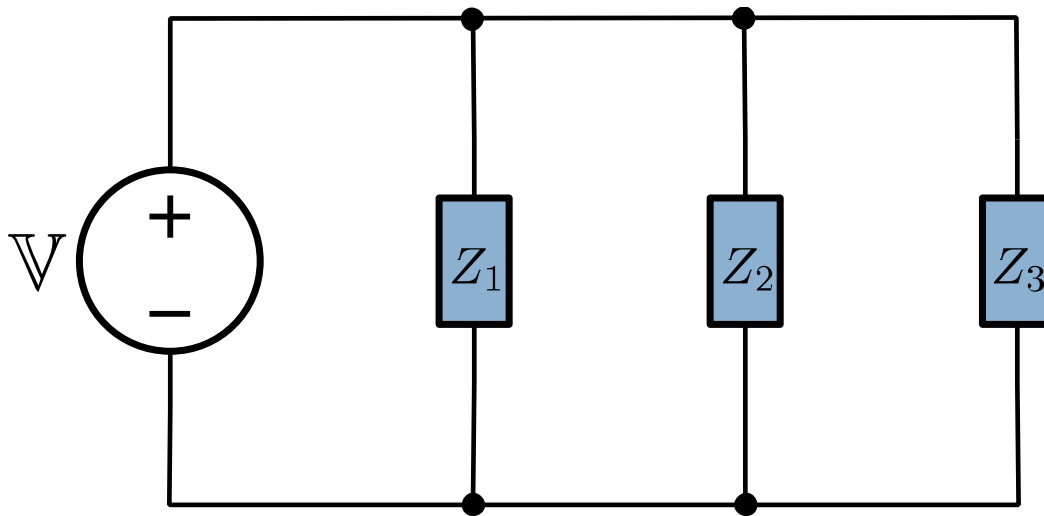


$$Z_{\text{eq}} = \left[ \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right]^{-1}$$

$$Z_{\text{eq}} = \left[ \sum_i \frac{1}{Z_i} \right]^{-1}$$

# Kirchhoff's Laws

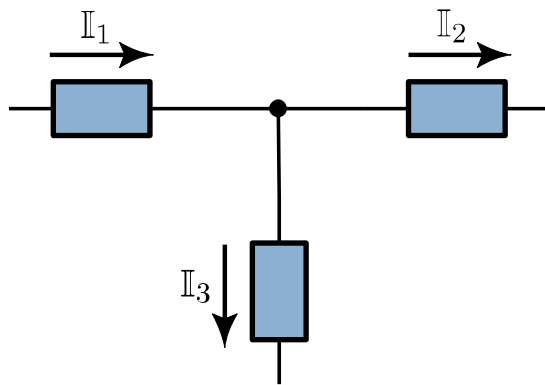


$$I_1 = I_2 + I_3$$

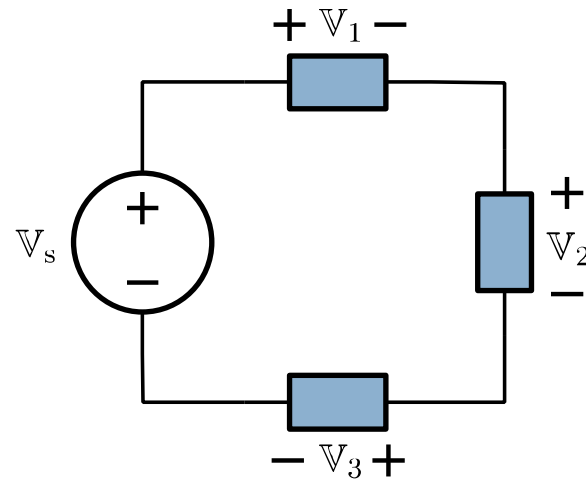


$$V_s = V_1 + V_2 + V_3$$

# Source Transformations

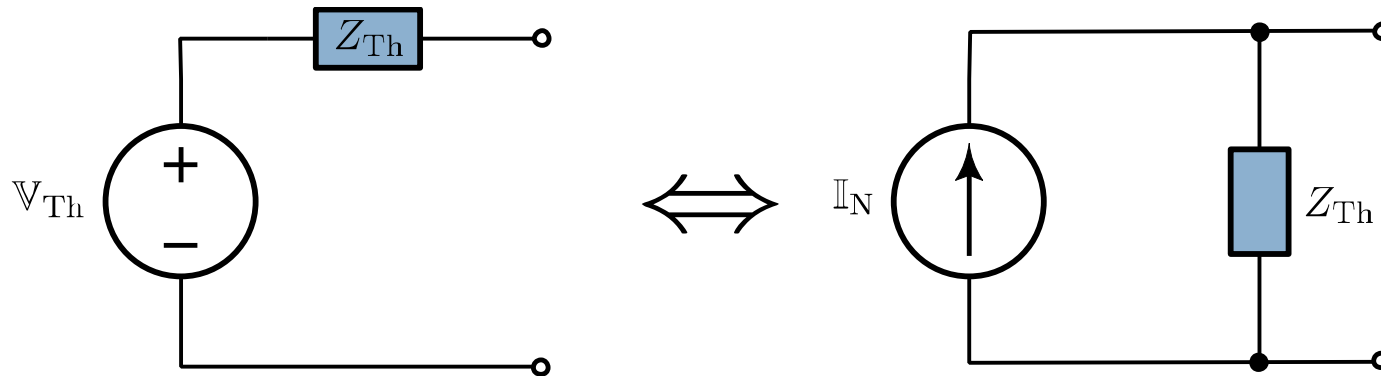

$$V_{Th} = I_N Z_{Th}$$

# Superposition

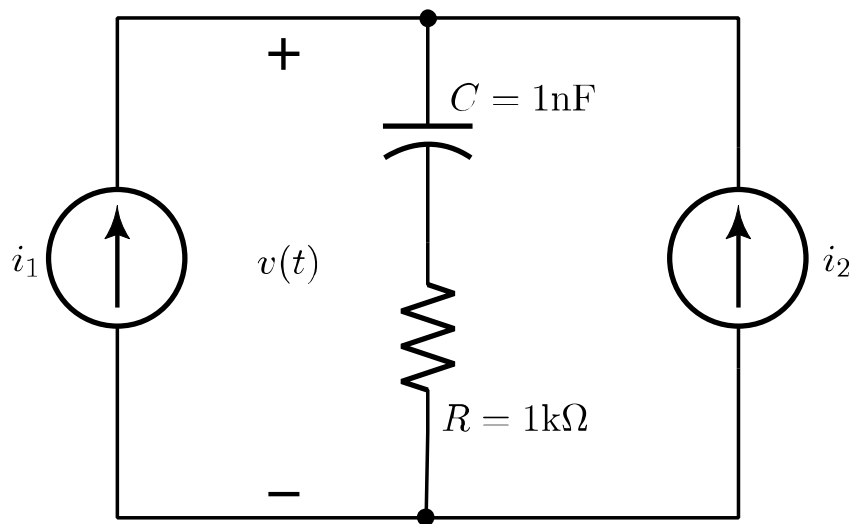


$$i_1(t) = \sqrt{2} \cos(10^6 t) \text{ A}$$

$$i_2(t) = 3 \sin\left(\frac{1}{\sqrt{3}} \cdot 10^6 t\right) \text{ A}$$

# Valid Impedance Techniques

- ⦿ Kirchhoff's Laws
- ⦿ Superposition
- ⦿ Node-voltage
- ⦿ Mesh-current
- ⦿ Thévenin and Norton Equivalent Circuits
- ⦿ Source Transformations

## Example

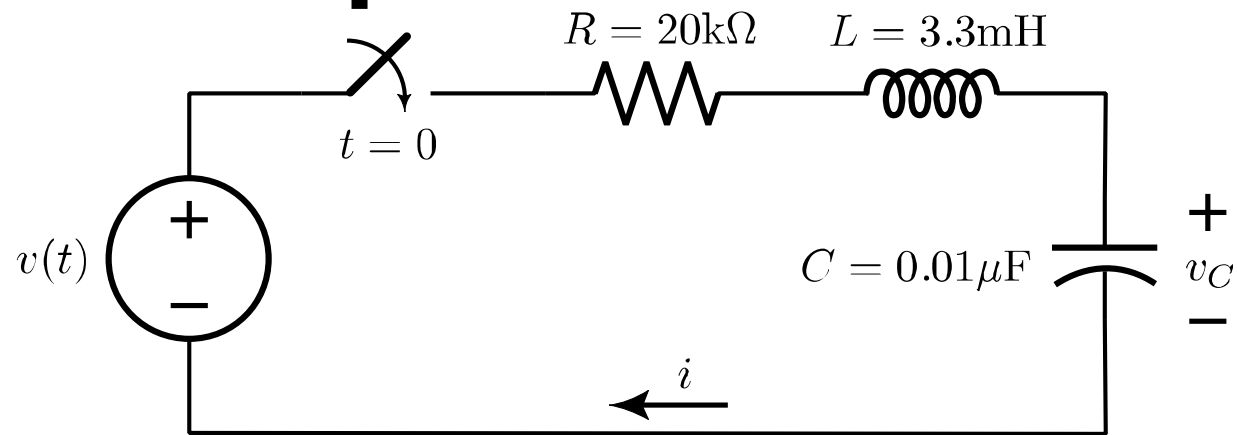

$$v(t) = \cos(2\pi(780)t)$$

## Summary

- ⦿ Showed how DC analysis techniques are applied in sinusoidal systems
- ⦿ Used superposition to analyze a system with multiple frequencies
- ⦿ Solved an example system using these techniques

## Next Lesson

- ⦿ Demo showing sinusoidal response
- ⦿ Transfer functions – how systems react across different frequencies