

Linear Circuits



Nathan V. Parrish

PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering



An introduction to linear electric circuit elements and a study of circuits containing such devices.

School of Electrical and Computer Engineering



Nathan V. Parrish

PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

Transfer Functions



Understand how linear systems react to inputs of different frequencies.

Previous Lesson

- ◎ AC analysis
- ◎ Sinusoidal response lab


Module 4: Frequency Analysis

- ⦿ Sinusoids and phasors
- ⦿ Impedance
- ⦿ Analysis of sinusoidal systems
- ⦿ Transfer functions
- ⦿ Frequency response
- ⦿ Low-pass and high-pass filters
- ⦿ Bandpass and notch filters

Lesson Objectives

- ◎ Describe the definition of a transfer function and how they are used
- ◎ Plot transfer functions in both linear and logarithmic spaces and interpret the results

Behavior of Sinusoids in Linear Systems

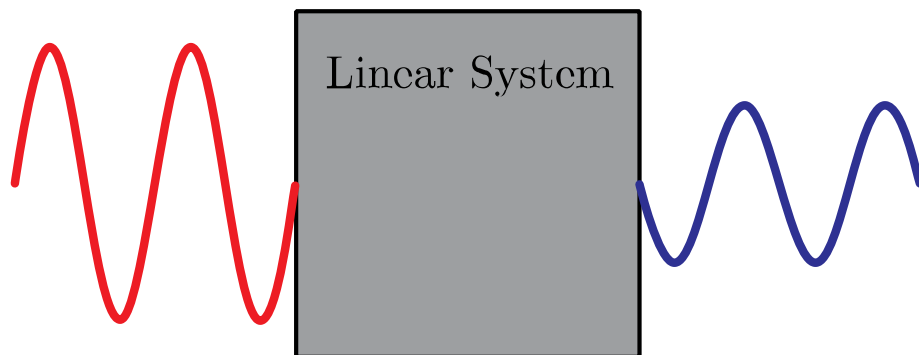


$$v_{\text{in}} = A_{\text{in}} \cos(\omega t + \theta_{\text{in}})$$

$$\mathbb{V}_{\text{in}} = A_{\text{in}} \angle \theta_{\text{in}}$$

$$v_{\text{out}} = A_{\text{out}} \cos(\omega t + \theta_{\text{out}})$$

$$\mathbb{V}_{\text{out}} = A_{\text{out}} \angle \theta_{\text{out}}$$

Transfer Function

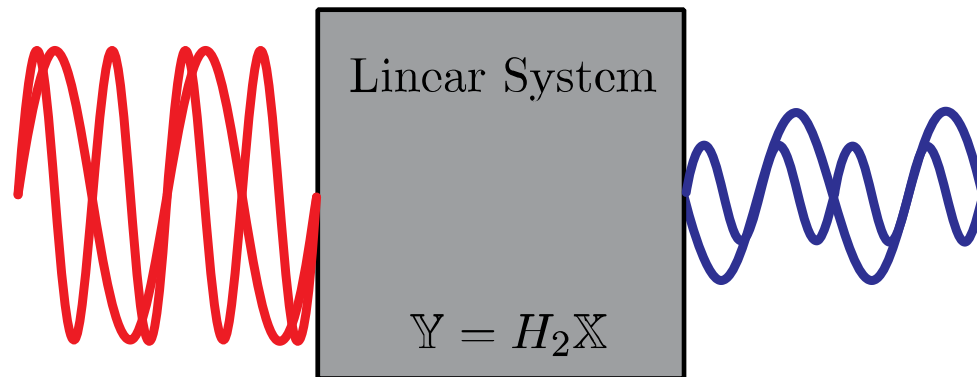

$$x(t) = X \cos(\omega_2 t)$$


$$\mathbb{X} = X \angle 0$$

$$y(t) = Y_2 \cos(\omega_2 t + \theta_2)$$

$$\mathbb{Y} = Y_2 \angle \theta_2$$


$$H(f) = \frac{\mathbb{Y}_f}{\mathbb{X}_f} = \frac{Y_f}{X_f} \angle \theta_{y,f} - \theta_{x,f}$$

Example 1: Effect of Frequency

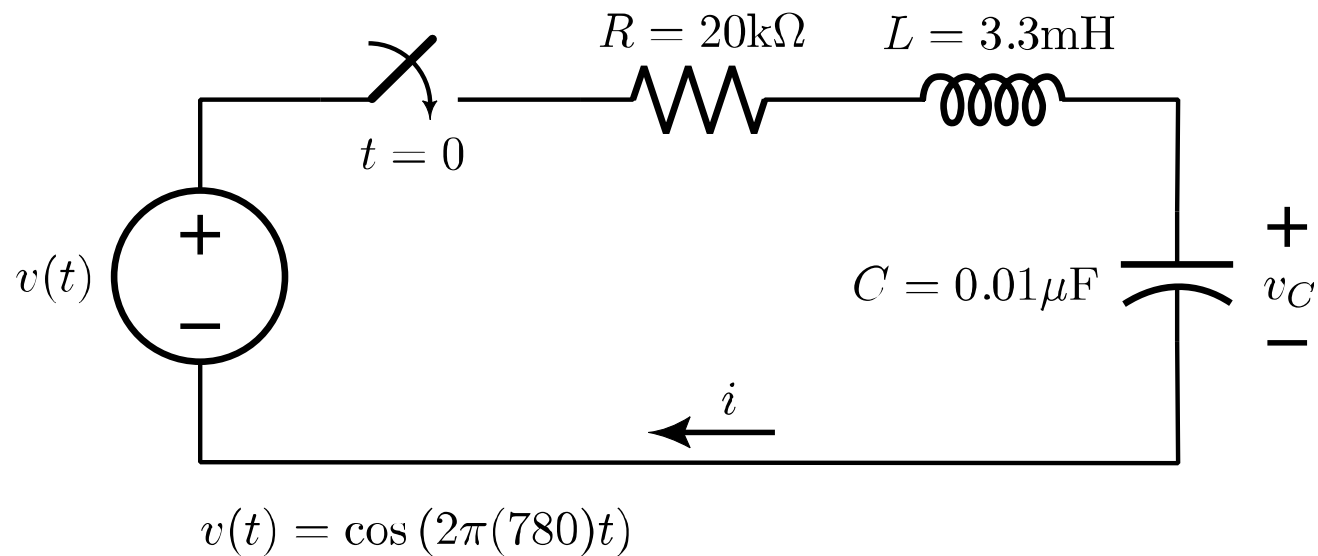

$$H(780) = 0.51 - j0.50 = \frac{1}{\sqrt{2}} \angle -\frac{\pi}{4}$$

Example 2: RC

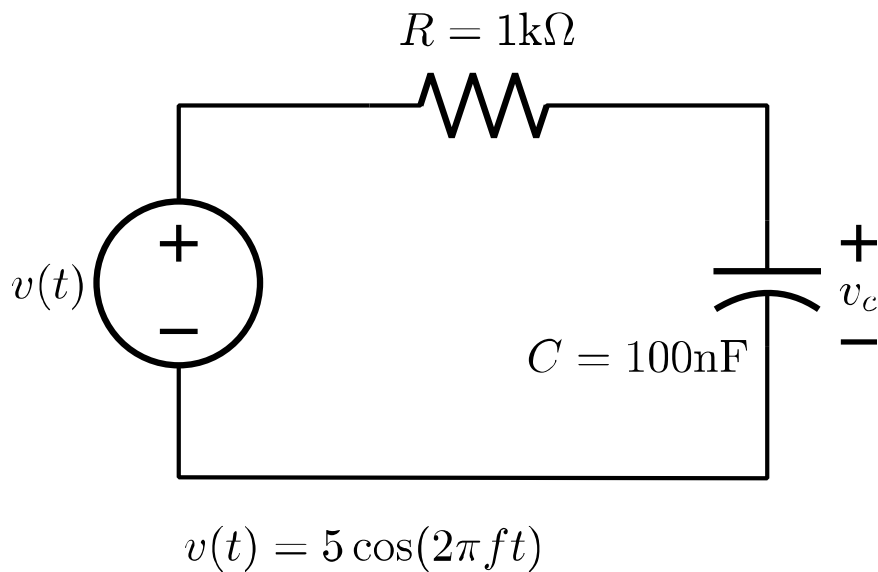


$$H(f) = \frac{1}{1+j2\pi fRC} \quad \text{Let } f_B = \frac{1}{2\pi RC}$$

$$H(f) = \frac{1}{1+j(f/f_B)}$$

$$|H| = \frac{1}{\sqrt{1+(f/f_B)^2}}$$

$$\angle H = -\text{atan}(f/f_B)$$


Transfer Function Plots

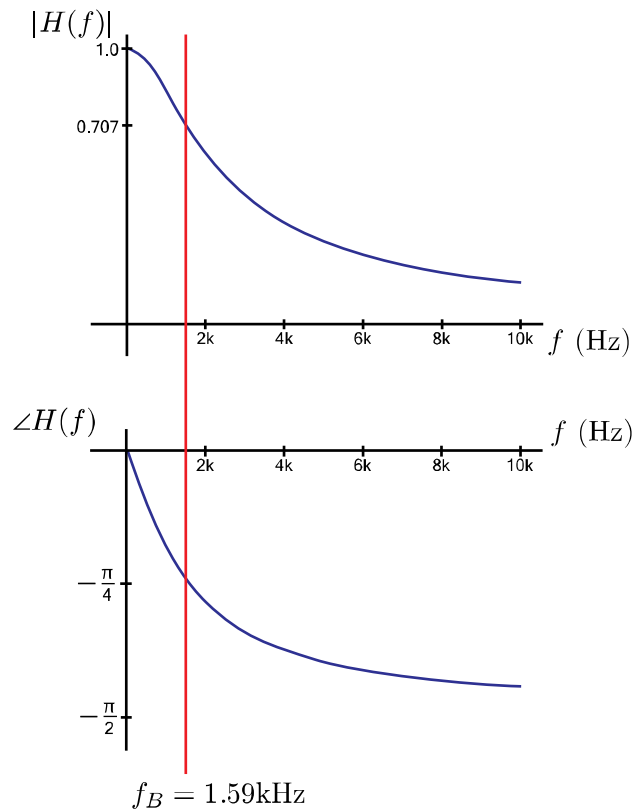

$$|H| = \frac{1}{\sqrt{1+(f/f_B)^2}}$$

$$\angle H = -\text{atan}(f/f_B)$$

Example 3: RLC

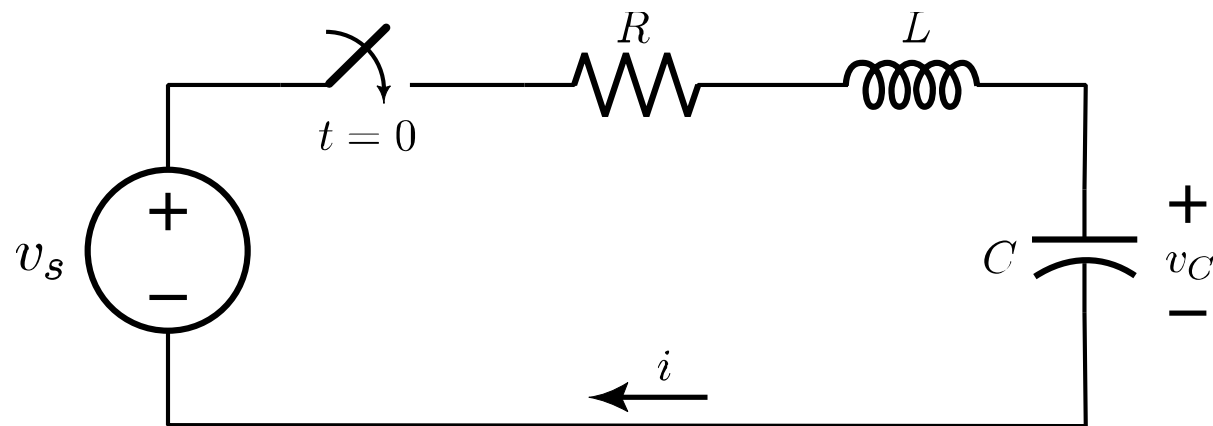

$$H(\omega) = \frac{1}{(1 - \omega^2 LC) + j\omega RC}$$

$$|H(\omega)| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

$$\angle H(\omega) = -\text{atan}\left(\frac{\omega RC}{1 - \omega^2 LC}\right)$$

Summary

- ⦿ Introduced the concept of a transfer function
- ⦿ Showed how to calculate a transfer function for a particular system
- ⦿ Demonstrated how to graph the magnitude and phase response

Next Lesson

- ◎ Time and frequency domain
- ◎ Demo with a guitar string to show frequency spectrum