



Nathan V. Parrish
PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

Linear Circuits



An introduction to linear electric circuit elements and a study of circuits containing such devices.



Nathan V. Parrish
PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

Power Factor and Power Triangles Part 1



Gain an understanding of the way that sinusoidal power is analyzed.

Previous Lesson

- ◎ Calculated RMS values
- ◎ Sinusoid and triangular function examples



Module 5: Power

- ◎ Root-Mean Square
- ◎ Power Factor and Power Triangles
- ◎ Maximum Power Transfer
- ◎ Transformers



Lesson Objectives

- ◎ Identify average power in resistive and reactive devices
- ◎ Calculate complex power

Instantaneous Power

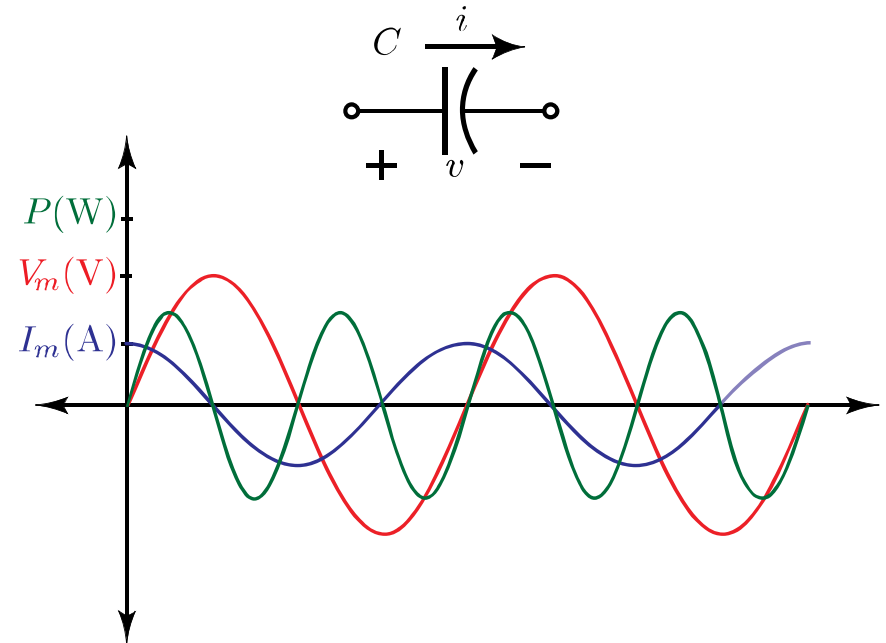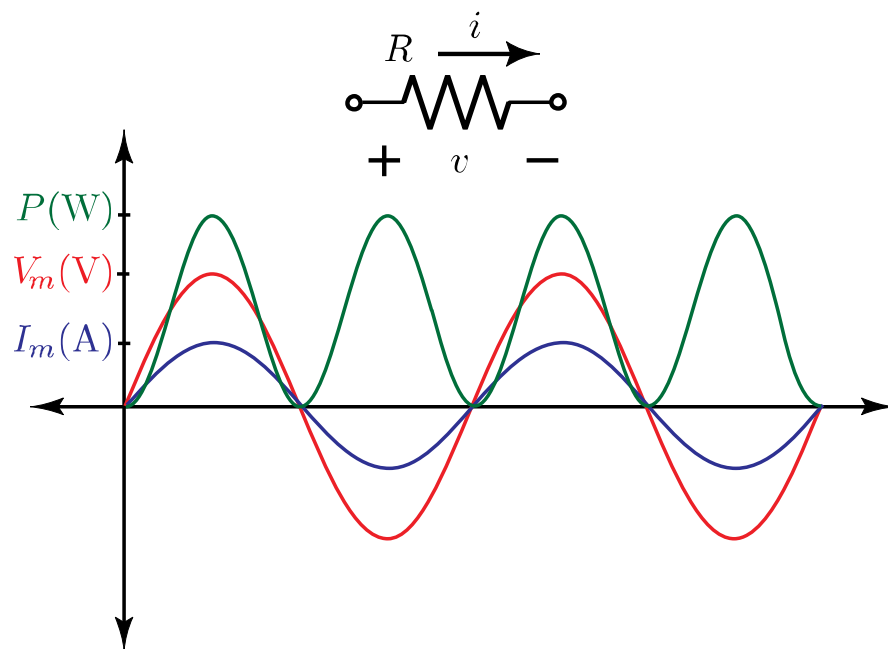


Average Power

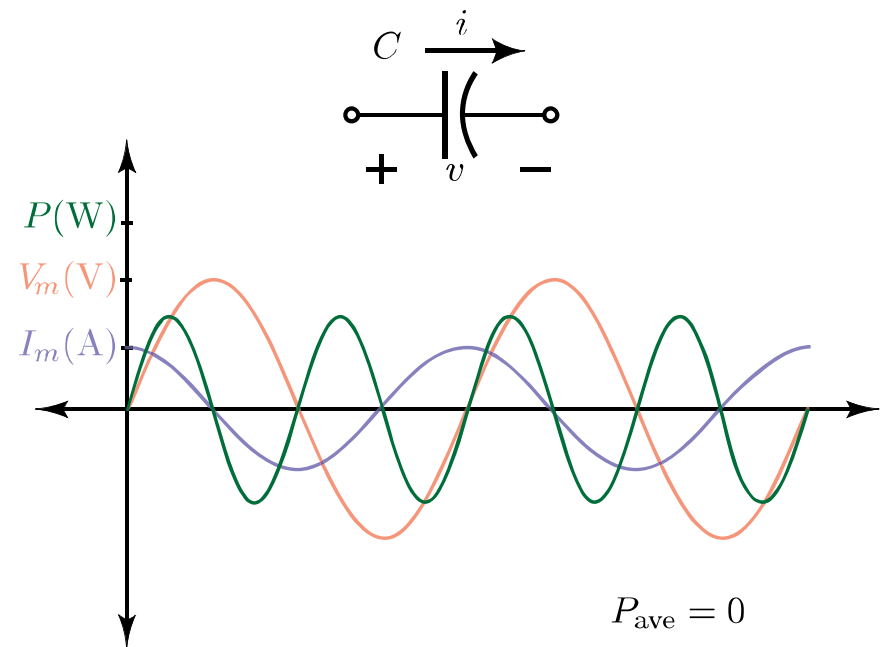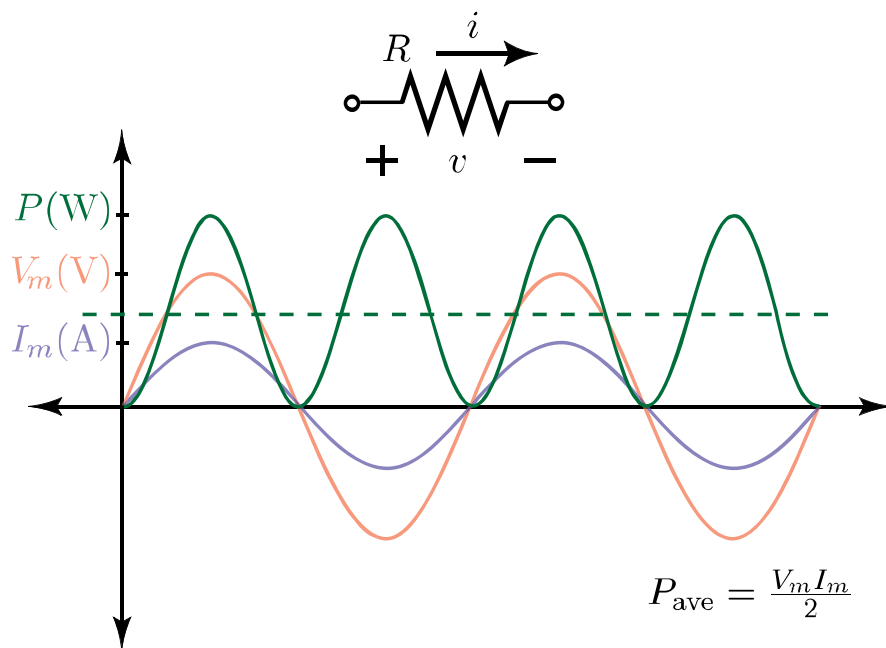

$$P_{\text{ave}} = \frac{V_m I_m}{2} = V_{\text{rms}} I_{\text{rms}}$$

Average Power

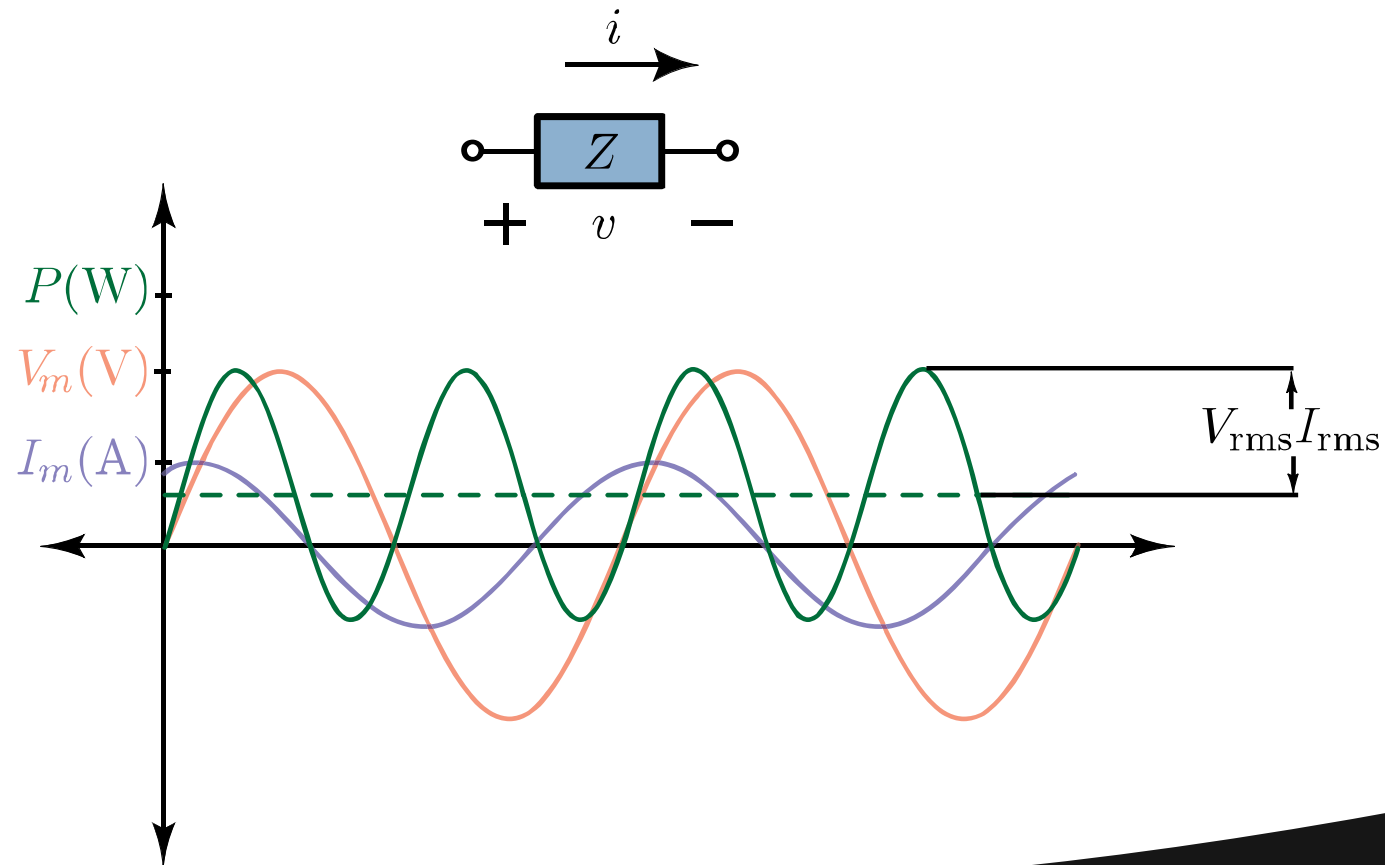

Complex Power

$$v = 5 \cos \left(\omega t + \frac{\pi}{3} \right)$$


$$i = 2.5 \cos \left(\omega t + \frac{\pi}{12} \right)$$

$$S = \frac{1}{2} \mathbb{V} \mathbb{I}^*$$

$$\mathbb{V} = V_m \angle \theta_v$$



$$\mathbb{I} = I_m \angle \theta_i$$
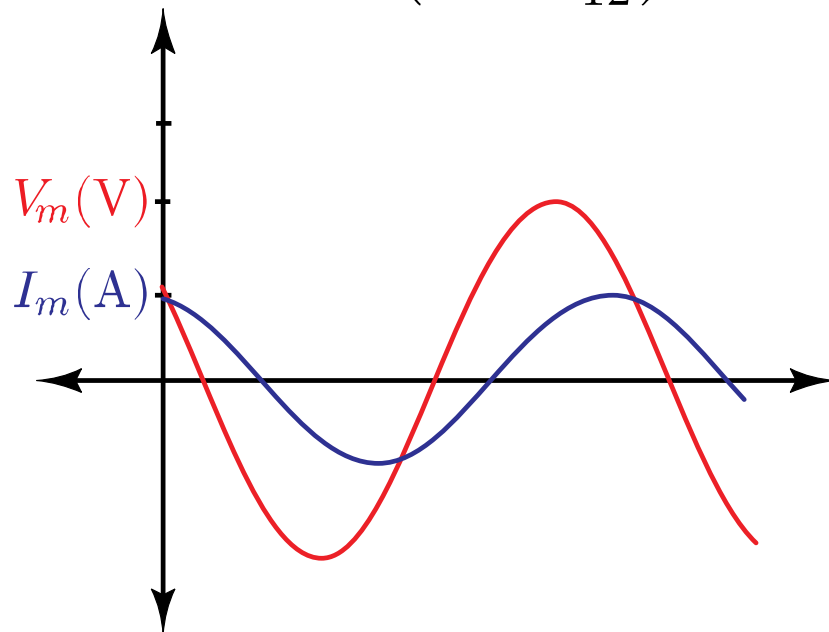
$$S = \frac{V_m I_m}{2} \angle \theta_v - \theta_i = 6.25 \angle \frac{\pi}{4}$$



What Complex Power Represents
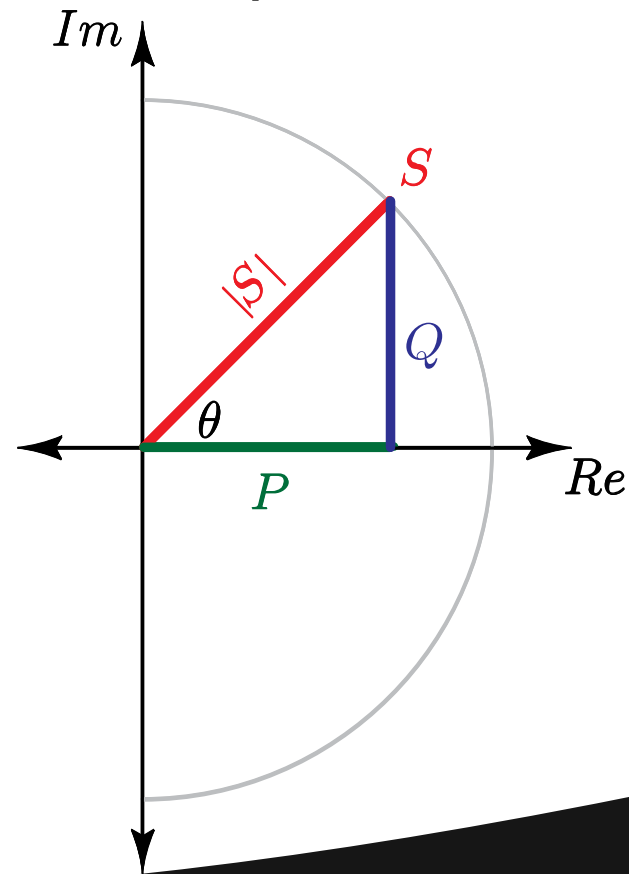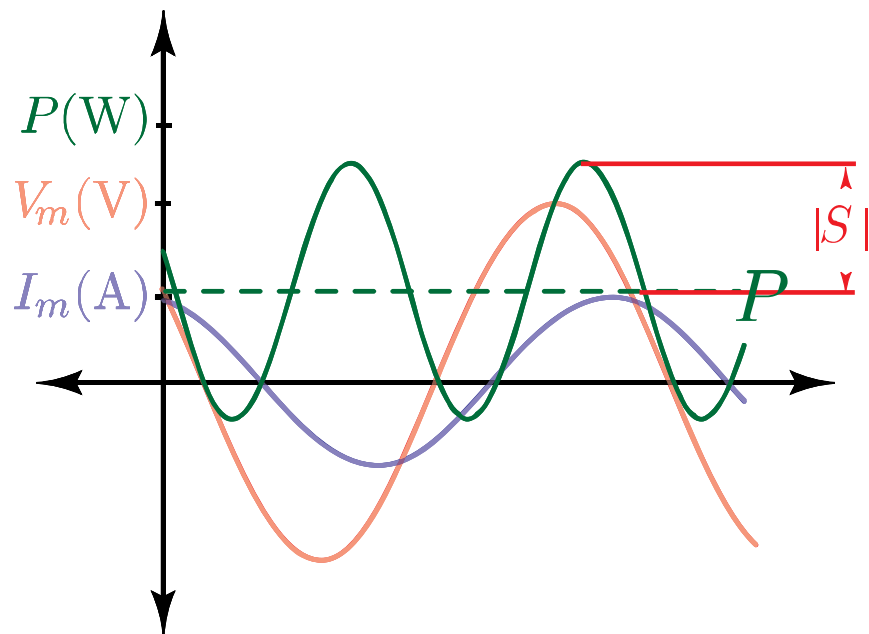
$$S = \frac{V_m I_m}{2} \angle \theta_v - \theta_i$$



Summary

- ◎ Calculated complex power
- ◎ Identified the meaning behind complex power

Next Lesson

- ◎ Power triangles
- ◎ Define important quantities for power analysis