



Nathan V. Parrish
PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

Linear Circuits



An introduction to linear electric circuit elements and a study of circuits containing such devices.



Nathan V. Parrish
PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

Sinusoidal Maximal Power Transfer

Show how maximum power transfer works in AC systems as contrasted to DC systems, and show how to use extra reactive loads for power factor correction.

Previous Lesson

- ◎ Showed how power is calculated in AC systems
- ◎ Defined the values associated with power triangles and how to use them


Module 5: Power

- ◎ Root-Mean Square
- ◎ Power Factor and Power Triangles
- ◎ Maximum Power Transfer
- ◎ Transformers


Lesson Objectives

- ◎ Be able to find the load impedance that gives maximum power transfer and the average power consumed by this load
- ◎ Be able to find the optimal purely resistive impedance that gives largest possible power transfer
- ◎ Be able to do power factor correction using additional reactive components
- ◎ Power budget

Thévenin and Norton Equivalent

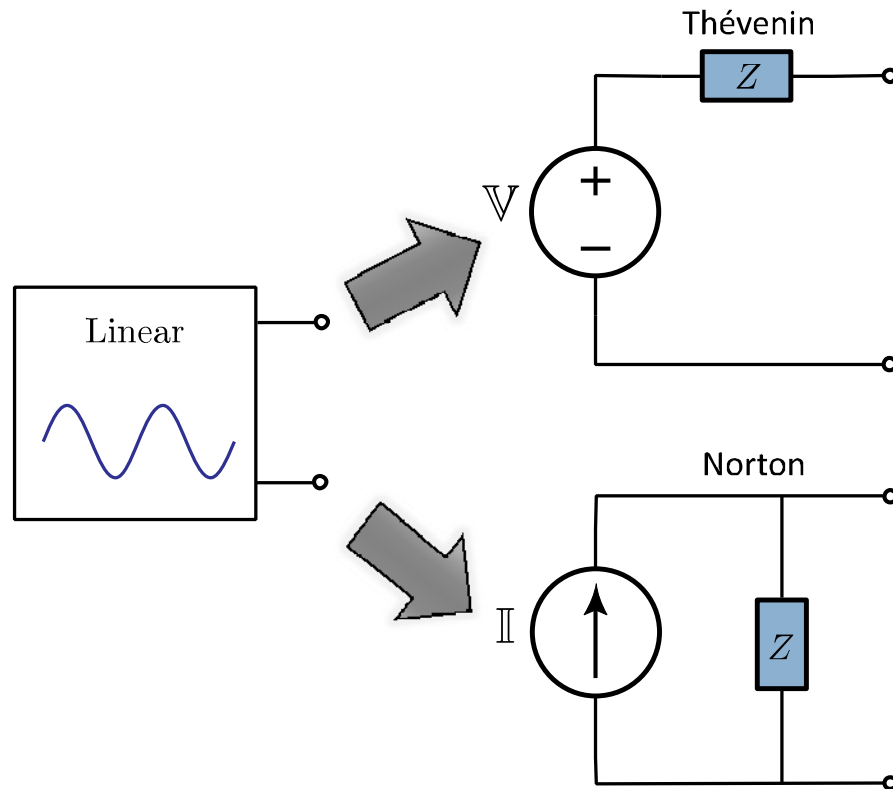

Maximum Power Transfer for AC

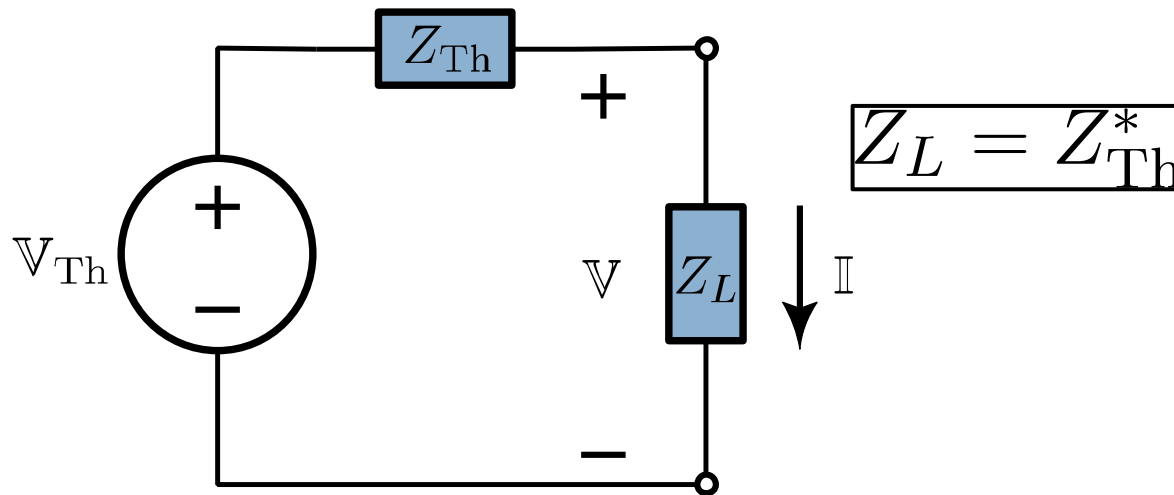

$$P = \frac{V_{Th}^2}{8\text{Re}(Z_{Th})}$$


$$Q = -\frac{V_{Th}^2 \text{Im}(Z_{Th})}{8[\text{Re}(Z_{Th})]^2}$$

$$V = \frac{Z_L}{Z_{Th} + Z_L} V_{Th}$$

$$I = \frac{V_{Th}}{Z_{Th} + Z_L}$$

$$S = \frac{1}{2} V I^*$$


Example 1

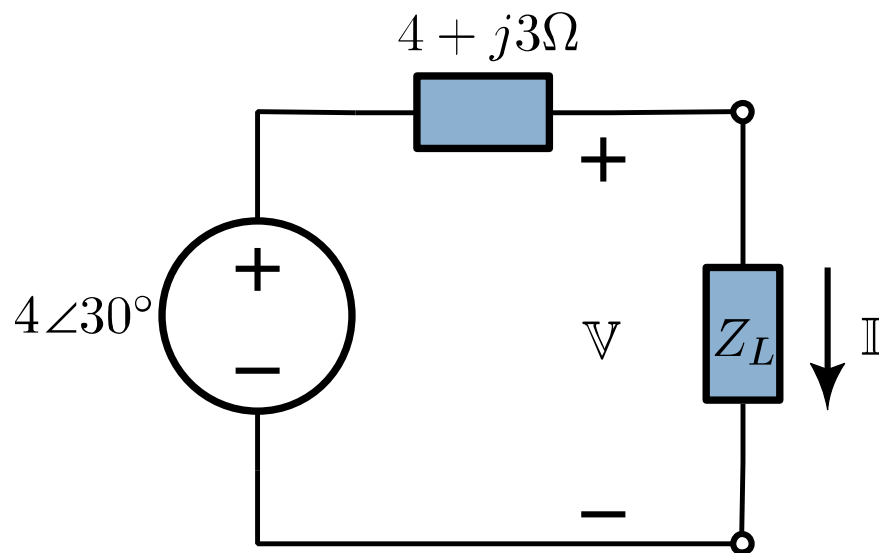

$$P = \frac{V_{Th}^2}{8\text{Re}(Z_{Th})}$$


$$Z_L = Z_{Th}^*$$

Max Transfer with Constrained Load Phase

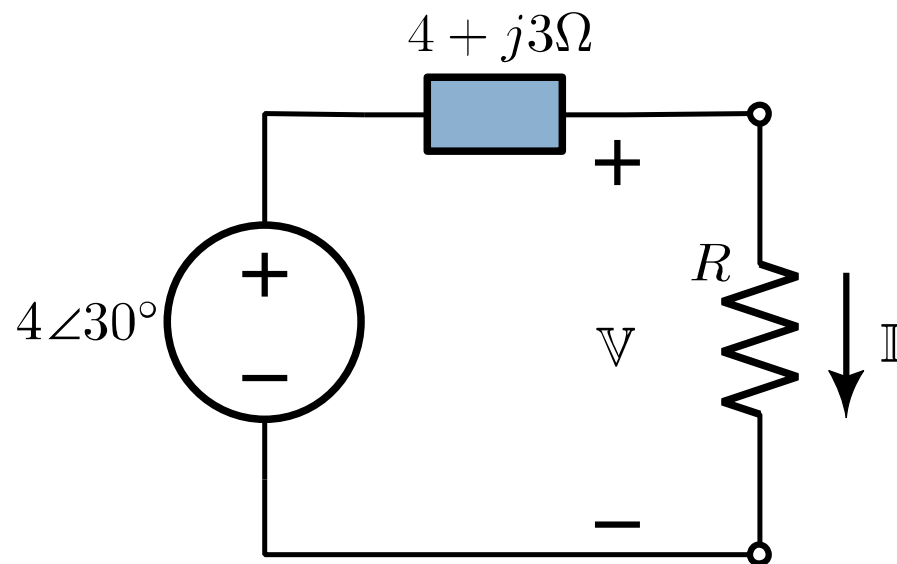

$$Z_L = Z_{Th}$$

Power Factor Correction

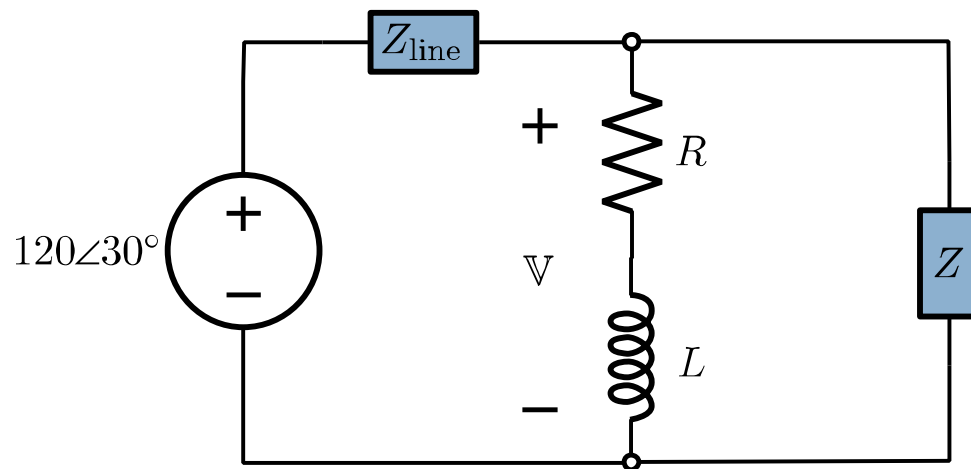

$$S = \frac{1}{2} \mathbb{V} \mathbb{I}^* = \frac{|\mathbb{V}|^2}{2Z^*} = \frac{|\mathbb{I}|^2 Z}{2}$$

$$C = \frac{L}{R^2 + \omega^2 L^2}$$

Comments on Power Factor Correction

- ◎ Purely reactive devices use no power
- ◎ May also want to correct for line impedance
- ◎ Adding the capacitor changes the voltage and so also the power behavior of the system
- ◎ Using capacitors is a common practice in heavy industry to limit reactive power

Summary

- ◎ Found impedance that gives maximum power transfer
- ◎ Found best impedance given the load must be purely resistive
- ◎ Used a capacitor for power factor correction and found the capacitance that gives a particular power factor

Next Lesson

- ◎ New device: transformers