



Nathan V. Parrish
PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

Linear Circuits



An introduction to linear electric circuit elements and a study of circuits containing such devices.



Nathan V. Parrish
PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

Linear Model of Transformers

Present linear model for analyzing transformers.




Previous Lesson

- ◎ Introduced transformers and how they work
- ◎ Identified some analysis models which exist for transformers

Lesson Objectives

- ◎ Identify the linear model of transformers
- ◎ Use circuit analysis to analyze the behavior of a transformer system
- ◎ Apply this analysis to solving a transformer circuit problem

Linear Transformer

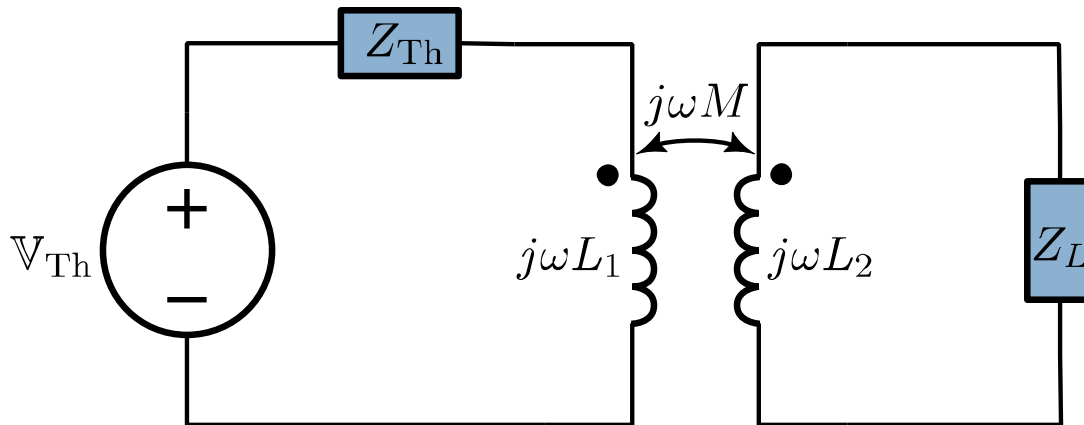


$$\begin{aligned} V_{Th} &= (Z_{Th} + j\omega L_1)I_1 - j\omega M I_2 \\ 0 &= (Z_L + j\omega L_2)I_2 - j\omega M I_1 \end{aligned}$$

$$I_1 = \frac{Z_L + j\omega L_2}{(Z_{Th} + j\omega L_1)(Z_L + j\omega L_2) + \omega^2 M^2} V_{Th}$$

$$Z_{eq} = \frac{V_{Th}}{I_1} = Z_{Th} + j\omega L_1 + \frac{\omega^2 M^2}{Z_L + j\omega L_2}$$

Reflected
impedance

Transformer Example

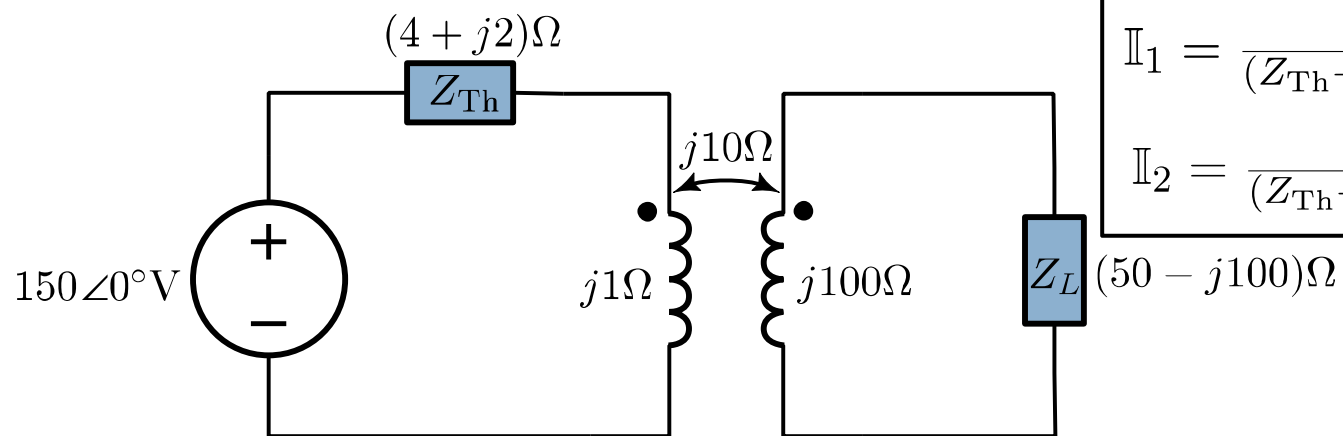

$$\mathbb{I}_1 = \frac{Z_L + j\omega L_2}{(Z_{Th} + j\omega L_1)(Z_L + j\omega L_2) + \omega^2 M^2} \mathbb{V}_{Th}$$

$$\mathbb{I}_2 = \frac{j\omega M}{(Z_{Th} + j\omega L_1)(Z_L + j\omega L_2) + \omega^2 M^2} \mathbb{V}_{Th}$$

Summary

- ◎ Presented the linear model
- ◎ Derived the phenomenon of reflected impedance
- ◎ Used circuit analysis to analyze an example transformer circuit

Next Lesson

- ◎ Ideal transformer model