

Linear Circuits



Nathan V. Parrish
PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

An introduction to linear electric circuit elements and a study of circuits containing such devices.

Ideal Transformers



Nathan V. Parrish
PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

Use the ideal transformer model for transformer analysis.




Previous Lesson

- ◎ Presented the linear model for analyzing transformers

Lesson Objectives

- ◎ Identify the assumptions used for the ideal transformer model
- ◎ Use the ideal transformer model for doing simple circuit analysis
- ◎ Describe the importance of transformers in power transmission

k : Coefficient of Coupling

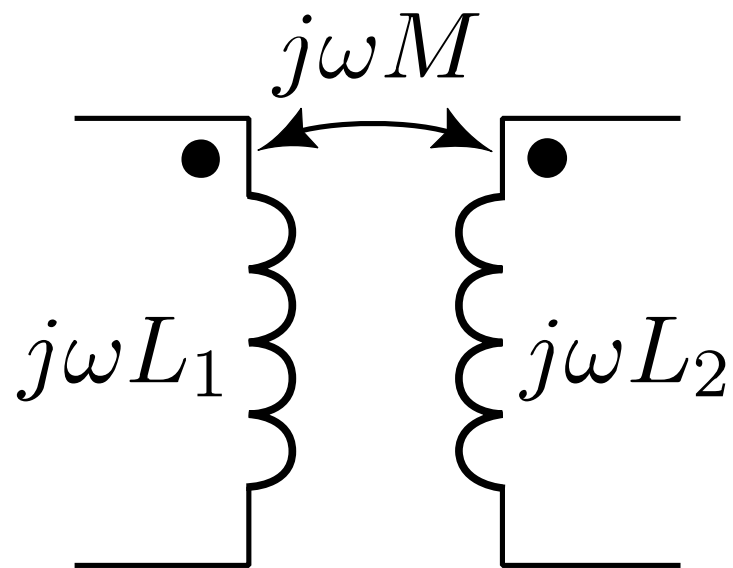


$$0 \leq k \leq 1$$

$$L_1 = 4\text{mH} \quad L_2 = 9\text{mH} \quad M = 2\text{mH}$$


$$M = k\sqrt{L_1 L_2}$$

The Ideal Transformer

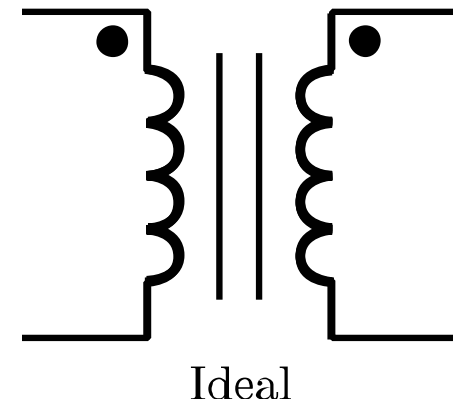- ⊙ Coupling coefficient $k=1$
- ⊙ $L_1 = L_2 = \infty$
- ⊙ Losses from coil resistances are negligible




Properties of the Ideal Transformer

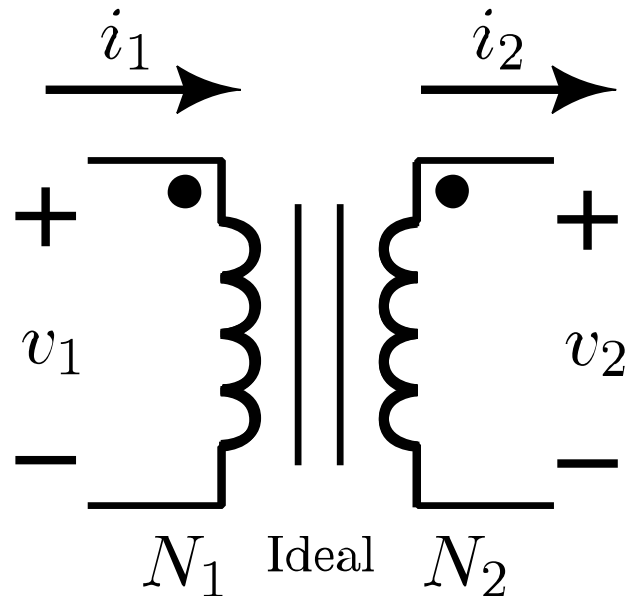

$$\frac{v_1}{N_1} = \frac{v_2}{N_2}$$

$$N_1 i_1 = N_2 i_2$$

Example

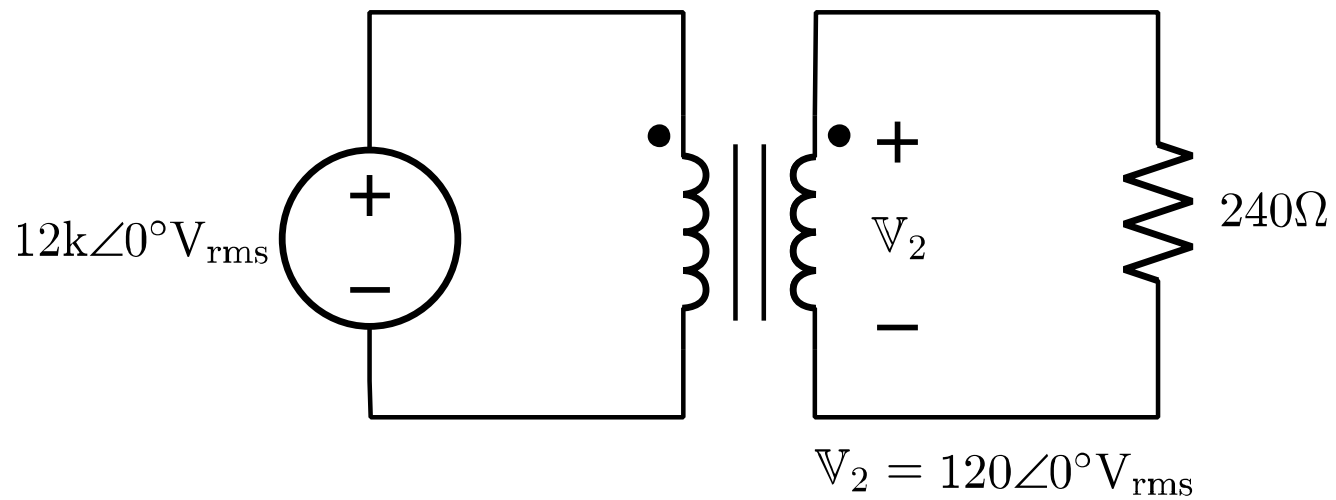

Implications

- ◎ Transformers allow a change from one voltage to another voltage
- ◎ High-voltage low-current power transmission allows long-distance power distribution systems

Summary

- ⦿ Showed the ideal transformer model
- ⦿ Used the model to solve an example system
- ⦿ Identified the usefulness of transformers for power transmission

Next Lesson

- ◎ Sensor: linear-variable differential transformers (LVDT)