

Linear Circuits




Nathan V. Parrish
PhD Candidate & Graduate
Research Assistant
School of Electrical and
Computer Engineering

An introduction to linear electric components and a study of circuits containing such devices.



Concept Map: Power

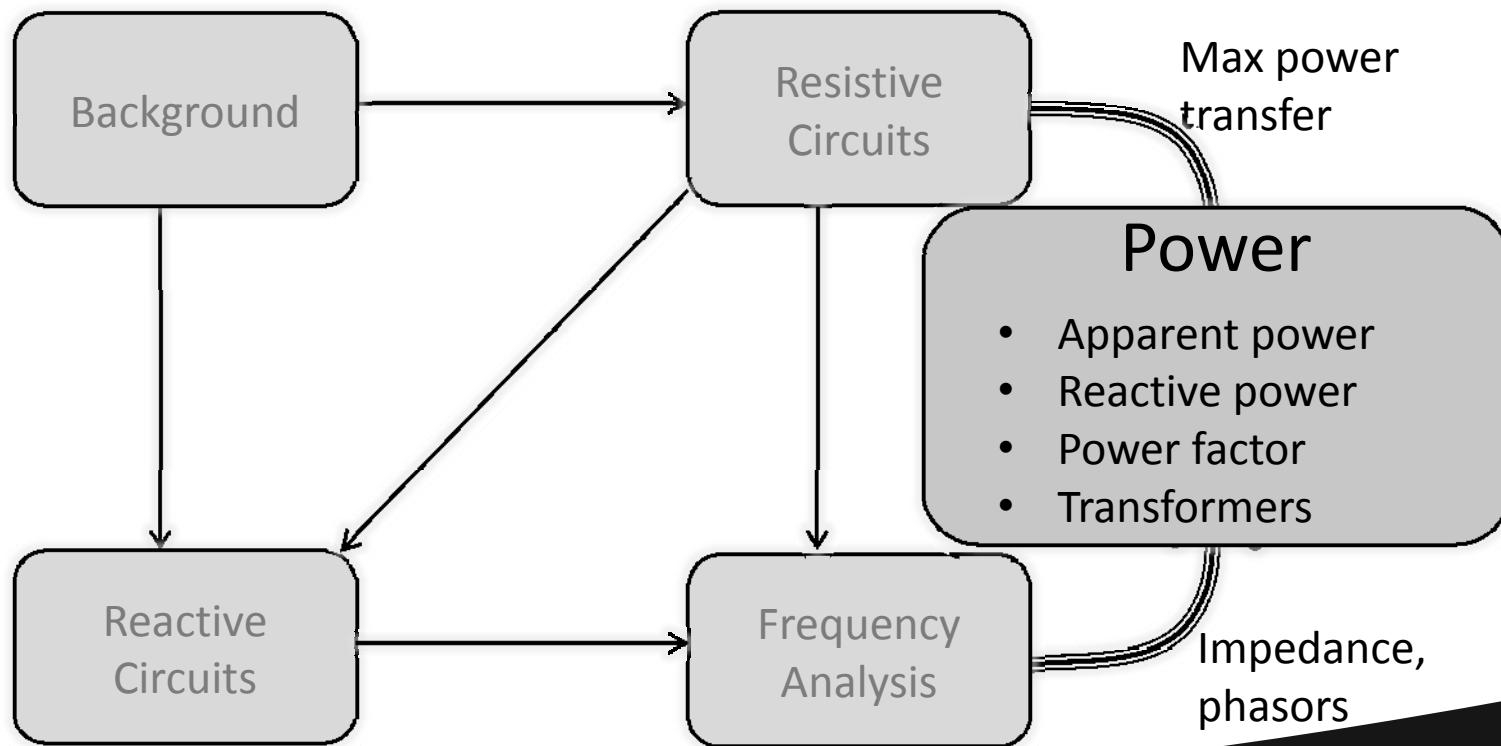

Important Concepts and Skills

◎ ROOT MEAN SQUARE

- Be able to calculate the root-mean square of a periodic function
- Recognize that RMS is invariant to frequency
- Use known RMS value equations to find RMS values given peak values
- Use known RMS value equations to find peak value given RMS values

Important Concepts and Skills

◎ **POWER FACTOR AND POWER TRIANGLES**

- Calculate the complex power from either equations or phasors
- Generate power triangles
- Using power triangles, be able to find
 - Apparent power, $|S|$
 - Real (or average) power, P
 - Reactive power, Q
 - Power factor
 - Power angle

Important Concepts and Skills

◎ **POWER FACTOR AND POWER TRIANGLES**

- Using the phase angle, identify if a load is resistive, capacitive, or inductive
- From equations, identify if a load is resistive, capacitive, or inductive
- From a plot of current and voltage, identify if a load is reactive, capacitive, or inductive
- Recognize if a system is “leading” or “lagging”

Important Concepts and Skills

◎ **MAXIMUM POWER TRANSFER IN AC**

- Calculate the impedance which gives maximal power transfer
- Calculate the average power consumed when the load gives maximal power transfer
- Find the optimal purely resistive load for constrained maximal power transfer
- Calculate average power for purely resistive load

Important Concepts and Skills

◎ TRANSFORMERS

- Describe the physical effects which make transformers work
- Use the linear model to analyze a circuit with a transformer
- Use the ideal model to analyze a circuit with a transformer
- Identify circumstances when a transformer is an appropriate device to be used in a system
- Explain how the use of transformers allow long-distance power distribution
- Describe why transformers do not typically function for direct current systems
- Identify, from amplitude and phase, the relative displacement for an LVDT transformer