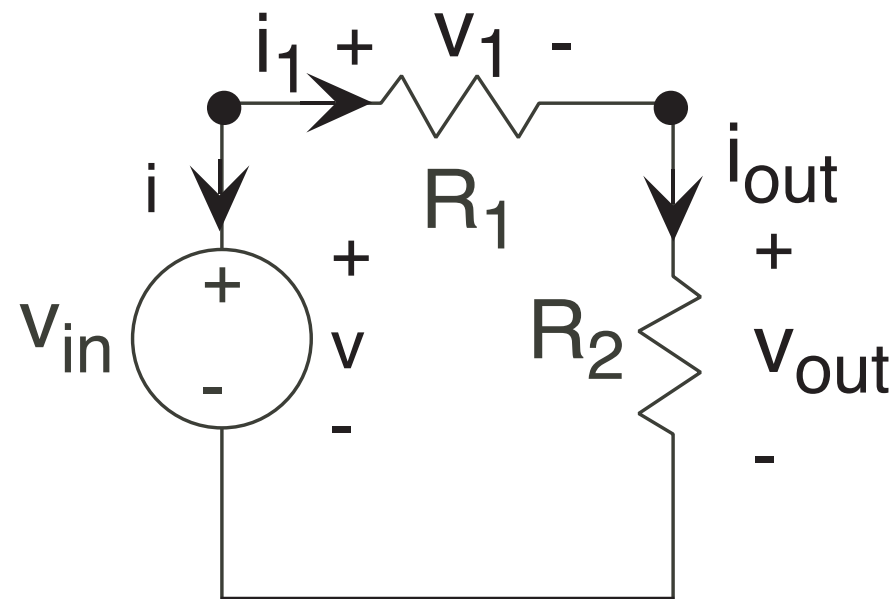


Fundamentals of Electrical Engineering

Circuit Interconnection Laws

- Kirchhoff's Current Law
- Kirchhoff's Voltage Law

A Simple Circuit




$$v(t) = v_{\text{in}}(t)$$

$$v_1 = R_1 i_1(t)$$

$$v_{\text{out}}(t) = R_2 i_{\text{out}}(t)$$

Kirchhoff's Current Law (KCL)

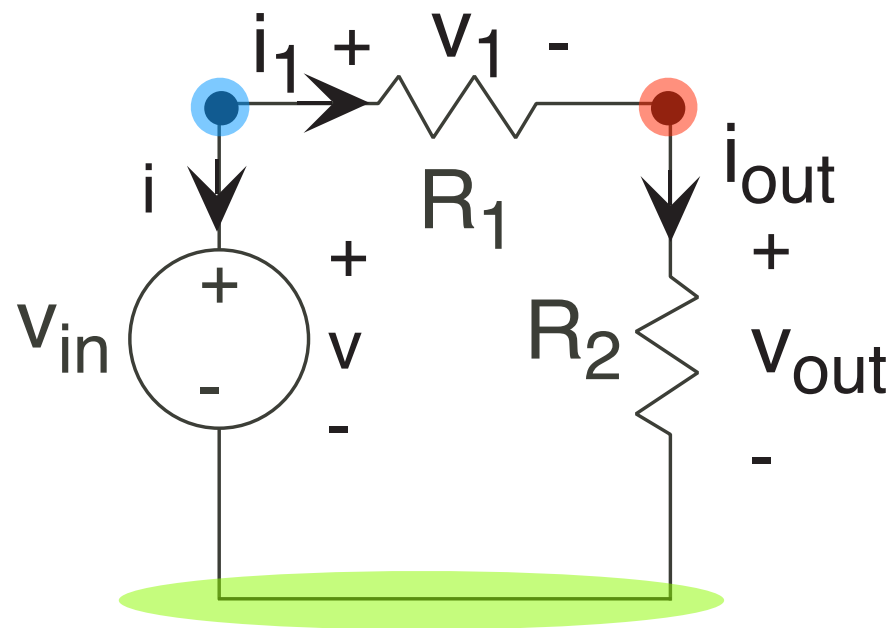
- The sum of currents entering a node (or leaving a node) equals zero



● $-i - i_1 = 0$

● $i_1 - i_{out} = 0$


● ~~$i + i_{out} = 0$~~

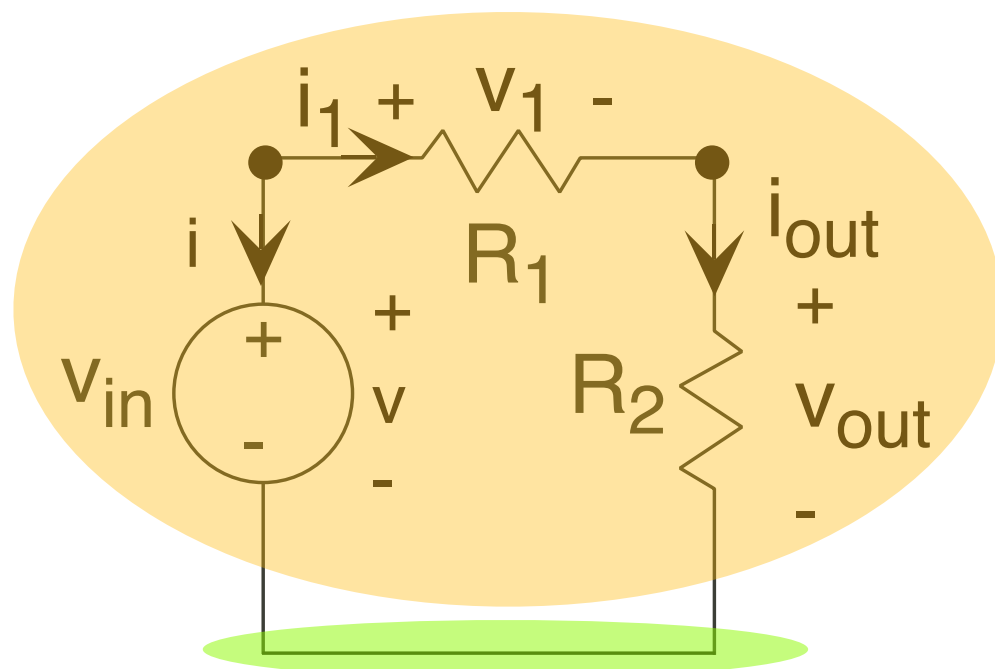


For an n node circuit, only $n-1$ KCL equations are linearly independent

Kirchhoff's Voltage Law (KVL)

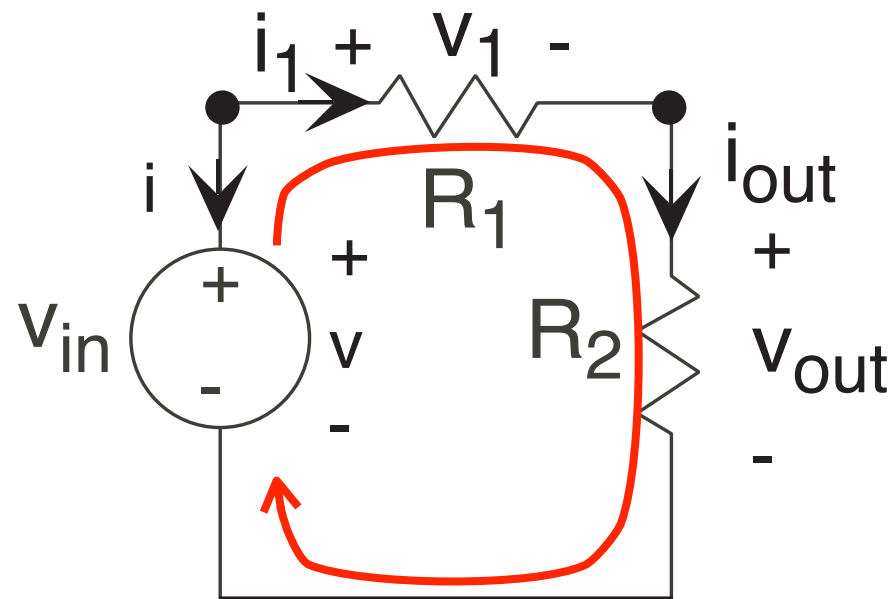
- The sum of voltages around any closed loop equals zero



$$v_1 + v_{out} - v = 0$$

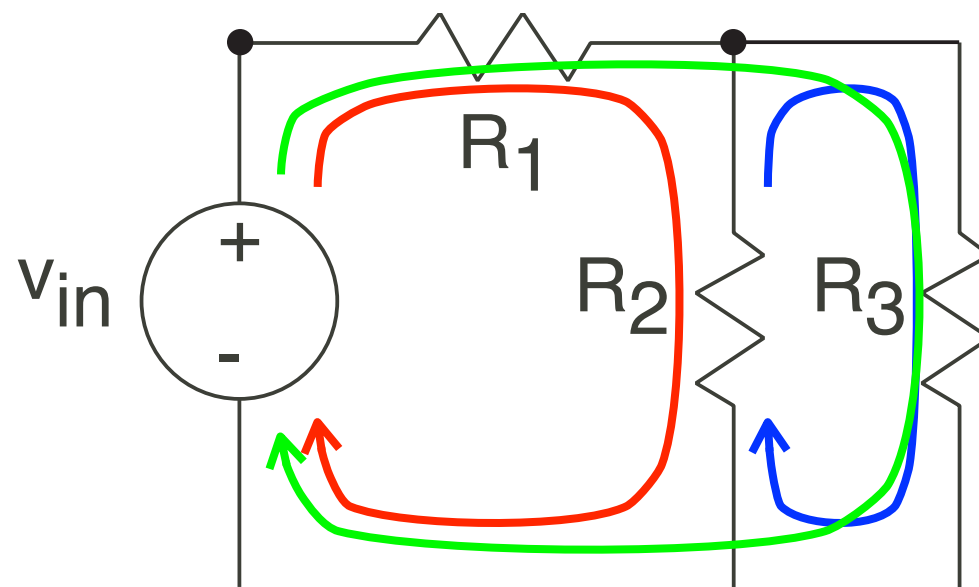

Solving the Circuit

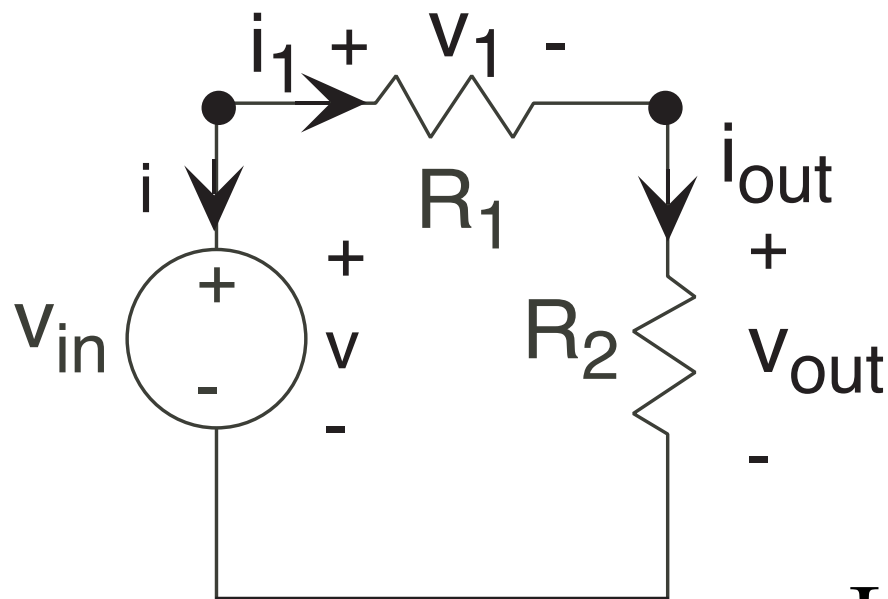

v - i relations:

$$v(t) = v_{in}(t)$$

$$v_1 = R_1 i_1(t)$$

$$v_{out}(t) = R_2 i_{out}(t)$$

KCL equations:

$$-i - i_1 = 0$$



$$i_1 - i_{out} = 0$$

KVL equation: $v_1 + v_{out} - v = 0$

After some manipulation, it is *easily* shown that


$$v_{out}(t) = \frac{R_2}{R_1 + R_2} v_{in}(t)$$

What Does Our Circuit Do?

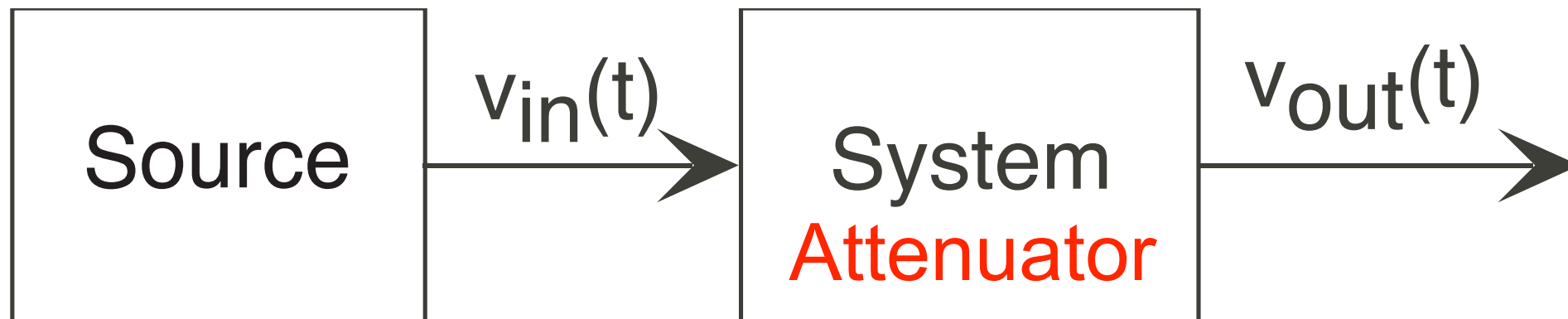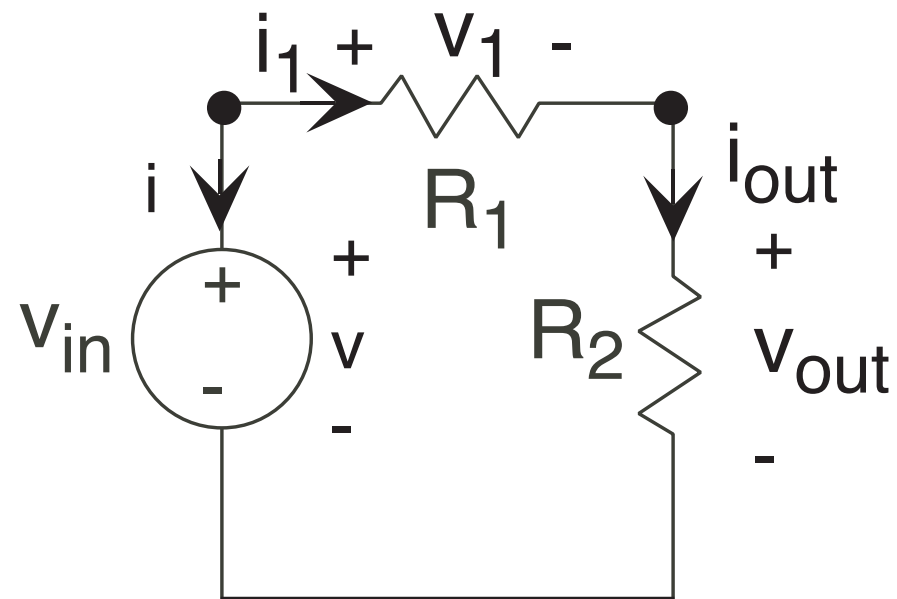

$$v_{out}(t) = \frac{R_2}{R_1 + R_2} v_{in}(t)$$

Circuits and Power

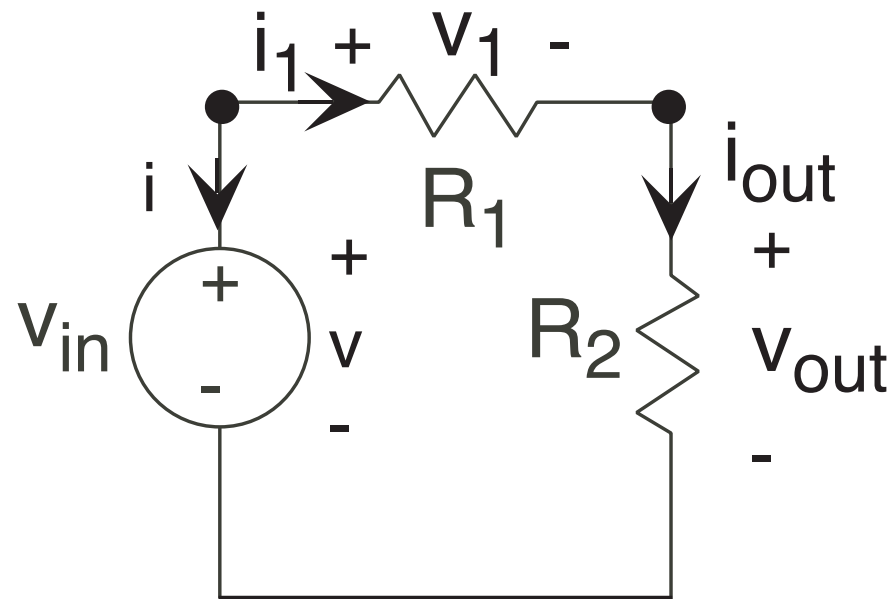

$$p_2(t) = \frac{v_{out}^2}{R_2} = \frac{R_2}{(R_1 + R_2)^2} v_{in}^2$$

$$p_1(t) = \frac{v_1^2}{R_1} = \frac{R_1}{(R_1 + R_2)^2} v_{in}^2$$

Since $i_{out} = \frac{v_{out}}{R_2}$, $i_{out} = \frac{v_{in}}{R_1 + R_2}$

Now $i = -i_{out}$, which means $p_{source}(t) = -\frac{v_{in}^2}{R_1 + R_2}$

No net power produced or consumed!

$$\sum_k v_k(t) \cdot i_k(t) = 0$$

Circuit Interconnection Laws

- Along with the v - i relations, KVL and KCL *always* provide exactly the number of equations needed to solve *any* circuit
- Need streamlined methods for solving circuit equations
- Later, we will show that only KVL and KCL are needed to show that circuits conserve power