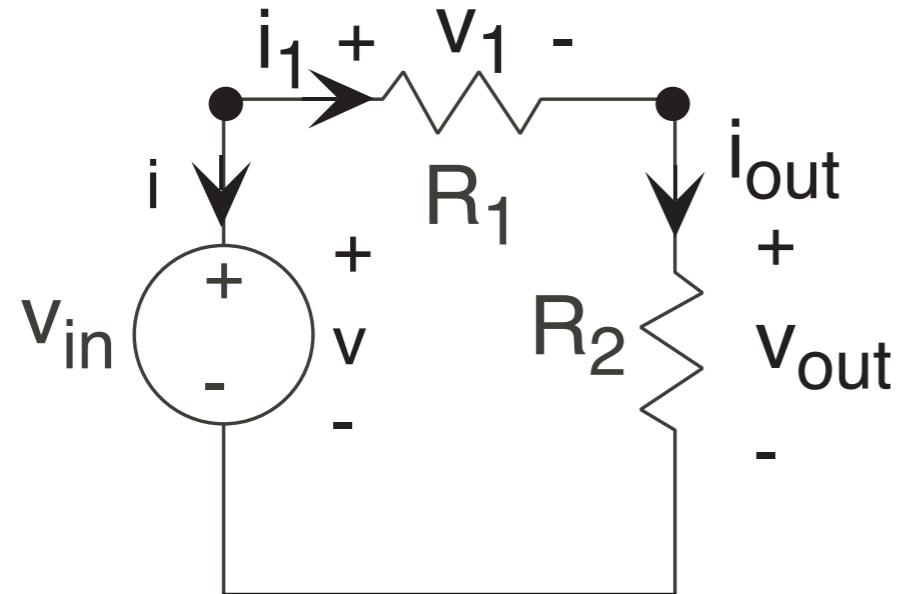


Fundamentals of Electrical Engineering

Equivalent Circuits

- What does a source “see”?
- Series and parallel combinations

Our Simple Circuit



$$v_{out}(t) = \frac{R_2}{R_1 + R_2} v_{in}(t)$$




voltage divider




RICE

Our Simple Circuit

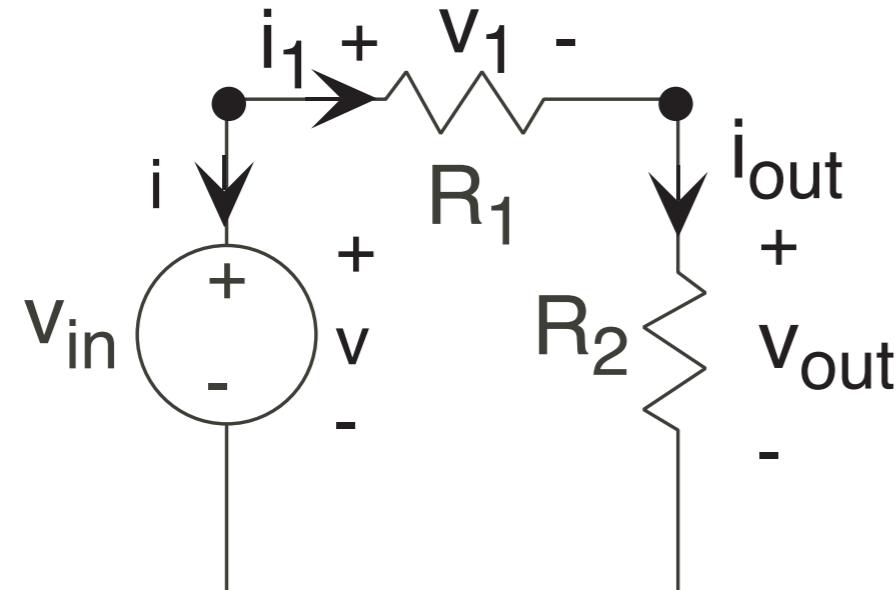

$$v_{\text{out}}(t) = \frac{R_2}{R_1 + R_2} v_{\text{in}}(t)$$
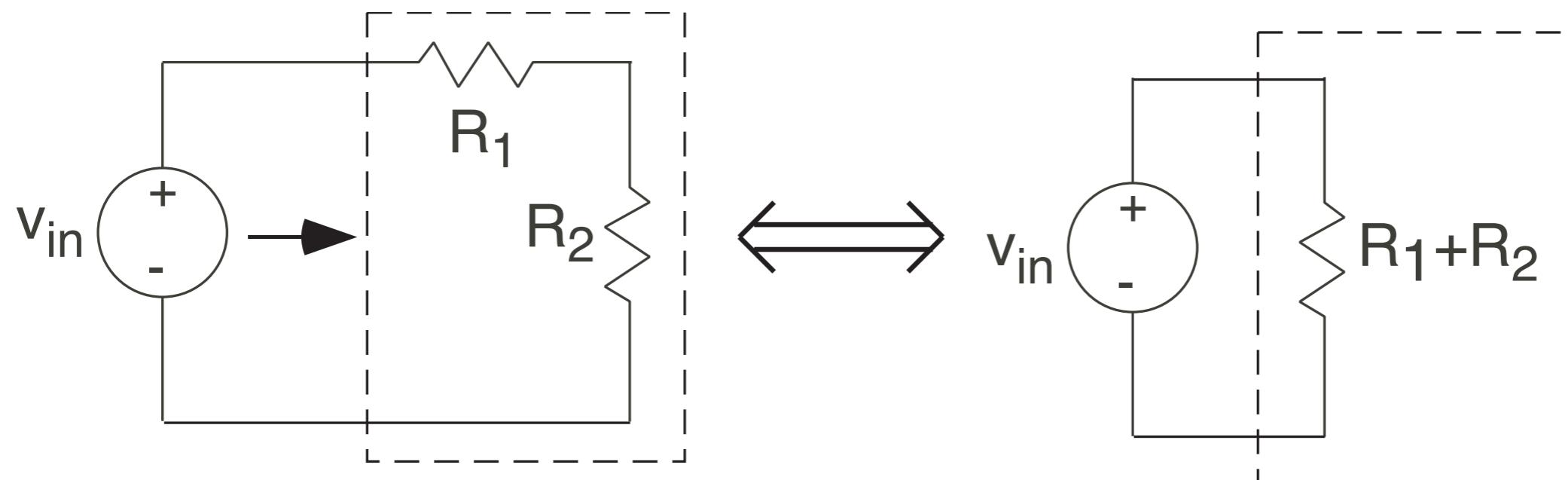
$$i_1 = \frac{v_{\text{in}}}{R_1 + R_2}$$




Resistors in series appear to be a *single* resistor, the value of which is the sum of the component values



RICE

Another Simple Circuit

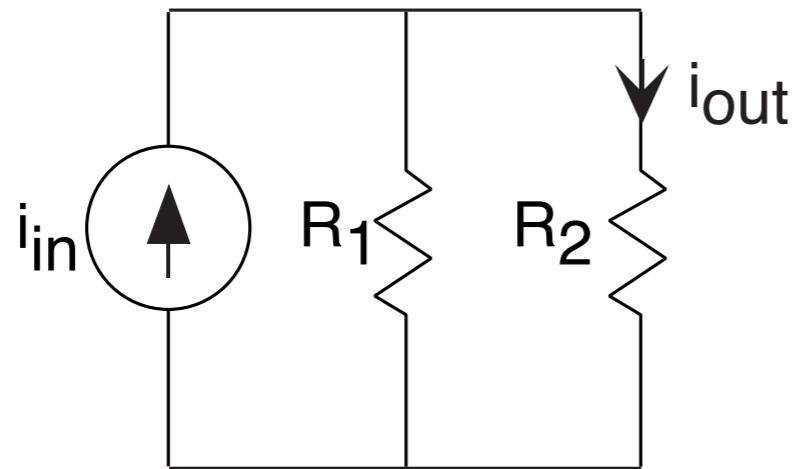

$$v-i: \quad v_1 = R_1 i_1$$

$$v_2 = R_2 i_{out}$$

$$\text{KCL: } i_{in} = i_1 + i_{out}$$



$$i_{out} = \frac{R_1}{R_1 + R_2} i_{in}$$

$$\text{KVL: } v = v_1$$


current divider

$$v_2 = v_1$$

Another Simple Circuit

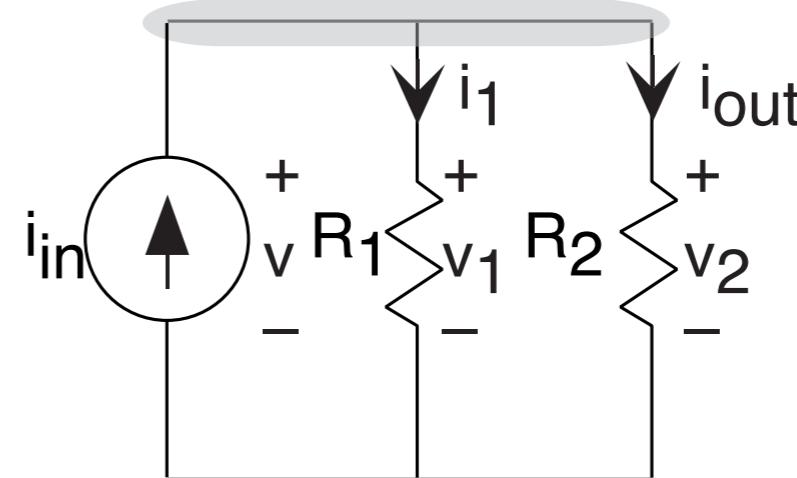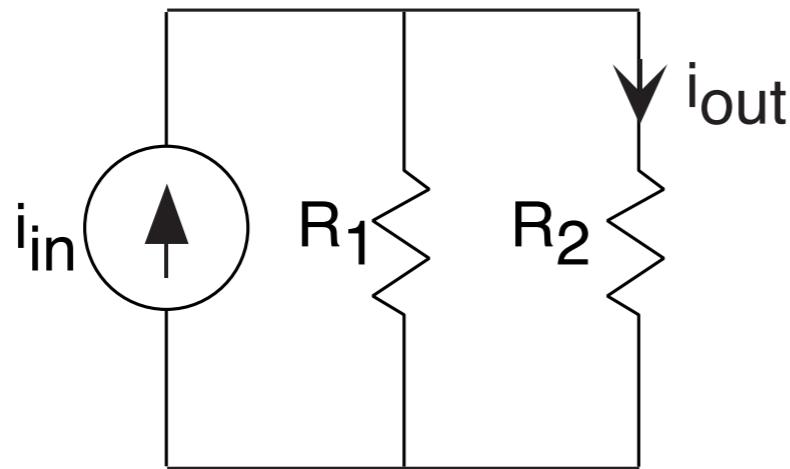
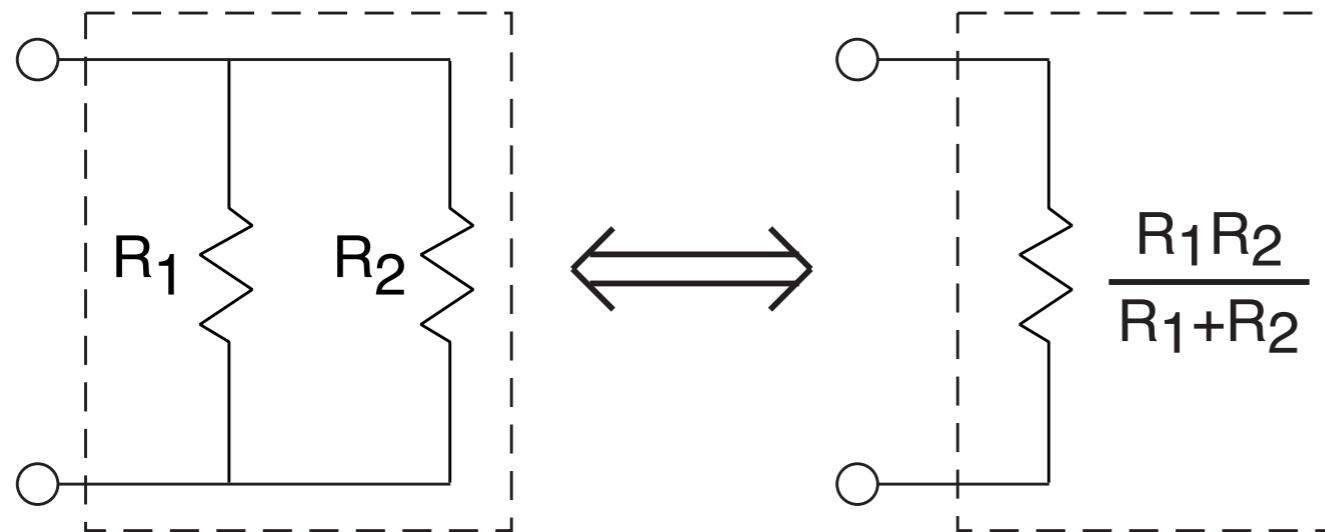
$$i_{out} = \frac{R_1}{R_1 + R_2} i_{in} \implies v = v_2 = \frac{R_1 R_2}{R_1 + R_2} i_{in}$$




$$R_1 \parallel R_2 \equiv \frac{R_1 R_2}{R_1 + R_2}$$




RICE

Using Equivalent Resistance

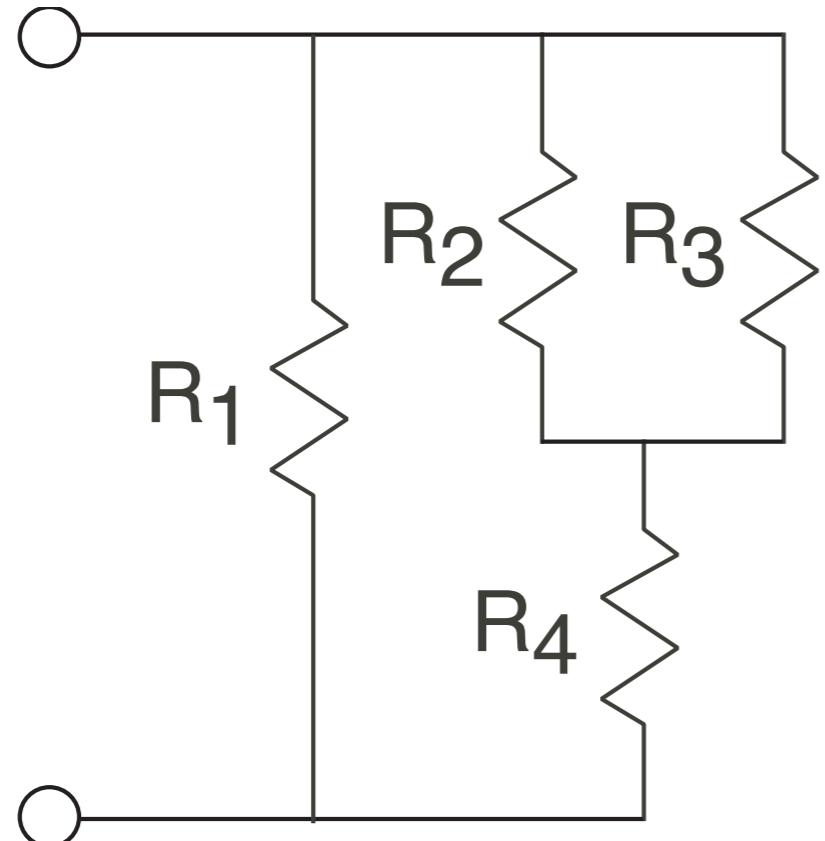


$$R_1 \parallel (R_2 \parallel (R_3 + R_4))$$

Solving a Circuit “the Easy Way”

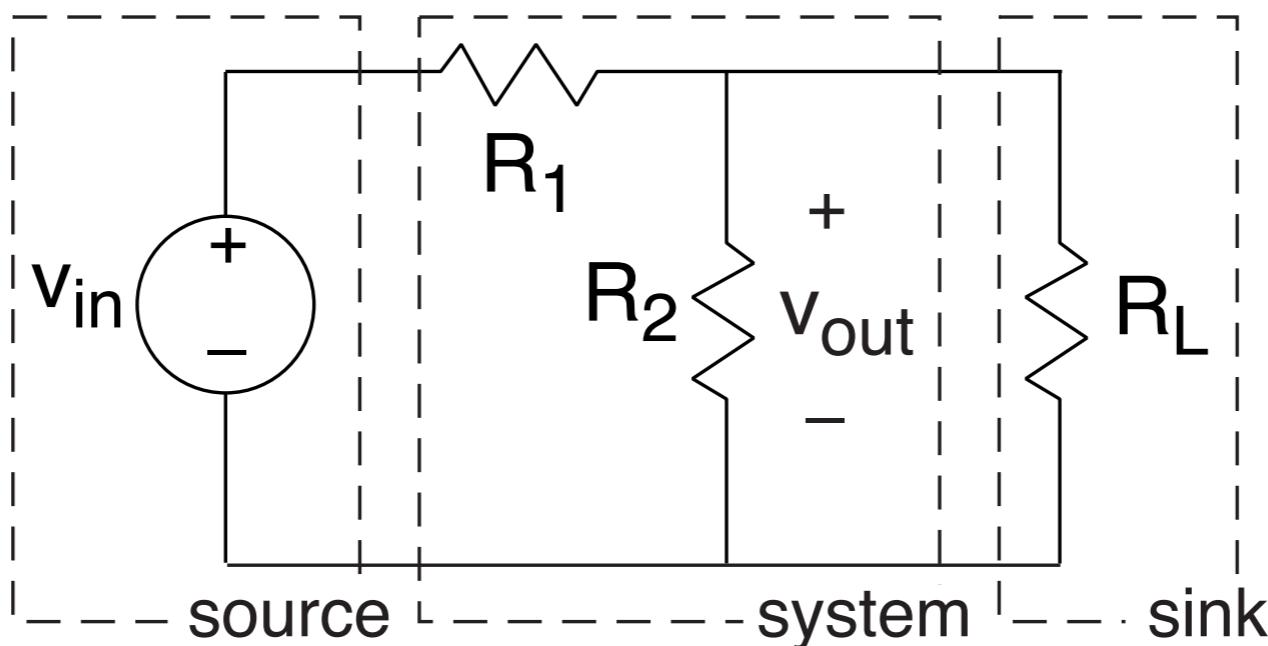


$$\begin{aligned}v_{out} &= \frac{R_2 \| R_L}{R_1 + R_2 \| R_L} v_{in} \\&= \frac{\frac{R_2 R_L}{R_2 + R_L}}{R_1 + \frac{R_2 R_L}{R_2 + R_L}} v_{in} \\&= \frac{R_2 R_L}{R_1 R_2 + R_1 R_L + R_2 R_L} v_{in}\end{aligned}$$

Resistor Equivalents

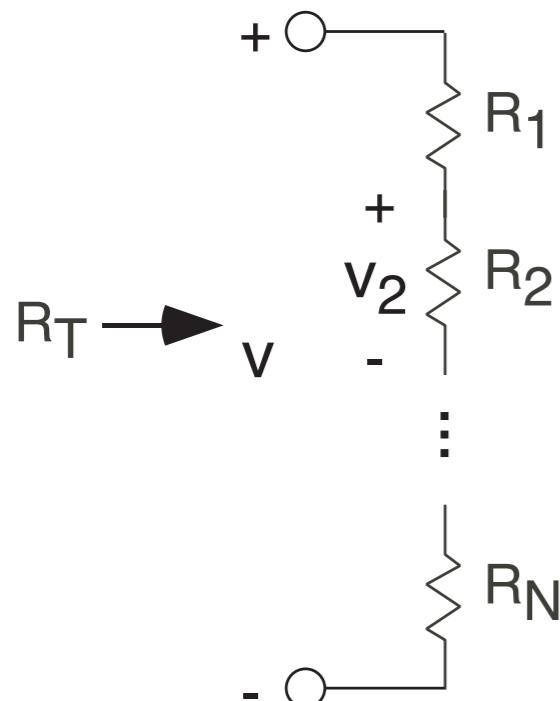
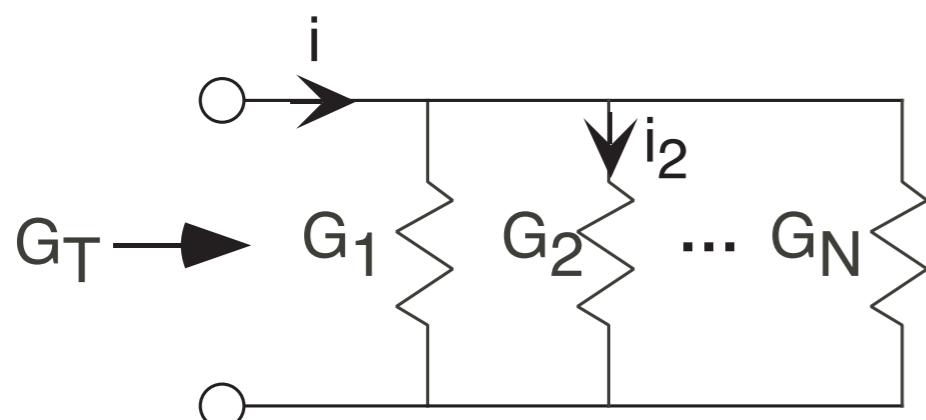
$$R_T = \sum_{n=1}^N R_n \quad v_2 = \frac{R_2}{R_T} \cdot v$$



$$G_T = \sum_{n=1}^N G_n \quad i_2 = \frac{G_2}{G_T} \cdot i$$



RICE

Solving Circuits

- Equivalent resistance, along with voltage and current divider, allows us to *easily* solve any circuit with resistors and sources
- Structure of a circuit: where are the series and parallel combinations?