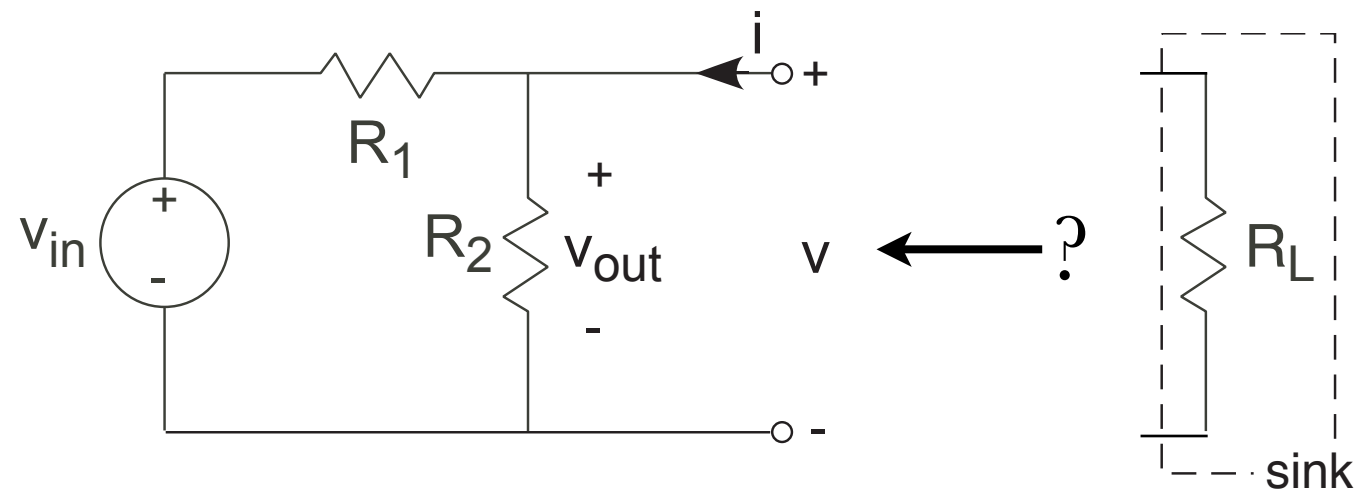


# Fundamentals of Electrical Engineering

## More Equivalent Circuits

- What do circuit elements “see”?
- Thévenin and Mayer-Norton equivalent circuits


# More Equivalent Circuits



## Principle of Superposition


$$v = v|_{v_{in}=0} + v|_{i=0}$$
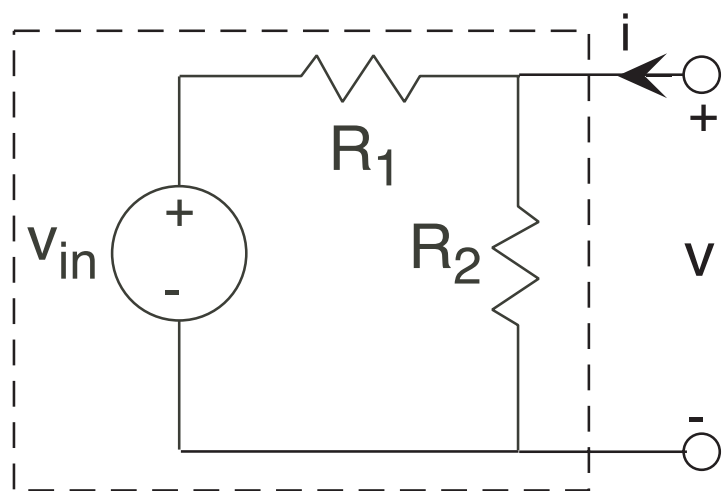
$$(R_1 \parallel R_2)i + \frac{R_2}{R_1 + R_2}v_{in}$$




$$v = (R_1 \parallel R_2)i + \frac{R_2}{R_1 + R_2}v_{in}$$

# But There's More!

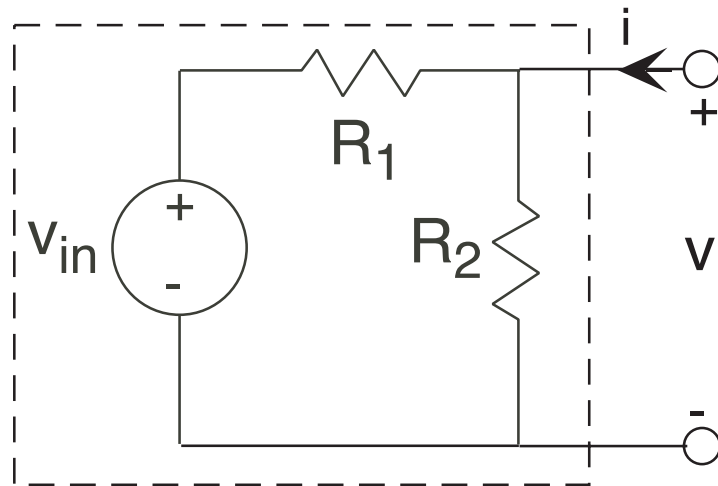

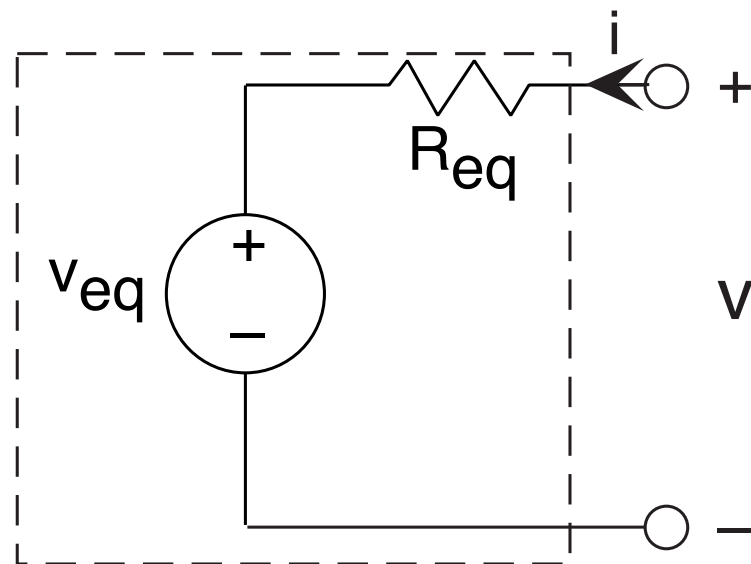
$$v = \underbrace{(R_1 \parallel R_2)}_{R_{eq}} i + \underbrace{\frac{R_2}{R_1 + R_2} v_{in}}_{v_{eq}}$$




$$v = R_{eq} i + v_{eq}$$

Thévenin equivalent circuit

# But There's Even More!

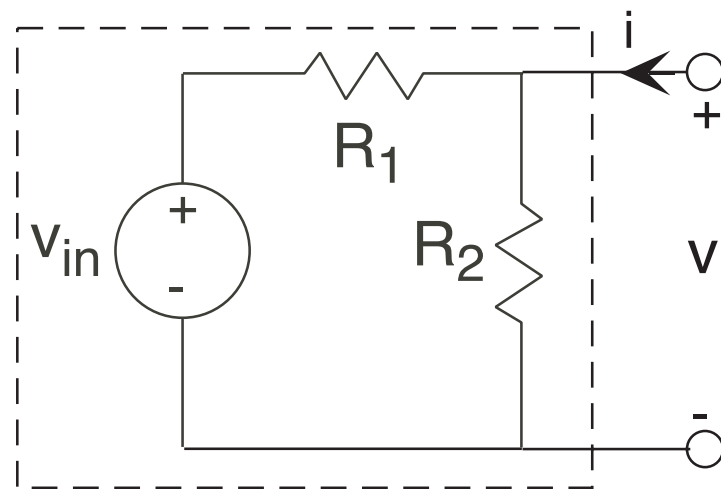


$$v = R_{eq}i + v_{eq}$$

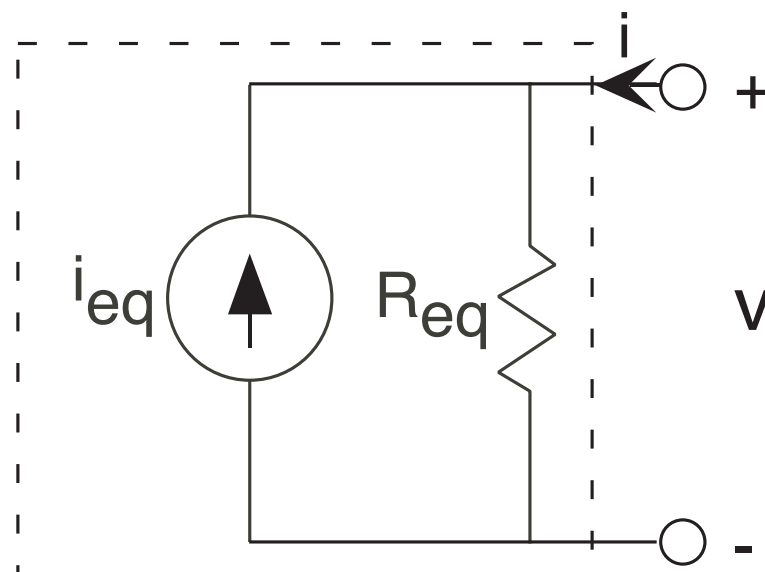

$$i = \frac{v}{R_{eq}} - \underbrace{\frac{v_{eq}}{R_{eq}}}_{i_{eq}}$$

Mayer-Norton equivalent circuit


# Equivalent Circuits

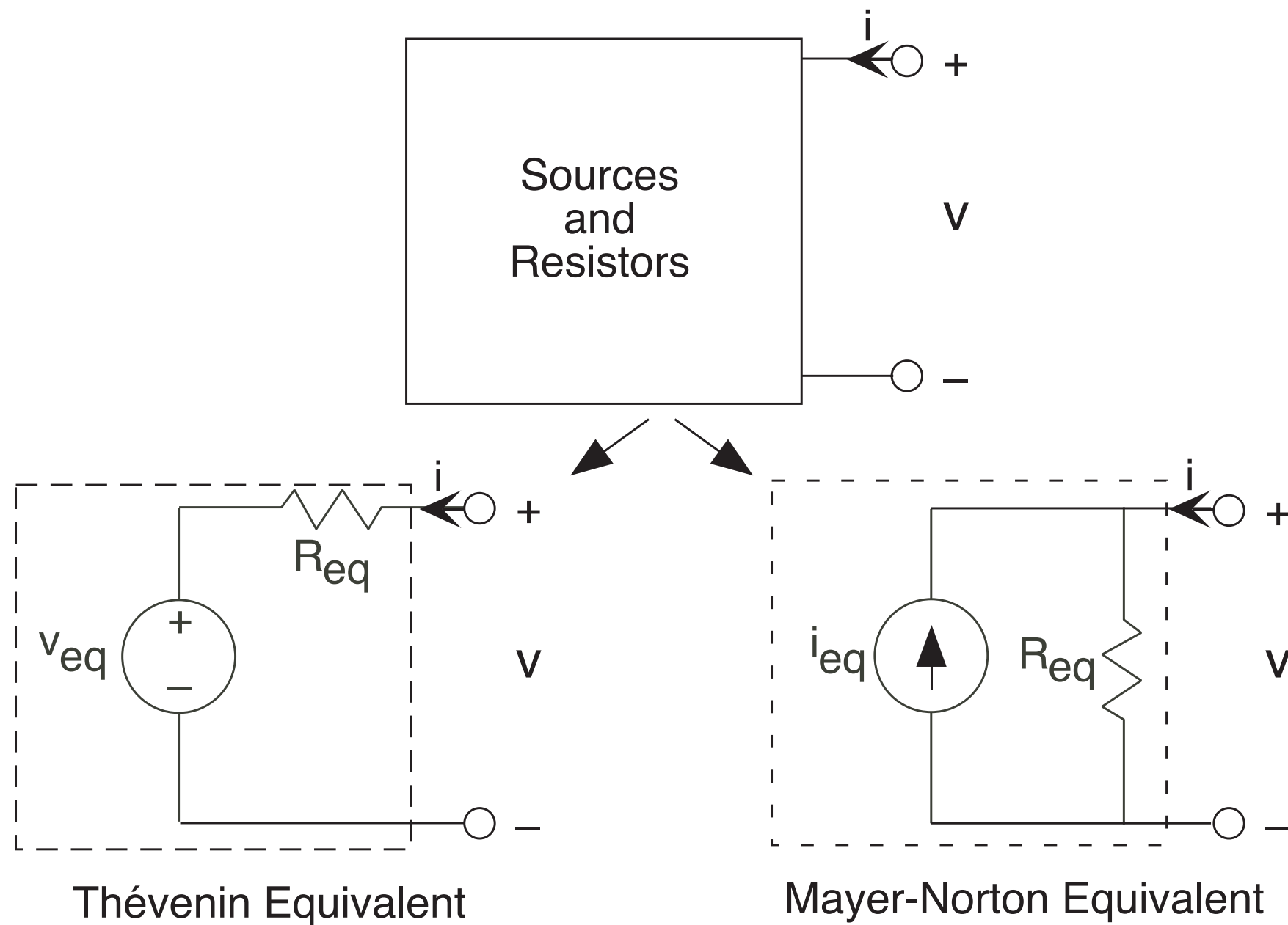

$$v_{eq} = R_{eq} i_{eq}$$
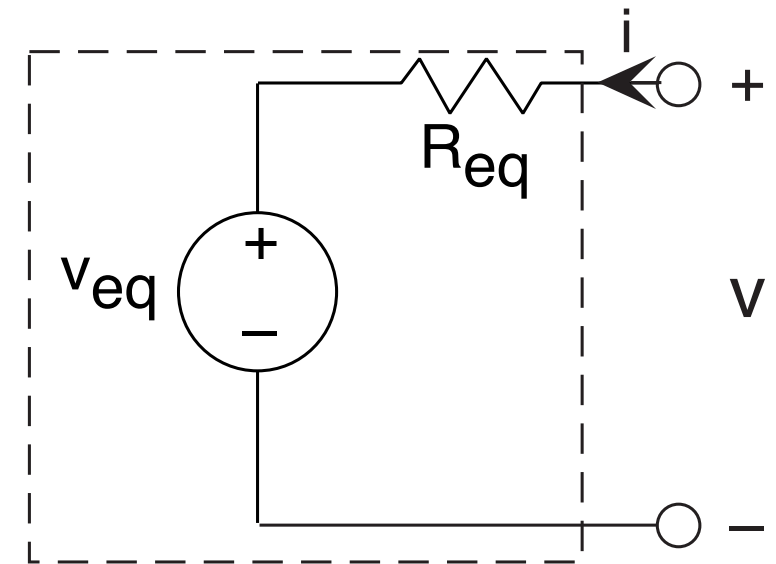
# Finding Equivalent Circuits

How do you find the equivalent circuit without “looking inside”?



Open-circuit voltage: Connect nothing to the terminals



$$i = 0 \implies v_{oc} = v_{eq} = R_{eq} i_{eq}$$

Short-circuit current: Connect a wire to the terminals

$$v = 0 \implies i_{sc} = -\frac{v_{eq}}{R_{eq}} = -i_{eq}$$

If you can “turn off” the sources, the resistance viewed from the terminals is  $R_{eq}$

# Example

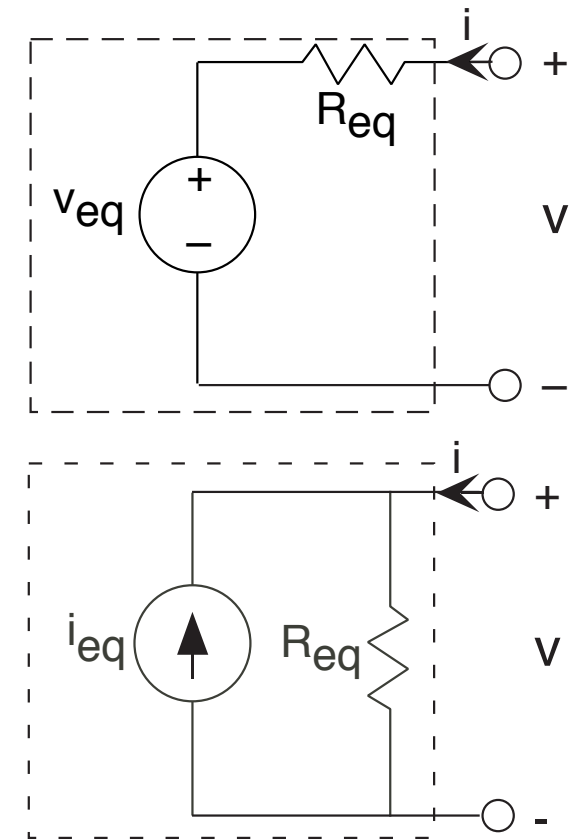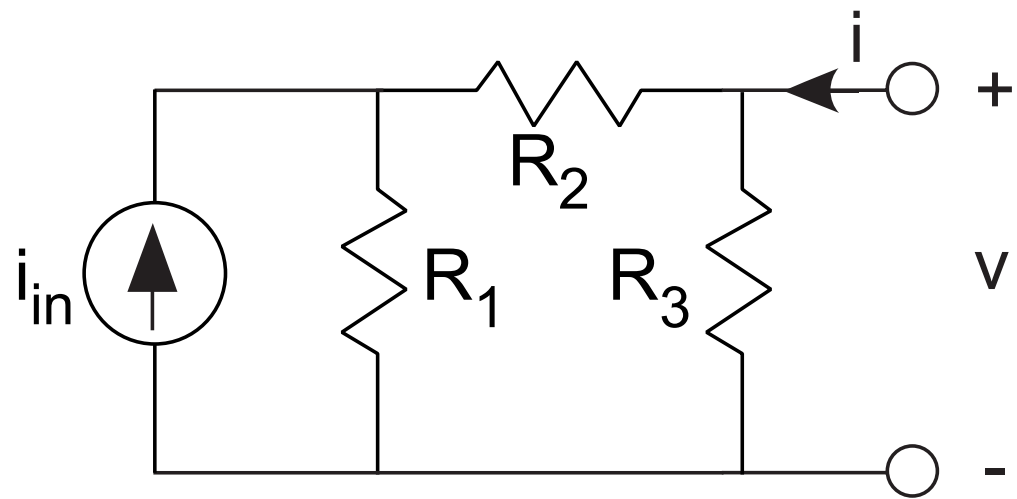

To find  $R_{eq}$ , set source(s) to zero.

$$i_{in} = 0: R_{eq} = R_3 \parallel (R_1 + R_2)$$

To find  $v_{eq}$ , find open-circuit voltage.


$$i = 0: v_{oc} = R_3 \cdot \frac{R_1}{R_1 + R_2 + R_3} i_{in} = v_{eq}$$

To find  $i_{eq}$ , find short-circuit current.

$$v = 0: i_{sc} = -\frac{R_1}{R_1 + R_2} i_{in} = -i_{eq}$$
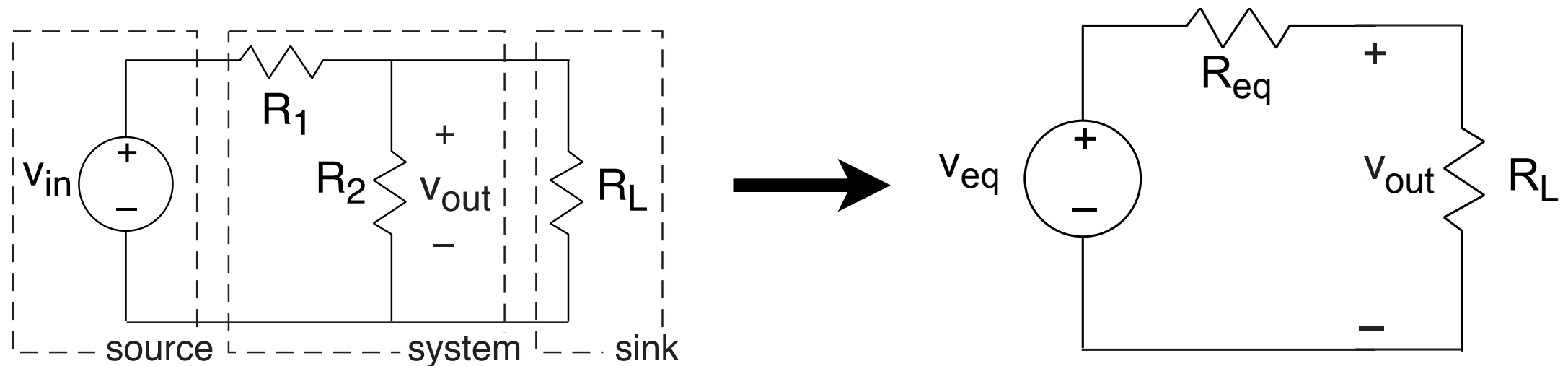
# Equivalent Circuits

- *All* circuits consisting of sources and resistors are equivalent to one source in series/parallel with one resistor
- Thévenin and Mayer-Norton equivalent circuits
- Remember “loading”?



$$v_{out} = \frac{R_L}{R_{eq} + R_L} v_{eq}$$