

# Feedback — RLC Circuit Exercises

You submitted this homework on **Wed 3 Apr 2013 2:06 PM CDT -0500**. You got a score of **0.00** out of **9.00**. You can [attempt again](#), if you'd like.

## Question 1

Checking units of expressions is an important way of achieving correct answers for impedances. The "secret" is to note that  $R$ ,  $LS$  and  $\frac{1}{CS}$  all have units of ohms ( $\Omega$ ).

What are the units of  $RLCs^2$ ?

Your Answer	Score	Explanation
<input type="radio"/> siemens ( $\Omega^{-1}$ )		
<input type="radio"/> ohms		
<input type="radio"/> dimensionless		
Total	0.00 / 1.00	

### Question Explanation

$LCs^2$  is dimensionless, making  $RLCs^2$  have units of ohms.

## Question 2

Is this expression correct:  $LCs^2 + R$ ?

Your Answer	Score	Explanation
<input type="radio"/> No		
<input type="radio"/> Yes		

Total

0.00 / 1.00

**Question Explanation**

No.  $LCs^2$  is dimensionless and  $R$  has units of ohms.

## Question 3

Can the following answer be correct?

$$Z = \frac{R_1 R_2 C s + R_3}{LCs^2 + RCs + 1}$$


Your Answer	Score	Explanation
<input type="radio"/> No		
<input type="radio"/> Yes		
Total	0.00 / 1.00	

**Question Explanation**

Numerator has units of ohms and the denominator is dimensionless. So, yes!
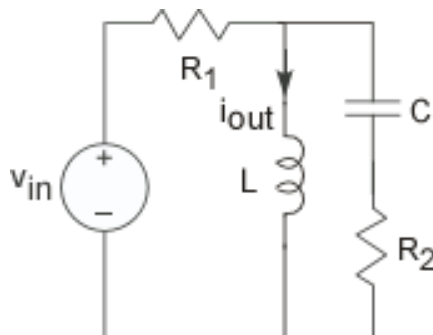
## Question 4

The following two questions concern this circuit.



What is the impedance of the circuit the voltage source "sees"?

Express your answer in terms of  $s = j2\pi f$ . Use  $R_1$ ,  $R_2$ ,  $L$ ,  $C$  for the element

values,  $R_1$ ,  $R_2$ ,  $L$  and  $C$ . For example, if

$$Z = \frac{R_1 L C s^2 + R_1 R_2 C s + 2 R_2}{L C s^2 + R_1 C s} \bigg|_{s=j2\pi f}$$

is your answer, type

$(R_1 * L * C * s^2 + R_1 * R_2 * C * s + 2 * R_2) / (L * C * s^2 + R_1 * C * s)$ . Because the expression is complicated, check units!

You entered:

Preview

[Help](#)

Your Answer	Score	Explanation
	✖ 0.00	Could not parse student submission
Total	0.00 / 1.00	

#### Question Explanation

$$Z = R_1 + L s \parallel \left( \frac{1}{C s} + R_2 \right) = \frac{(R_1 + R_2) L C s^2 + (R_1 R_2 C + L) s + R_1}{L C s^2 + R_2 C s + 1}$$

## Question 5

Find the transfer function between the complex amplitude  $V_{in}$  of the source and the output current's complex amplitude  $I_{out}$ .

Express your answer in terms of  $s = j2\pi f$ . For example, if

$$\frac{I_{out}}{V_{in}} = \frac{L C s^2 + R_1 C s}{R_1 L C s^2 + R_1 R_2 C s + 2 R_2} \bigg|_{s=j2\pi f}$$

is your answer, type

$(L * C * s^2 + R_1 * C * s) / (R_1 * L * C * s^2 + R_1 * R_2 * C * s + 2 * R_2)$ . Because the expression is complicated, check units!

You entered:

Preview

[Help](#)

Your Answer	Score	Explanation
	<span style="color: red;">✗</span> 0.00	Could not parse student submission
Total	0.00 / 1.00	


**Question Explanation**

We can use voltage divider to find the voltage across the inductor- $RC$  combination, then divide by the impedance of the inductor to find the current we need.

$$I_{\text{out}} = V_{\text{in}} \cdot \frac{Ls \parallel \left(R_2 + \frac{1}{Cs}\right)}{R_1 + Ls \parallel \left(R_2 + \frac{1}{Cs}\right)} \cdot \frac{1}{Ls} = V_{\text{in}} \cdot \frac{R_2 Cs + 1}{(R_1 + R_2)LCs^2 + (R_1 R_2 C + L)s + R_1}$$

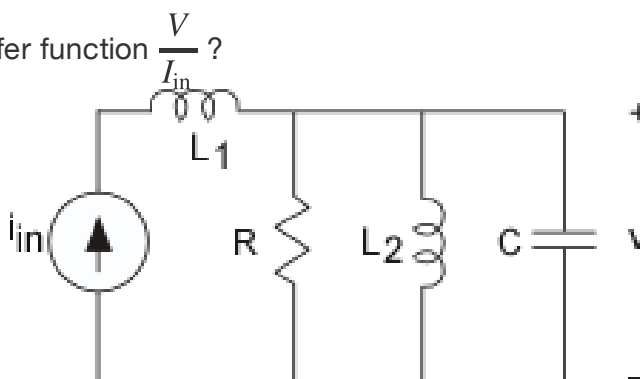**Question 6**

What is the transfer function  $\frac{V}{I_{\text{in}}}$  ?



Express your answer in terms of  $s = j2\pi f$ . Represent the element values  $R$ ,  $L_1$ ,  $L_2$  and  $C$  by  $R$ ,  $L1$ ,  $L2$  and  $C$  respectively.

You entered:

Preview

[Help](#)

Your Answer	Score	Explanation
<span style="color: red;">✗</span>	0.00	Could not parse student submission
Total	0.00 / 1.00	


**Question Explanation**

Because the inductor  $L_1$  is in series with the current source, it does not affect the behavior of the circuit. That leaves an RLC parallel combination. To find the voltage, we simply need the impedance. This impedance is the transfer function we seek.

$$Z = R \parallel L_2 s \parallel \frac{1}{Cs} = \frac{1}{\frac{1}{R} + \frac{1}{L_2 s} + Cs} = \frac{RL_2 s}{RL_2 Cs^2 + L_2 s + R}$$

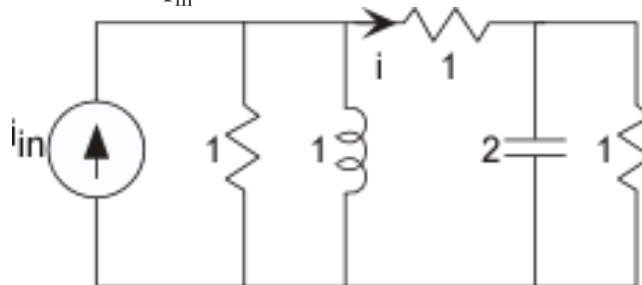**Question 7**

What is the transfer function  $\frac{I}{I_{\text{in}}}$  ?



Express your answer in terms of  $s = j2\pi f$  .

You entered:

Preview

[Help](#)

Your Answer	Score	Explanation
<span style="color: red;">✗</span>	0.00	Could not parse student submission
Total	0.00 / 1.00	

### Question Explanation

Perhaps the simplest approach is to use current divider expressed in terms of *admittance*  $Y$ . The admittance for an element is defined to be the reciprocal of impedance, just as conductance is the reciprocal of resistance. Here,


$$I = \frac{\frac{1}{1 + 1 \parallel \frac{1}{2s}}}{1 + \frac{1}{s} + \frac{1}{1 + 1 \parallel \frac{1}{2s}}} \cdot I_{\text{in}}$$

The term  $\frac{1}{1 + 1 \parallel \frac{1}{2s}}$  equals  $\frac{2s + 1}{2s + 2}$ . Consequently, the transfer function is

$$\frac{\frac{2s+1}{2s+2}}{1 + \frac{1}{s} + \frac{2s+1}{2s+2}} = \frac{s(2s + 1)}{4s^2 + 5s + 2}.$$
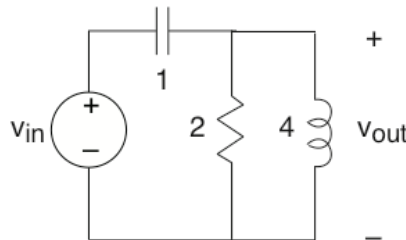
## Question 8

The following two questions concern this circuit.



Find the transfer function between the source and the indicated voltage.

Express your answer in terms of  $s = j2\pi f$ .

You entered:

Preview

[Help](#)

Your Answer	Score	Explanation
	✖ 0.00	Could not parse student submission
Total	0.00 / 1.00	

**Question Explanation**

Using voltage divider, we have  $\frac{2 \parallel 4s}{\frac{1}{s} + 2 \parallel 4s} = \frac{8s^2}{8s^2 + 4s + 2} = \frac{4s^2}{4s^2 + 2s + 1}$ .

**Question 9**

When the source is  $v_{in}(t) = 10 \sin\left(\frac{t}{2}\right)$ , what is the output voltage  $v(t)$ ?

Express your answer as a sinusoid: if  $4 \sin(2\pi t + \pi/4)$  is your answer, enter it as  $4 * \sin(2 * \pi * t + \pi / 4)$ .

You entered:

**Preview**

[Help](#)

Your Answer	Score	Explanation
	<span style="color: red;">✖</span> 0.00	Could not parse student submission
Total	0.00 / 1.00	

**Question Explanation**

The frequency of the source is  $\frac{1}{2\pi \cdot 2}$ , making  $s = j/2$ . Substituting this result into the transfer function, we have

$$\left. \frac{4s^2}{4s^2 + 2s + 1} \right|_{s=j/2} = \frac{4 \cdot \left(-\frac{1}{4}\right)}{4 \cdot \left(-\frac{1}{4}\right) + 2\left(\frac{j}{2}\right) + 1} = \frac{-1}{-1 + j + 1} = -\frac{1}{j} = j$$

Expressing the source as  $\text{Im}[10e^{jt/2}]$ , the output is given by  $\text{Im}[10je^{jt/2}] = 10 \cos\left(\frac{t}{2}\right)$ .

